

Design and implementation of a digital clock showing digits in Bangla font using microcontroller AT89C4051

Nasif Muslim, Md. Tanvir Adnan, Mohammad Zahidul Kabir, Md. Humayun Kabir, Sheikh Mominul Islam
American International University-Bangladesh (AIUB), Bangladesh

Abstract—In this paper, a digital clock is designed where the microcontroller is used for timing controller and the font of the Bangla digits are designed, and programmed within the microcontroller. The design is cost effective, simple and easy for maintenance.

I. INTRODUCTION

A clock is an instrument for measuring time. In principle, it requires no more than some physical process which will proceed at a known rate, and a way to gauge how long that process has been continuing. There are different types and sizes of clocks are available.

Depending on the method of time display, clocks can be classified by four types. They are i) analog clocks, ii) digital clocks, iii) auditory clocks, iv) textual clocks. Digital clocks display a numeric representation of time. Two numeric display formats are commonly used on digital clocks. They are: 24-hour notation with hours ranging 00 to 23 and 12 hour notation with AM/PM indicator. Most digital clocks use an LCD or LED display.

Generally for the designing a digital clock, a microcontroller is used as the controller of the circuit and a Real Time Clock IC [4] is used as counter. But for displaying a Bangla digit character set in Seven Segment Display [5], it is required to use about a hundred or more NAND/NOR gate. It is not feasible to use so many gates and it will increase the size of the hardware too. To solve this problem, bangla digits are designed and programmed in the microcontroller and LCD display [1] is used as a display.

II. SOFTWARE DESIGN

The software design process consists of two steps.

- 1) Bangla digit design
- 2) Clock algorithm design

A. Bangla digit design

Bascom-8051 [3] is used to design and simulate Bangla digits. It is a windows BASIC compiler for the AVR family microcontroller. The main advantage of using this software is that, it has an LCD designer by which it is possible to design custom characters or digits for LCD display. It is also possible to examine the custom design using LCD simulator.

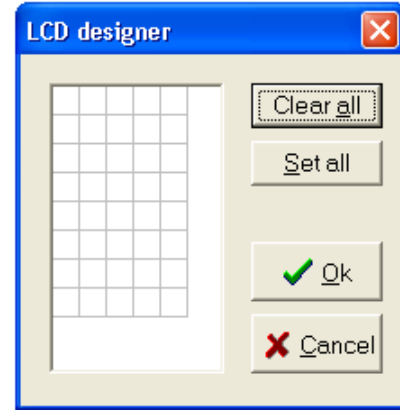


Figure 1. LCD designer - the LCD matrix has 7x5 cells

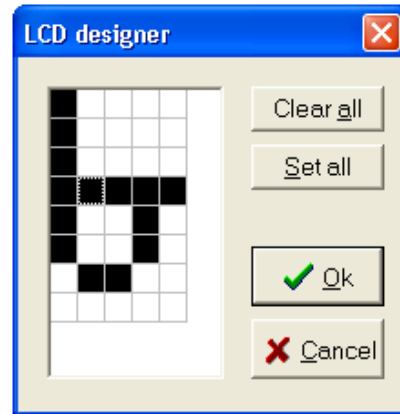


Figure 2. Bangla digit "8" is designed in the LCD designer

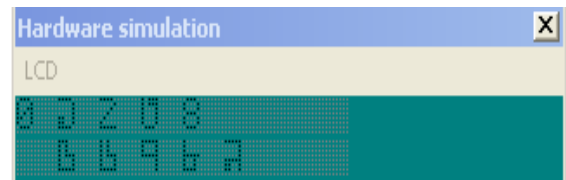


Figure 3. LCD simulator - Ten Bangla digits

B. Clock algorithm design

Clock algorithm design consists of two steps.

- 1) Time counting process
- 2) Time adjustment process

1) *Time counting process*: The responsibility of this process is to count time. At beginning of the process *hour*, *minute* and *second* are set to zero. After passing each second, *second* is incremented and checked if it exceeds fifty-nine. When *second* exceeds fifty-nine then *second* is set to zero and *minute* is incremented. After passing one minute, it is checked if *minute* exceeds fifty-nine. when *minute* exceeds fifty-nine then *minute* is set to zero and *hour* is incremented. After passing one hour, it is checked if *hour* exceeds twenty-three. When *hour* exceeds twenty-three then *hour* is set to zero and the process continues all over again.

2) *Time adjustment process*: The responsibility of this process is to adjust time. This process starts when the user has pressed the *SET* button. Then, it is checked if the *INCREMENT* button is pressed. If *Yes* then *hour* is incremented and checked if the value is twenty-four. If *Yes* then *hour* is set to zero. On the other hand, if the *DECREMENT* button is pressed then *hour* is decremented and checked if the value is minus one. If *Yes* then *hour* is set to twenty-three.

The user again presses the *SET* button for modifying minutes. It is checked if the *INCREMENT* button is pressed. If *Yes* then *minute* is incremented and checked if the value is sixty. If *Yes* then *minute* is set to zero. If the *DECREMENT* button is pressed then *minute* is decremented and checked if the value is minus one. If *Yes* then *minute* is set to fifty-nine.

Similarly, the user again presses the *SET* button for altering seconds. It is checked if the *INCREMENT* button is pressed. If *Yes* then *second* is incremented and checked if the value is sixty. If *Yes* then *second* is set to zero. if the *DECREMENT* button is pressed then *second* is decremented and checked if the value is minus one. If *Yes* then *second* is set to fifty-nine.

Now, the user again presses the *SET* button to stop the process.

III. DESIGN OF DIGITAL CLOCK

The design of a clock circuit includes three units. They are input unit, processing unit and output unit. For input three push button switches are used which reset the time of the clock. For processing a microcontroller AT89C4051 [2] is used. And for output 16*2 LCD display is used.

A. List of circuit components

Component name	Quantity
AT89C4051	1
16*2 LCD	1
IN4001 diode	1
11.06Mhz crystal oscillator	1
10K potentiometer	1
10K resistor	3
8.2 resistor	1
Push button switch	3
30pF capacitor	2
10uF capacitor	2
0.1uF capacitor	1
9V battery	1

B. Circuit description

The three switches set, increment and decrement of the clock are connected to microcontroller through port P3.2, P3.1 and P3.0 shown in figure 6. The crystal oscillator of the clock is connected to the microcontroller through pin no. 5 and 4. The upper four bits of the LCD display is connected to microcontroller pin no. P1.7, P1.6, P1.5, P1.4. The enable, reset pin of the LCD is connected to the microcontroller with pin no. 15 and 14. The R/W pin of the microcontroller is connected to the ground. The contrast of the LCD is connected to the potentiometer. The power supply connection is connected to the pin no. 20 and ground connection is to the pin no. 10.

IV. SOURCE CODE IMPLEMENTATION

The source code is written in BASIC language.

A. Change hour

```
1 If P3.2 = 0 Then
2   Do
3     If P3.1 = 0 Then
4       Incr Hh
5       If Hh = 24 Then
6         Hh = 0
7       End If
8     End If
9
10    If P3.0 = 0 Then
11      Decr Hh
12      If Hh = -1 Then
13        Hh = 23
14      End If
15    End If
16
17    If P3.2 = 0 Then
18      Exit Loop
19    End If
20  Loop
21 End If
```

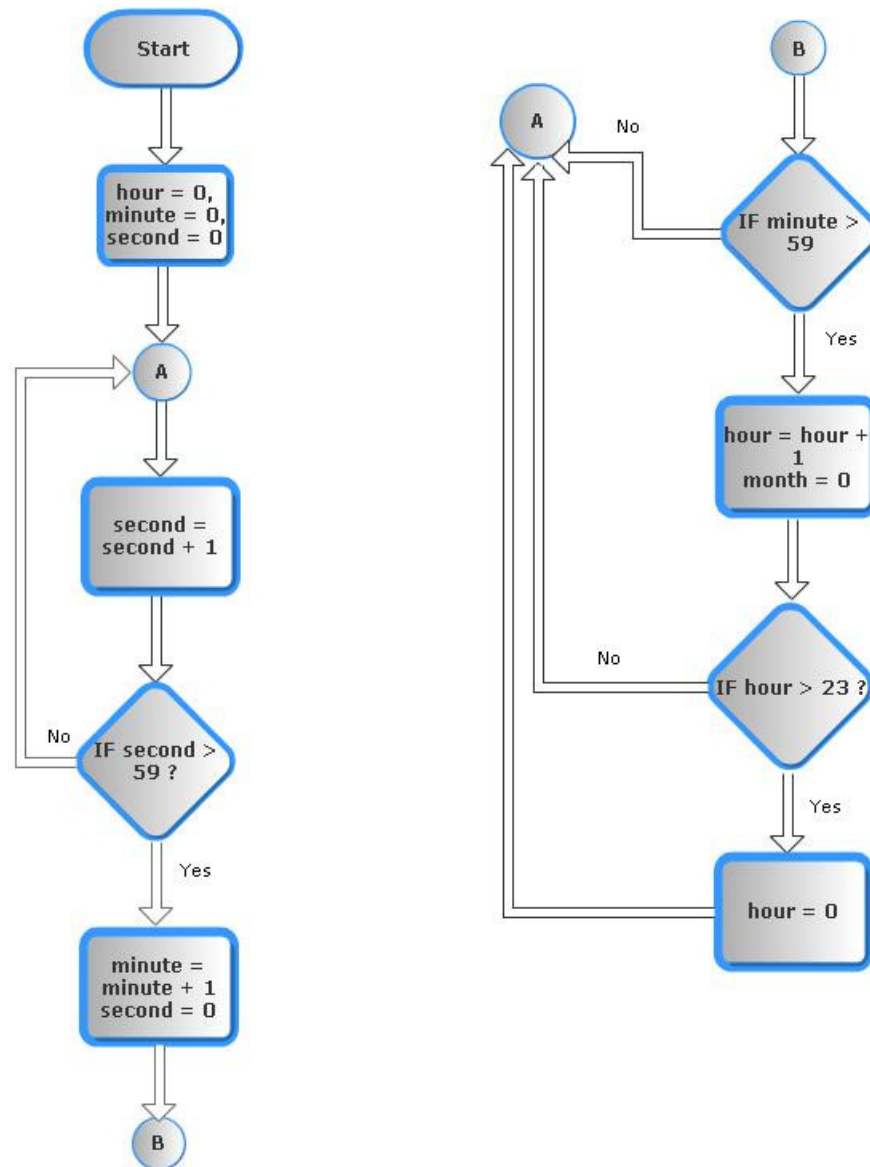


Figure 4. Time counting process flowchart

B. Change minute

```

1 If P3.2 = 0 Then
2   Do
3     If P3.1 = 0 Then
4       Incr Mm
5       If Mm = 60 Then
6         Mm = 0
7       End If
8     End If
9
10    If P3.0 = 0 Then
11      Decr Mm
12      If Mm = -1 Then
13        Mm = 59
14      End If
15    End If
16  
```

```

17    If P3.2 = 0 Then
18      Exit Loop
19    End If
20  Loop
21 End If
  
```

C. Change second

```

1 If P3.2 = 0 Then
2   Do
3     If P3.1 = 0 Then
4       Incr Ss
5       If Ss = 60 Then
6         Ss = 0
7       End If
8     End If
9
10    If P3.0 = 0 Then
  
```

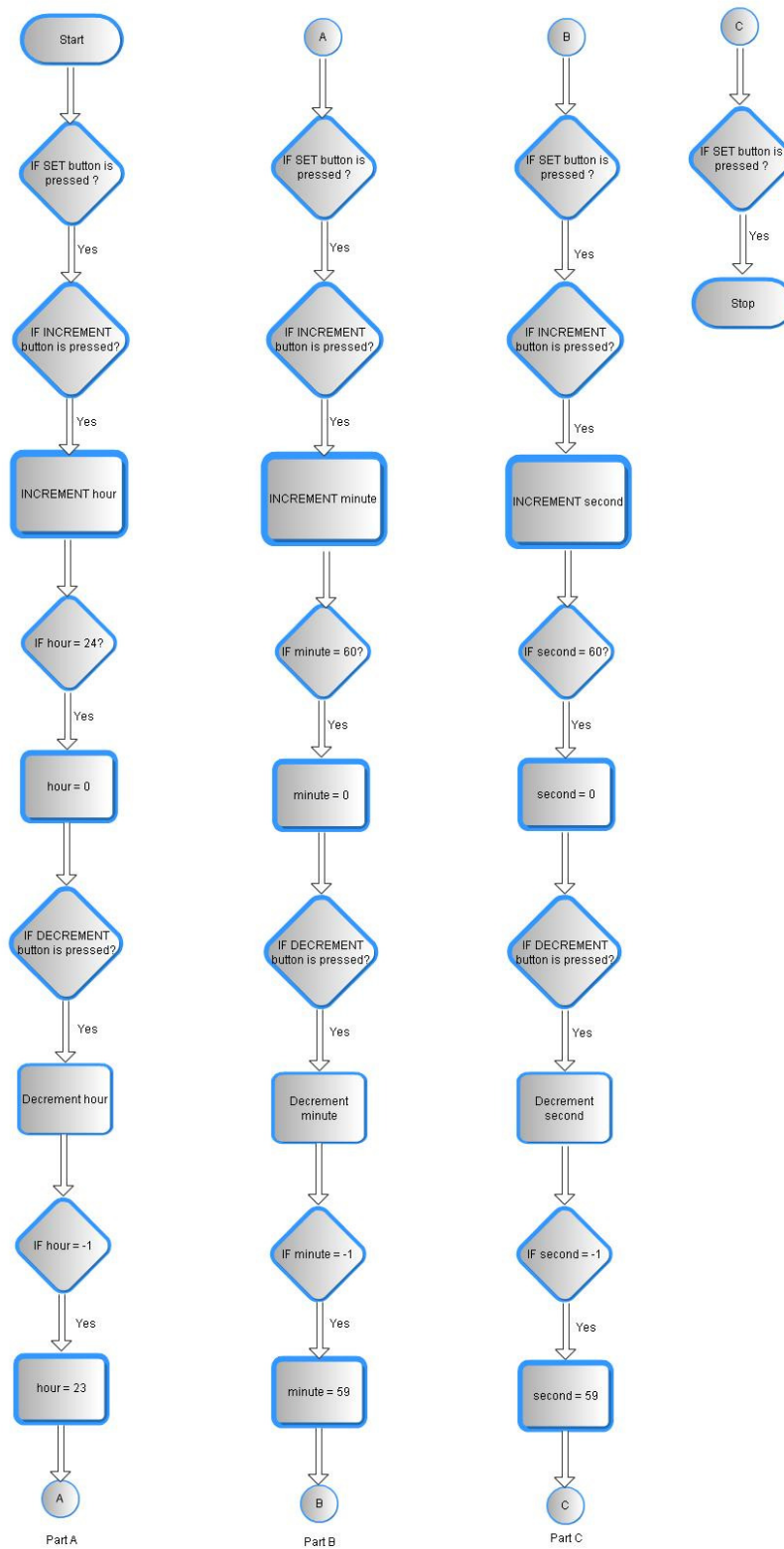


Figure 5. Time adjustment process flowchart

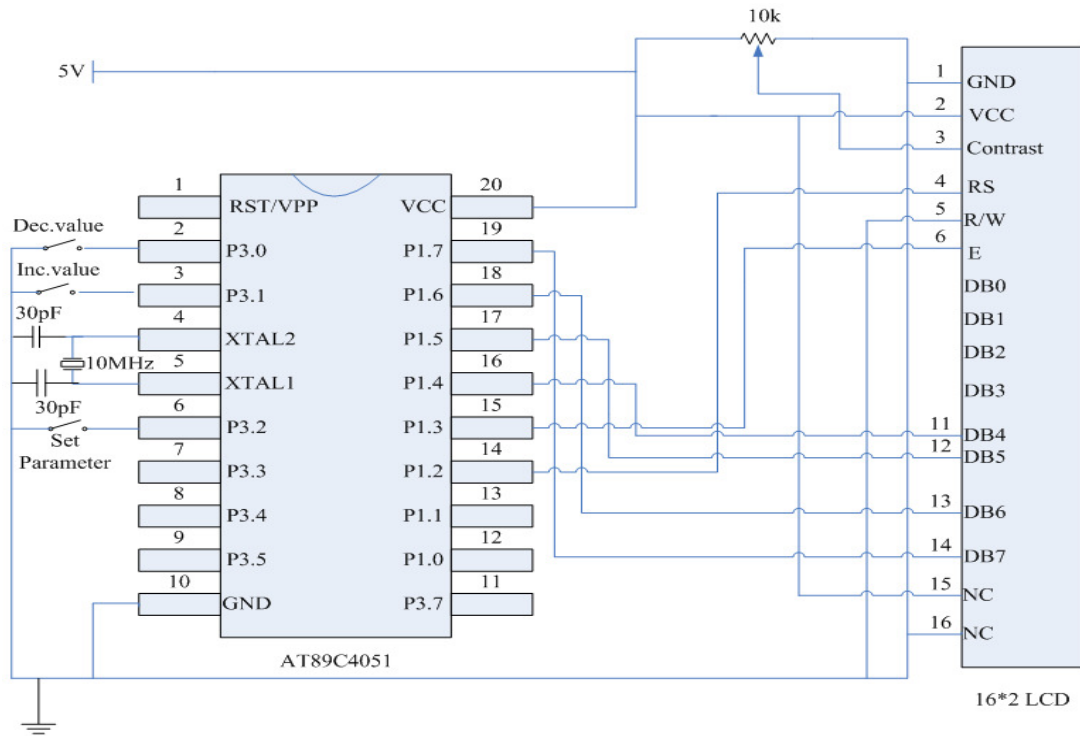


Figure 6. Circuit diagram of digital Bangla clock

```

11 Decr Ss
12 If Ss = -1 Then
13     Ss = 59
14 End If
15 End If
16
17 If P3.2 = 0 Then
18     Exit Loop
19 End If
20 Loop
21 End If

```

font of the clock is Bangla. The design of the Bangla digital clock is small and easy to use like other digital clocks.

It is possible to enhance the capability of this digital clock. With some hardware and software modification, it can become a fully automatic digital alarm clock showing digits in Bangla. This digital Bangla clock can be more useful if it can provide information like 12 hour clock or 24 hour clock, days of a week, month names, year etc. This features can be added very easily by software modification. In this design, 16*2 LCD display is used and first eight blocks is used to display second, minute and hour. So there are another eight blocks left to show additional information. The microcontroller AT89C4051 which has 4K memory, has enough memory space available for the additional programming of the microprocessor. The display of the digital Bangla clock can be more attractive by using graphic LCD.

REFERENCES

- [1] Vishay electronic gmbh, 16 x 2 Character LCD datasheet.
- [2] Atmel corporation, Atmel AT89C4051 datasheet.
- [3] Mcs electronics, BASCOM-AVR.
- [4] Dallas semiconductor, DS12885 Real Time Clock datasheet.
- [5] Avago technologies, HDSP Series datasheet.

Figure 7. Digital clock showing digits in Bangla

V. SUMMARY AND FUTURE WORK

To implement a simple timer or counter is trivial, but to design and implement a digital clock showing real time is a complex task. The task becomes more complex when the

