# Computing all monomials of degree n-1 using 2n-3 AND gates

### Thomas Häner<sup>†</sup>

<sup>†</sup>Amazon Quantum Solutions Lab, Zürich, Switzerland

#### Abstract

We consider the vector-valued Boolean function  $f:\{0,1\}^n \to \{0,1\}^n$  that outputs all n monomials of degree n-1, i.e.,  $f_i(x) = \bigwedge_{j\neq i} x_j$ , for  $n\geq 3$ . Boyar and Find have shown that the multiplicative complexity of this function is between 2n-3 and 3n-6. Determining its exact value has been an open problem that we address in this paper. We present an AND-optimal implementation of f over the gate set  $\{AND, XOR, NOT\}$ , thus establishing that the multiplicative complexity of f is exactly 2n-3.

# 1 Introduction

The multiplicative complexity of a Boolean function  $f:\{0,1\}^n \to \{0,1\}^m$  is the minimal number of AND gates required to implement f over  $\{\land, \oplus, 1\}$ , where  $\land$  is the logical AND of two Boolean inputs,  $\oplus$  computes the exclusive OR of an arbitrary number of Boolean inputs, and the constant 1 input can be used to invert a Boolean input  $\overline{x} = x \oplus 1$ . The multiplicative complexity is thus a good measure of the implementation cost of a function in cases where AND gates are much more costly than XOR gates. This is the case, for example, in fault-tolerant quantum computing [1] and secure computation protocols [2].

While it is computationally intractable to compute the multiplicative complexity for a general function [3], there are specific (classes of) functions for which the exact multiplicative complexity is known [4, 5, 6, 7].

Boyar and Find [8] have shown that the vector-valued Boolean function f(x) where each output  $f_i(x)$  for  $i \in \{1, ..., n\}$  is given by

$$f_i(x) = \bigwedge_{j \in \{1, \dots, n\} \setminus \{i\}} x_j \tag{1}$$

has multiplicative complexity between 2n-3 and 3n-6. Boyar and Find prove the lower bound using an iterated algebraic degree argument, and they provide a construction that computes f(x) with 3n-6 AND gates.

**Our contribution.** We improve upon the construction by Boyar and Find, and present an AND-optimal implementation of f(x) using 2n-3 AND gates, allowing us to conclude that the multiplicative complexity of f(x) is exactly 2n-3. This solves an open problem from Ref. [8].

# 2 Preliminaries

**Definition 1** (Algebraic Normal Form (ANF)). For a Boolean function  $f: \{0,1\}^n \to \{0,1\}$ , its algebraic normal form is the unique representation

$$f(x) = \bigoplus_{I \subset \{1, \dots, n\}} a_I \bigwedge_{i \in I} x_i,$$

with  $a_I \in \{0,1\}$  and  $x_i$  denoting the ith bit of the integer  $x \in \{0,...,2^n-1\}$ . Each  $\bigwedge_{i \in I} x_i$  where  $a_I = 1$  is called a monomial of f.

**Definition 2** (Algebraic Degree). For a Boolean function  $f : \{0,1\}^n \to \{0,1\}$ , its algebraic degree, denoted by  $\deg(f)$  is

$$\deg(f) = \max_{I \subset \{1, \dots, n\}} a_I |I|,$$

where  $a_I \in \{0,1\}$  denote the ANF coefficients of f and |I| is the number of elements in the set I.

**Definition 3** (Multiplicative Complexity). For a Boolean function  $f: \{0,1\}^n \to \{0,1\}$ , its multiplicative complexity, denoted by  $c_{\wedge}(f)$ , is defined as the smallest number of AND gates in any implementation of f consisting only of AND gates with two Boolean inputs, exclusive OR gates, and NOT gates.

One general way to obtain a lower bound on the multiplicative complexity of a function is by the degree lower bound [9].

**Lemma 1** (Proposition 3.8 in [9]). For all Boolean functions f, it holds that  $c_{\wedge}(f) \geq deg(f) - 1$ .

We use the short-hand notation  $x_1 \cdots x_n$  to represent  $\bigwedge_{i=1}^n x_i$ , and we refer to the computation of a logical AND of two Boolean values x, y, i.e.,  $x \wedge y$ , as multiplication of x by y. Similarly, we refer to the computation of a logical exclusive OR (XOR) of x and y, i.e.,  $x \oplus y$ , as addition (modulo 2).

We say a monomial has a "gap" at  $x_k$  if the monomial is of the form  $\bigwedge_{i \in I} x_i$  and  $k \notin I$ . When writing down monomials explicitly as  $x_i x_j \cdots x_m$ , we assume that the variables have been ordered such that  $i < j < \cdots < m$ . Similarly, we say that a multiplication of a monomial  $x_i x_j \cdots x_m$  by  $x_n$  appends  $x_n$  to the monomial if m < n.

# 3 Construction

In this section, we present an AND-optimal construction to evaluate f(x) using 2n-3 AND gates.

We evaluate f(x) in 3 stages. The first stage computes the XOR of all monomials of degree n-1, i.e., for n inputs  $x_1, ..., x_n$  the output of the first stage is

$$s_0^n := \bigoplus_{i=1}^n \bigwedge_{j \neq i} x_j \tag{2}$$

and it computes this output using n-2 AND gates (which is optimal by the degree lower bound).

The second stage produces an additional n-1 intermediate outputs starting from  $s_0^n$ . Specifically, if n is odd, then each of these additional outputs is the XOR of two monomials from  $s_0^n$  such that all n intermediate outputs are linearly independent, i.e., all monomials can be extracted from these n intermediate outputs using XORs. If n is even, then the same is true for the first n-2 outputs of the second stage, but the final output is just the monomial  $x_1, ..., x_{n-1}$ . In both cases, the number of AND gates used by the second stage is n-1.

The third and final stage combines the n-1 outputs of the second stage with  $s_0^n$  using XORs in order to generate the n different monomials corresponding to the n outputs of f(x). The total number of AND gates used to evaluate f(x) is then (n-2)+(n-1)=2n-3.

#### 3.1 Stage 1

The goal of the first stage is to compute  $s_0^n$  using n-2 AND gates. We treat the case where n is odd separately from the even case, and we start by assuming that n is odd. In this case, we first compute, for all  $i \in \{1, ..., \frac{n-1}{2}\}$ ,

$$t_{i} := x_{2i} \oplus \left[ (\bigoplus_{j=1}^{2i} x_{j}) \wedge (x_{2i} \oplus x_{2i+1}) \right]$$
$$= (\bigoplus_{j=1}^{2i-1} x_{j} x_{2i}) \oplus (\bigoplus_{j=1}^{2i} x_{j} x_{2i+1}).$$

For each i,  $t_i$  is the XOR of all degree-2 monomials where the larger index of the two variables is either 2i or 2i + 1.

We proceed by multiplying all of the  $t_i$ s together using  $\frac{n-1}{2}-1$  AND gates. We claim that the result is  $s_0^n$  and the number of AND gates is  $2\frac{n-1}{2}-1=n-2$ , as desired. We now show that the result is indeed the expression in (2), before describing the steps needed for even n.

**Lemma 2.** Let the number of inputs n be odd and let  $t_i$  for  $i \in \{1, ..., \frac{n-1}{2}\}$  be defined as above. Then,

$$T_{\frac{n-1}{2}} := \bigwedge_{i=1}^{\frac{n-1}{2}} t_i = \bigoplus_{i=1}^n \bigwedge_{j \neq i} x_j = s_0^n$$

*Proof.* We prove the statement by induction on  $p := \frac{n-1}{2}$ . First, note that the ANF of each  $t_i$  contains all degree-2 monomials  $x_k x_j$  with  $j \in \{2i, 2i+1\}$  and k < j. For p = 1,  $t_1 = x_2 \oplus (x_1 \oplus x_2)(x_2 \oplus x_3) = x_1 x_2 \oplus x_1 x_3 \oplus x_2 x_3$ , as claimed. For the induction step, we assume that the statement holds for p, i.e.,

$$T_p = \bigwedge_{i=1}^p t_i = s_0^n,$$

and we show that  $T_{p+1} = s_0^{n+2}$ .

Since n is odd, there is an odd number of monomials in the ANF of  $T_p$ , and each monomial is of degree n-1, which is even. Let us consider what happens upon multiplication of  $T_p$  by  $t_{p+1}$ , i.e.,  $T_{p+1} = T_p \wedge t_{p+1}$ : We multiply each monomial in the ANF of  $T_p$  by all degree-2 monomials in  $t_{p+1}$  and sum the results (modulo two). For each monomial  $x_{i_1} \cdots x_{i_{2p}}$  in  $T_p$ , there are 2p degree-2 monomials  $\{x_{i_1}x_m, \dots, x_{i_{2p}}x_m\}$  in  $t_{p+1}$  that, upon multiplication by  $x_{i_1} \cdots x_{i_{2p}}$ , yield the same degree-(2p+1) monomial. Since the number of such degree-2 monomials is even for each of the two possible values of  $m \in \{2p + 2, 2p + 3\}$ and for each monomial from  $T_p$ , there will be no degree-(2p+1) monomials in the ANF of  $T_{p+1}$ . The remaining cases to consider are collision-free, i.e., multiplications between monomials that have no variables in common. This corresponds to either (1) a multiplication by the degree-2 monomial  $x_{2n+2}x_{2n+3}$ , which does not result in a collision and produces a unique new monomial in  $T_{p+1}$  for each monomial in  $T_p$ , or (2) a multiplication of a monomial that has a gap at index i by the degree-2 monomial  $x_i x_m$  with  $m \in \{2p+2, 2p+3\}$ . It is easy to see that (1) ensures that all monomials containing both  $x_{2p+2}$  and  $x_{2p+3}$  are present in the ANF of  $T_{p+1}$ . To see that (2) adds the two missing monomials  $x_1 \cdots x_n x_m$  with  $m \in \{2p+2, 2p+3\}$ , note that for each monomial in  $T_p$  and for each m, there is exactly one degree-2 monomial in  $t_{p+1}$  that, upon multiplication, results in  $x_1 \cdots x_n x_m$ . Since the number of monomials in  $T_p$  is odd, both monomials  $x_1 \cdots x_n x_m$  are generated an odd number of times and thus will be present in  $T_{p+1}$ .

This completes the first stage when n is odd. If n is even, we use the construction above for n' := n-1, which requires n'-2=n-3 AND gates, and we then multiply  $T_{\frac{n-2}{2}}$  by  $\bigoplus_{i=1}^n x_i$ . We claim that this results in the expression in (2) when n is even. The number of AND gates is again n-2, as desired.

**Lemma 3.** Let the number of inputs n be even and let  $T_{\frac{n-2}{2}}$  be defined as in Lemma 2. Then,  $s_0^n$  can be computed via

$$s_0^n = T_{\frac{n-2}{2}} \wedge \bigoplus_{i=1}^n x_i$$

*Proof.* The ANF of  $T_{\frac{n-2}{2}}$  contains all n-1 monomials of degree n-2 containing the variables  $x_1, ..., x_{n-1}$ . The multiplication of each of these monomials by each  $x_i$  for  $i \in \{1,...,n\}$  can be categorized into three separate cases: (1)  $x_n$  being appended to the monomial from  $T_{\frac{n-2}{2}}$ , (2)  $x_i$  ( $i \neq n$ ) filling the "gap" in the monomial from  $T_{\frac{n-2}{2}}$ , and (3)  $x_i$  ( $i \neq n$ ) already being present in the monomial. Because none of the monomials in  $T_{\frac{n-2}{2}}$  contain  $x_n$ , the first case creates n-1unique monomials of degree n-1, all of which feature the variable  $x_n$ . It remains to show that the other two cases only add the one missing monomial where  $x_n$  is not present. For each monomial in  $T_{\frac{n-2}{2}}$  of degree n-2, there are n-2 variables  $x_i$  that, upon multiplication, leave the monomial invariant (case (3) above). Because the same degree-(n-2) monomial is generated an even number of times, it will not be present in the ANF of the multiplication result. The only remaining variable to be multiplied by for each monomial from  $T_{\frac{n-2}{2}}$  is then the variable that fills the gap in the monomial, which results in the missing monomial  $x_1 \cdots x_{n-1}$ . Since this monomial is produced an odd number of times (once for each monomial in  $T_{\frac{n-2}{2}}$ ), the monomial  $x_1 \cdots x_{n-1}$  will be present in the ANF of the multiplication result. Therefore, the ANF of the multiplication result consists of n monomials of degree n-1, as claimed.

By combining Lemma 2 with Lemma 3, we have shown how to compute  $s_0^n$  for any  $n \geq 3$  using n-2 AND gates.

### 3.2 Stage 2

In the second stage of our construction, we generate n-1 additional linearly independent intermediate results that can be used to extract all n monomials using XORs in the third stage. Specifically, for odd n, we compute

$$s_i^n := (x_i \oplus x_{i+1}) \wedge s_0^n$$

for all  $i \in \{1, ..., n-1\}$ . For even n, we compute the same  $s_i^n$  for  $i \in \{1, ..., n-2\}$  and we additionally compute the last output of f(x) directly via

$$f_n(x) = T_{\frac{n-2}{2}} \wedge \bigoplus_{i=1}^{n-1} x_i.$$
(3)

We claim that the ANF of  $s_i^n$  contains exactly those two monomials of degree n-1 where either  $x_i$  or  $x_{i+1}$  is missing. We prove this next, before proving the equality in (3).

**Lemma 4.** Let n be the number of inputs. Then, for each  $i \in \{1, ..., n-1\}$ , the ANF of

$$s_i^n := (x_i \oplus x_{i+1}) \wedge s_0^n$$

consists of exactly two monomials of degree n-1; one where  $x_i$  is missing, and one where  $x_{i+1}$  is missing.

Proof. Each of the n monomials of degree n-1 in the ANF of  $s_0^n$  is multiplied by  $(x_i \oplus x_{i+1})$ . For each monomial where both  $x_i$  and  $x_{i+1}$  are present, a multiplication by either of these two variables results in the same monomial, and they thus cancel. Multiplying the two monomials where  $x_i$  or  $x_{i+1}$  is missing by  $(x_i \oplus x_{i+1})$  results in (1) the degree-n monomial  $x_1 \cdots x_n$ , and (2) the monomial itself (where  $x_i$  or  $x_{i+1}$  is missing) for each of the two monomials. The degree-n monomial is thus generated twice and, therefore, the only two monomials remaining in the ANF of the multiplication result are those two where  $x_i$  or  $x_{i+1}$  is missing.

Finally, we show that the equality in (3) holds for even n.

**Lemma 5.** Let the number of inputs n be even. Then the last output of f(x) may be computed from  $T_{\frac{n-2}{2}}$  using one additional AND gate via

$$f_n(x) = T_{\frac{n-2}{2}} \wedge \bigoplus_{i=1}^{n-1} x_i.$$

Proof. The n-1 monomials in the ANF of  $T_{\frac{n-2}{2}}$  are of even degree n-2 with variables from  $\{x_1,...,x_{n-1}\}$ . Therefore, for each monomial, n-2 out of the n-1 variables in  $\{x_1,...,x_{n-1}\}$  are already present in the monomial, and a multiplication by such an  $x_i$  results in the same monomial. As this happens an even number of times, all of these terms cancel. For each monomial, the only nontrivial contribution to the result comes from the  $x_i$  not present in the monomial, and the contribution is the same for each monomial, namely  $x_1 \cdots x_{n-1}$ . Because this contribution is added to the result an odd number of times (once for each monomial in  $T_{\frac{n-2}{2}}$ ), the only monomial that is left in the ANF of the multiplication result is  $x_1 \cdots x_{n-1}$ , which is equal to  $f_n(x)$ , as claimed.

#### 3.3 Stage 3

After completing stages 1 and 2, we have n linearly independent intermediate results, each containing either 1 (if n is even), 2, or n monomials of degree n-1. In this final stage, we combine these n intermediate results using XORs in order to compute the outputs of f(x). This allows us to prove our main result.

**Theorem 1.** The multiplicative complexity of the vector-valued Boolean function f with n Boolean inputs  $x_1, ..., x_n$ , where the i-th output is given by

$$f_i(x_1, ..., x_n) = \bigwedge_{j \neq i} x_j,$$

for  $i \in \{1, ..., n\}$  is  $c_{\wedge}(f) = 2n - 3$ .

*Proof.* Since Boyar and Find have shown that  $c_{\wedge}(f) \geq 2n-3$  [8], it remains to show that  $c_{\wedge}(f) \leq 2n-3$  by completing our construction, which establishes that  $c_{\wedge}(f) = 2n-3$ .

We first consider the case where n is odd. From Lemma 2 it follows that  $s_0^n$  can be computed using n-2 AND gates. From Lemma 4 we know that each  $s_k^n$  for  $k \in \{1, ..., n-1\}$  can be computed from  $s_0^n$  using a single AND gate. We may compute the first output  $f_1(x)$  via

$$f_1(x) = s_0^n \oplus \bigoplus_{i=1}^{\frac{n-1}{2}} s_{2i}^n.$$

To see that this is correct, note that  $\bigoplus_{i=1}^{\frac{n-1}{2}} s_{2i}^n$  contains all degree-(n-1) monomials except  $f_1(x) = x_2 \cdots x_n$ , whereas  $s_0^n$  contains all degree-(n-1) monomials. This first output  $f_1(x)$  may now be used to obtain  $f_2(x)$  via  $f_1(x) \oplus s_1^n$ . In turn,  $f_3(x) = f_2(x) \oplus s_2^n$ , and so on, until the final output  $f_n(x) = f_{n-1}(x) \oplus s_{n-1}^n$  has been computed. The total number of AND gates in this case is (n-2) + (n-1) = 2n-3.

For even n, Lemma 2 shows that  $T_{\frac{n-2}{2}}=s_0^{n-1}$  can be computed using  $\frac{n-2}{2}+(\frac{n-2}{2}-1)=n-3$  AND gates. From Lemma 3,  $s_0^n$  can be computed from  $s_0^{n-1}$  using a single AND gate, and Lemma 5 shows that a single AND gate is sufficient to compute  $f_n(x)$  from  $T_{\frac{n-2}{2}}$ . In addition, we compute  $s_k^n$  for  $k \in \{1,...,n-2\}$  using n-2 AND gates. The total AND gate count is thus (n-3)+1+1+(n-2)=2n-3, and we can extract the first output as follows:

$$f_1(x) = s_0^n \oplus f_n(x) \oplus \bigoplus_{i=1}^{\frac{n-2}{2}} s_{2i}^n.$$

To see that this is correct, note that  $\bigoplus_{i=1}^{\frac{n-2}{2}} s_{2i}^n$  contains all degree-(n-1) monomials except  $f_1(x) = x_2 \cdots x_n$  and  $f_n(x) = x_1 \cdots x_{n-1}$ , whereas  $s_0^n$  contains all degree-(n-1) monomials. To compute the remaining outputs  $f_i(x)$  for  $i \in \{2, ..., n-1\}$ , we may again use that  $f_i(x) = f_{i-1}(x) \oplus s_{i-1}^n$ .

# References

- [1] Giulia Meuli, Mathias Soeken, Earl Campbell, Martin Roetteler, and Giovanni De Micheli. The role of multiplicative complexity in compiling low t-count oracle circuits. In 2019 IEEE/ACM International Conference on Computer-Aided Design (ICCAD), pages 1–8. IEEE, 2019.
- [2] Martin R Albrecht, Christian Rechberger, Thomas Schneider, Tyge Tiessen, and Michael Zohner. Ciphers for mpc and fhe. In Annual International Conference on the Theory and Applications of Cryptographic Techniques, pages 430–454. Springer, 2015.

- [3] Magnus Gausdal Find. On the complexity of computing two nonlinearity measures. In Computer Science-Theory and Applications: 9th International Computer Science Symposium in Russia, CSR 2014, Moscow, Russia, June 7-11, 2014. Proceedings 9, pages 167–175. Springer, 2014.
- [4] Çağdaş Çalık, Meltem Sönmez Turan, and René Peralta. The multiplicative complexity of 6-variable boolean functions. *Cryptography and Communications*, 11(1):93–107, 2019.
- [5] Meltem Turan Sönmez and René Peralta. The multiplicative complexity of boolean functions on four and five variables. In *International Workshop on Lightweight Cryptography for Security and Privacy*, pages 21–33. Springer, 2014.
- [6] Çağdaş Çalık, Meltem Sönmez Turan, and René Peralta. Boolean functions with multiplicative complexity 3 and 4. *Cryptography and Communications*, 12(5):935–946, 2020.
- [7] Thomas Häner and Mathias Soeken. The multiplicative complexity of interval checking. arXiv preprint arXiv:2201.10200, 2022.
- [8] Joan Boyar and Magnus Gausdal Find. Multiplicative complexity of vector valued boolean functions. *Theoretical Computer Science*, 720:36–46, 2018.
- [9] Claus-Peter Schnorr. The multiplicative complexity of boolean functions. In *International Conference on Applied Algebra, Algebraic Algorithms, and Error-Correcting Codes*, pages 45–58. Springer, 1988.