

ULG_{SS}: A Strategy to construct a Library of Universal Logic Gates for N -variable Boolean Logic beyond NAND and NOR

Aadarsh G. Goenka^{ID}, Shyamali Mitra^{ID}, Mrinal K. Naskar, Nibaran Das, *Senior Member, IEEE*^{ID}

Abstract—In literature, NAND and NOR are two logic gates that display functional completeness, hence regarded as Universal gates. So, the present effort is focused on exploring a library of universal gates in binary that are still unexplored in literature along with a broad and systematic approach to classify the logic connectives. The study shows that the number of Universal Gates in any logic system grows exponentially with the number of input variables N . It is revealed that there are 56 Universal gates in binary for $N = 3$. It is shown that the ratio of the count of Universal gates to the total number of Logic gates is $\approx \frac{1}{4}$ or 0.25. Adding constants 0, 1 allow for the creation of 4 additional (for $N = 2$) and 169 additional Universal Gates (for $N = 3$). In this article, the mathematical and logical underpinnings of the concept of universal logic gates are presented, along with a search strategy *ULG_{SS}* exploring multiple paths leading to their identification. A fast-track approach has been introduced that uses the hexadecimal representation of a logic gate to quickly ascertain its attribute.

Index Terms—Functional Completeness; Universal Gates; N -Variable Logic; Hexadecimal encoding; MUX equivalent circuits;

I. INTRODUCTION

Logic gates [1]–[8] are the fundamental building blocks of any digital system [10]–[12]. An algebraic formula can be used to describe the operation of each gate, where each gate has its own unique graphic symbol. In Binary, computation is carried out by a lot of complex functions and logic gates [14]. Logic gates are categorized into three different types depending on their properties; Basic gates, Universal Gates and Non-Universal Gates. Basic gates (AND, OR and NOT gates) are those that can form any logic function by combining some or all of these gates to make a functionally complete set [13]. Universal Gate(s) can construct any logic function without utilizing any other logic gate in the process; as a result, they may form a *Functionally Complete Set* [15] themselves. Non-Universal gates, on the other hand, cannot construct all logic functions and must utilize other logic gates in the process.

At present, there are two known Universal logic gates in binary: NAND and NOR gates, which indicate that it is possible to create any Boolean expression using only NOR or NAND gates. There are no more Universal Gates documented in literature. Aside from the fact that a Universal

Gate should be able to produce AND, OR, and NOT gates, it is unknown how to determine whether a gate is Universal or not. This research unfolds several characteristics that may help to deduce the class of a logic connective using a broad and systematic approach. This leads to the identification of a library of universal gates in the Binary Logic System. In order to illustrate the universality possessed by an N -variable logic, a number of deductions are introduced. In addition to this, a discussion on how the logic of a Non-Universal logic changes when a full set consisting of logic constants 0 and 1 is included. A systematic approach in determining the nature of a given logic gate is introduced using some observations that explain the universality of a given logic. A mathematical expression to determine the number of universal logic gates is also presented to reveal that R_N , which is the ratio of universal logic gate count to all possible logic gates in the N -variable logic, increases linearly for $N = 3$, and saturates to $\frac{1}{4}$ of the total number of gates for higher values of N . Further, the applicability of the logic gates has been shown in applications like quantum dot cellular automata (QCA) to design full adder circuits to reduce the overall hardware cost to a great extent. The contribution in the proposed work can be summarized as:

- Creating a library of universal logic gates in binary and showing their applicability in certain applications.
- Revisiting the conditions of universality of logic gates as well as establishing some new criteria for better analysis of the class of a logic with the proposed algorithms.
- Deriving an expression to determine the number of universal gates in Boolean Logic with N -variables.
- Behaviour of Multiplexer equivalent circuits consisting of a set $\{0, 1, G\}$, where G is a logic gate in Binary.
- A fast-track methodology for determining the property of the logic gate based on its hexadecimal encoding.

II. UNIVERSAL GATES IN BINARY

A functionally complete set of logic connectives or Boolean operators is one that, when members of the set are combined to form a Boolean expression they can express every possible Boolean logic. Every possible logic function can be realised as a network of gates specified in the set, which is referred to as functionally complete [9]. Logic Gates which are part of Functionally Complete set of cardinality 1 are considered Universal. NAND and NOR are the examples of two singleton sets. In essence, all logic functions can be built using binary NOR or NAND gates alone. If we cascade an AND gate and

A. G. Goenka (e-mail: aggtur11@gmail.com) and N. Das (e-mail: nibaran@ieee.org) are with the Dept. of CSE, Jadavpur University, India

S. Mitra is with the Dept. of IEE, Jadavpur University, India (e-mail: shyamalimitra.tee@jadavpuruniversity.in)

M. K. Naskar is with the Dept. of ETCE, Jadavpur University, India (e-mail: mrinaletce@gmail.in)

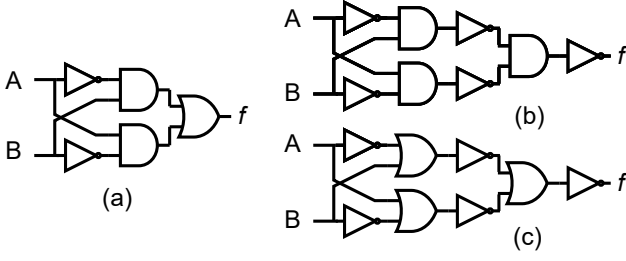


Fig. 1. Implementation of an expression $f = A\bar{B} + \bar{A}B$ using (a) AND-OR-NOT logic (b) AND-NOT logic (c) OR-NOT logic

a NOT gate, we have a NAND gate, which is a complete set of logic similar to AND and NOT. To make a NOR gate, we would cascade an OR gate and a NOT gate. However, {AND, OR} alone do not create a complete set. If NOT gate is included in the set, the set behaves a complete set. The combination of these Gates allows us to derive a wide variety of different Boolean operations and gates. However, the NAND and NOR gates are considered minimal sets due to their completeness; they can be used alone or in combination to build a wide variety of different logic circuits. The inference regarding a logic gate being universal can be drawn using the following properties:

Property 1: A logic connective or a set of logic connectives is said to be functionally complete, if all possible logic functions are equivalent to Boolean Expressions involving only that gate or gates in the set.

A set of Boolean functions is functionally complete if it is possible to generate all logic expressions using the set. A set is functionally complete if it can be derived from another set that is also functionally complete, e.g., {AND, OR, NOT}, {AND, NOT}, {OR, NOT}. As an example, it is possible to construct all Boolean functions using a combination of AND, OR and NOT gates. An example is shown in Fig. 1 (a),(b),(c) where a function $f = A\bar{B} + \bar{A}B$ is implemented using three complete sets each consisting of all elements from the set. Thus, all elements from a complete set must be considered to realize a function. However, if {AND,OR} is considered a set, only a subset of the functions can be realized, hence the set becomes functionally incomplete.

Property 2: A Universal gate of N -inputs can create all logic functions without using any other gate in the process.

Consider a Boolean expression $f = A\bar{B} + \bar{A}B$. This can be formed using NAND gates explicitly without involving any other gate in the process. The modified expression $f = A(\overline{AB}) \cdot B(\overline{AB})$ allows us to implement the logic function using only NAND gates. In applications, this is beneficial because NAND and NOR gates are less expensive and simpler to fabricate. Furthermore, these gates are fundamental building blocks of all IC logic families.

Property 3: A logic is considered to be Non-Universal if it cannot produce a functionally complete set with cardinality 1.

Let us consider three sets with cardinality 1; {AND}, {OR}, {NOT} which are functionally incomplete sets. From Table I, it is observed that, AND, OR, NOT gates can respectively implement only 3, 3 and 4 logic functions without using

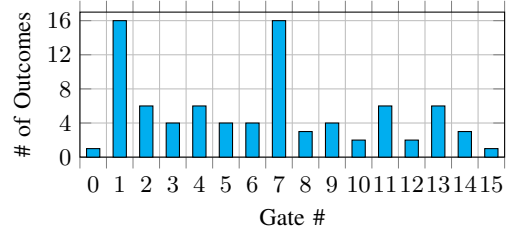


Fig. 2. Visualization of possible gates implemented for $N = 2$

logic constants 0, 1. Including the logic constants increase the number of implemented functions to 5, 5, and 6 respectively. Hence, they cannot be considered as Universal gates.

A. Universal logic gates in Binary for $N=2$

Logic gates, can be of one input (A) or two input variables (A and B) and a single binary output variable (say, Y). In Binary, there are $2^4 = 16$ possible Logic constructs. These range from 0000 to 1111 when 11, 10, 01, and 00 are given as inputs respectively to the two input lines of the gates. Thus, they can be numbered from 0 to 15 in decimal or 0 to F in hexadecimal. Table I shows each such logic and the number of functions implemented by each logic. It is observed that only NOR (#1) and NAND (#7), are capable of implementing all 16 logic functions and are thus regarded as Universal gates.

TABLE I. # of functions realized by a gate with and without logic constants 0,1 for $N = 2$. Numbers in bold correspond to implementations of all logic combinations and hence considered Universal.

Gate #	Logic function	# of logic Implemented	
		Without logic constants	With logic constants
0	$F(A,B)=0$	1	1
1	$A + B$	16	16
2	$\bar{A}\bar{B}$	6	16
3	\bar{A}	4	6
4	$\bar{A}\bar{B}$	6	16
5	\bar{B}	4	6
6	$A \text{ xor } B$	4	8
7	$\bar{A}B$	16	16
8	AB	3	5
9	$A \text{ xnor } B$	4	8
A/10	B	2	4
B/11	$\bar{A} + B$	6	16
C/12	A	2	4
D/13	$A + \bar{B}$	6	16
E/14	$A+B$	3	5
F/15	$F(A,B)=1$	1	1

B. Universal logic in Binary for $N=3$

In case of $N = 3$, each gate has eight possible outcomes corresponding to 2^3 input combinations ranging from 000 to 111. Thus, there are $2^{23} = 256$ logic outcomes ranging from 00000000 to 11111111. The 256 gates are numbered from 0 to 255 in decimal or 00 to FF in hexadecimal. Table V shows the logic gates coded in hexadecimal from 00 to FF with the corresponding number of logic gates implemented by each. The gates that can implement all 256 logic functions are Universal gates. It is found empirically that there are 56 universal gates for $N = 3$ fulfilling the criteria for the universal logic. A list of universal gates with the hexadecimal encoding are shown in Table II. Thus, dealing with higher number of variables increases the gate count proportionately.

C. Observations and Analysis for Universal Gates

In this section, we compile all observation notes, organize them, and analyze the data from the experimental outcomes.

Observation 1: *The Universal Gates are all located in the first half of the total gate count and are all odd-indexed.*

It may be deduced from Fig. 3b) that all the Universal Gates always lie in the first half of the total gate count when arranged in ascending order of their hexadecimal encoding i.e., output will be 0 when all inputs are 1, and that they will always be odd numbered, regardless of the number of inputs that a binary gate can accept (i.e., output will be 1 when all inputs are 0). If a gate fails to meet any one of these two conditions, it is said to be Non-Universal. A gate that satisfies both of these criteria can be either Universal or non-Universal depending on fulfillment of further criteria explained below.

TABLE II. List of 56 Universal Gates with their H-E for $N = 3$

01	03	05	07	09	0B	0D	11
13	15	19	1B	1D	1F	21	23
25	27	29	2D	2F	31	35	37
39	3B	3D	3F	41	43	45	47
49	4B	4F	51	53	57	59	5B
5D	5F	61	63	65	67	6B	6D
6F	73	75	77	79	7B	7D	7F

Observation 2: *It is implicit that for $N = 2$, out of 16 Logic Gates, 4 satisfy both the criteria stated in Observation1 and out of 4 gates, 2 are Universal. Similarly, for $N = 3$, out of 256 gates, 64 satisfy both criteria, and only 56 are Universal.*

TABLE III. Truth Table of Non-Universal gates with $N = 3$

A	B	C	#0F	#17	#2B	#33	#4D	#55	#69	#71
0	0	0	1	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	0	0	0
0	1	0	1	1	0	0	1	1	0	0
0	1	1	1	0	1	0	1	0	1	0
1	0	0	0	1	0	1	0	1	0	1
1	0	1	0	0	1	1	0	0	1	1
1	1	0	0	0	0	0	1	1	1	1
1	1	1	0	0	0	0	0	0	0	0

TABLE IV. Truth Tables of gate 3 and 5

A	B	#3	#5
0	0	1	1
0	1	1	0
1	0	0	1
1	1	0	0

Four gates located in the odd-numbered positions of hexadecimal encoding are 1, 3, 5, and 7. But Gate 3 and Gate 5 are non-universal. The reason can be explained with the help of truth tables shown in Table IV. Thus, gates 1 and 3 satisfy both the criteria stated in Observation1. Similarly, Gates F, 17, 2B, 33, 4D, 55, 69 and 71 in $N = 3$ satisfy both the criteria and are still Non-Universal. The truth tables of these non-universal gates are given in Table III. It can be observed that they all have equal number of 1s and 0s in their output. In addition, the first and second halves of the output of the gates have inversely mirrored arrangements of 0s and 1s. Therefore, each of them must satisfy,

$$\overline{F(A, B)} = F(\overline{A}, \overline{B}) \quad (1)$$

$$\overline{F(A, B, C)} = F(\overline{A}, \overline{B}, \overline{C}) \quad (2)$$

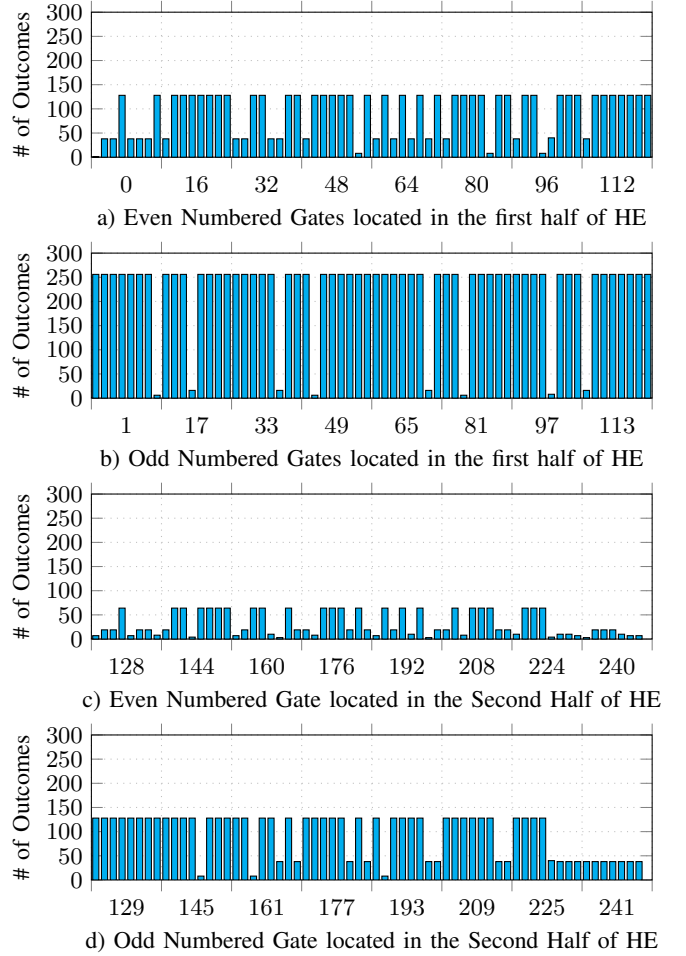


Fig. 3. Visualization of the entire logic in a 2 – D plane for $N = 3$. The height of the bar graph denotes the number of different logic functions implemented by a given logic. Fig. 3b) shows that all universal logic gates (implementing all 256 logic connectives) are entirely clustered in the first half of the hexadecimal encoding (HE) and that they are all odd numbered.

D. Data Interpretation using the logic analysis of Gates

To be expressively complete, any set of n -valued truth functional connectives must satisfy all of the conditions outlined in section II. This posits that a set of connectives is expressively complete if none of the highlighted properties that an arbitrary connective may possess are satisfied. It is stated in terms of the three conditions listed below.

Condition 1: *A logic gate G which is in the class of zero-preserving boolean functions T_0 (i.e., $f \in T_0$ if it satisfies $f(0,0,...,0)=0$) is always Non-Universal.*

Proof: To express that the proposition is true, let us consider a logic gate G which can be expressed as, $f(0,0,0,...,0) = 0$. In other way, for the gate to create $f_1(0,0,0,...,0) = 1$ at least one of the inputs must be 1. This requires an extra NOT Gate in conjunction with it or any gate that manifest itself in the form of f_1 (i.e., it produces a 1 when all the inputs are 0). Thus, an additional gate is needed to create f_1 . Therefore, f_1 cannot be produced with G alone; hence f is non-universal.

Condition 2: *A logic gate G which is in the class of one-preserving boolean functions T_1 (i.e., $f \in T_1$ if it satisfies*

$f(1,1,...,1)=1$) is always Non-Universal.

Proof: To express that the proposition is true, let us consider a logic gate G where, $f(1, 1, 1...1) = 1$. Therefore, for the gate to create $f(1, 1, 1...1) = 0$, at least one of the inputs must be 0. This requires a NOT Gate or any gate that is itself in the form of $f1$ (i.e. it gives 0 when all the inputs are 1). Thus, an additional gate is needed to create $f1$. Therefore, $f1$ cannot be produced with Gate f alone; hence f is Non-Universal.

Consider the gate $F8$ in a 3 variable Boolean logic given by, $f = (A + BC)$, which does not satisfy any of the conditions of universality i.e., $f(0,0,0) = 1$ (non-zero preserving) and $f(1,1,1) = 0$ (non-one preserving). $F8$ is capable of producing the following Logic Gates: $AA, CC, EA, EC, EE, F0, F8, FA, FC$, and FE . These gates meet the criteria of a 0-preserving function, $f(0,0,0) = 0$, and a 1-preserving function, $f(1,1,1) = 1$.

Condition 3: A logic gate F belonging to a class of self-dual Boolean functions S , $f \in S$ and satisfies $f(A, B, C...) = f(\bar{A}, \bar{B}, \bar{C}...)$ is always Non-Universal.

Consider Gate $2B$ with $f=(\bar{A}+\bar{B}+\bar{A}C+\bar{B}C)$, which satisfies the equation $\bar{F}(A,B,C) = F(\bar{A},\bar{B},\bar{C})$. The truth table is given in Table III which shows the function is self-dual, hence considered as non-universal. The possible Logic Gates that can be created by it are $0F, 17, 33, 4D, 55, 69, 71, 8E, 96, AA, B2, CC, D4, E8$ and $F0$. All of the gates satisfy the equation $\bar{F}(A,B,C) = F(\bar{A},\bar{B},\bar{C})$. Since these are all generated using a non-universal logic, the implemented gates become non-universal by virtue.

Condition 4: Functions that neither preserve 0 nor 1 nor do they belong to the class of self-dual functions are said to be Universal.

The proposed set of connectives is functionally complete as neither of the conditions $f(0,0,0...0) = 0$, nor $f(1,1,1...1) = 1$, nor $f(A,B,C...) = f(\bar{A},\bar{B},\bar{C}...)$ are satisfied. A logic which is functionally complete does not satisfy the condition for self-duality such that, there occurs a row in the truth table $\{y_1, y_2..., y_n\}$ so, $f(y_1, y_2, ..., y_n) = f(-y_1, -y_2..., -y_n)$.

E. A systematic approach for classifying Boolean Logic

In this section, a systematic method for determining the class of a logic connective is presented. In order for the proposed set of connectives to be functionally complete, each of the theorems listed below must be satisfied by a connective in the set. We begin by outlining these properties.

Theorem 1: A Logic Gate which is a part of a Functionally Complete Set of cardinality 1 is a Universal Gate.

Proof: If a set consists of only one unique element, say, $\{NAND\}$ and $\{NOR\}$, then this is regarded as functionally complete set with cardinality 1. The interpretation of which is, that the constituent element can form any logic without requiring any other gate in the process.

Theorem 2: A logic gate of N -inputs that can create any other Universal Gate is also a Universal Gate.

Proof: Take into consideration a gate G that has the ability to produce another gate $G1$. If this is the case, the set of

gates that is produced by G will incorporate the logic that is produced by $G1$. If $G1$ is a Universal Gate, then the set of logic connectives that it generates will include 2^{2^N} possible gates without the need for any additional gates to be used at any point in the process. As $G1$ is contained within G , it is deducible that G is a Universal logic. Thus, it is possible to create all logic functions by utilising G on its own. Take, for illustration, a gate that generates a NOR gate, which is a universal logic. NAND gate can solely generate a NOR logic and hence considered to be universal.

Corollary 1: A Non-Universal Gate can generate only Non-Universal logic for all possible inputs.

The correctness of this statement can be stated using **Theorem 2**, that recognise a general transformation of the proposition. For the 3-Input Non Universal Gate $2B$, the possible logic gates that it can implement are: $0F, 17, 2B, 33, 4D, 55, 69, 71, 8E, 96, AA, B2, CC, D4, E8$ and $F0$. These instances may serve to infer that all of these gates are Non-Universal as they are expressed by a non-universal logic that always excludes a universal set. The algorithm for finding a universal logic is shown in **Algorithm 1**.

Algorithm 1 Search for Universal Logic Gate

```

1: Input:  $TT$  //Truth Table of a given logic with  $N$  inputs.
   Output: Universal Gate, Non-Universal Gate.
2: Variable Initialization:
    $N$  = Number of Inputs
    $M = 2^N$  //No. of input logic combinations.
   Initialize  $TT[]$  with the Values from Truth Table of a function
    $i \leftarrow 1$ 
3: if ( $TT[0] = 1$  &&  $TT[M-1] = 0$ ) then
4:   while  $i \leq \frac{M}{2}$  do
5:     if  $TT[i] = TT[M-i-1]$  then
6:       return Universal Gate
7:     else
8:        $i \leftarrow i + 1$ 
9:     end if
10:  end while
11: end if
12: return Non-Universal Gate

```


F. Universal Gate count for N -variables

Let, the total number of input combinations for a given logic with N number of input variables is I_N , given by $I_N = 2^N$. So, the total number of possible logic functions in an N input binary system is $G_N = 2^{I_N}$. The total number of input combinations for a particular gate which are unrestricted by **Condition 1** and **Condition 2** is given by $2^N - 2$. The number of logic gates that are neither 0-preserving nor 1-preserving can be given by $G_S = 2^{2^N - 2} = \frac{2^{I_N}}{2^2} = \frac{G_N}{4}$. The total number of input combinations for a particular gate that are unrestricted by all **Condition 1**, **Condition 2** and **Condition 3** = $\frac{(2^N - 2)}{2}$. The total number of logic connectives that satisfy the condition of self-duality but are neither 0 nor 1 preserving is given by, $2^{\frac{(2^N - 2)}{2}} = \sqrt{\frac{2^{I_N}}{2^2}} = \sqrt{\frac{G_N}{4}}$. Therefore, the total number of universal gates U_N for an N input system can be stated as,

$$U_N = \frac{G_N}{4} - \sqrt{\frac{G_N}{4}} \quad (3)$$

TABLE V. Showing the number of functions realized by each 256 gates for $N = 3$. Cells in yellow shows the realization of all functions in the set.

Gate #	Output	Gate #	Output	Gate #	Output	Gate #	Output	Gate #	Output	Gate #	Output	Gate #	Output	Gate #	Output
00	1	01	256	02	38	03	256	04	38	05	256	06	128	07	256
08	38	09	256	0A	38	0B	256	0C	38	0D	256	0E	128	0F	6
10	38	11	256	12	128	13	256	14	128	15	256	16	128	17	16
18	128	19	256	1A	128	1B	256	1C	128	1D	256	1E	128	1F	256
20	38	21	256	22	38	23	256	24	128	25	256	26	128	27	256
28	38	29	256	2A	38	2B	16	2C	128	2D	256	2E	128	2F	256
30	38	31	256	32	128	33	6	34	128	35	256	36	128	37	256
38	128	39	256	3A	128	3B	256	3C	8	3D	256	3E	128	3F	256
40	38	41	256	42	128	43	256	44	38	45	256	46	128	47	256
48	38	49	256	4A	128	4B	256	4C	38	4D	16	4E	128	4F	256
50	38	51	256	52	128	53	256	54	128	55	6	56	128	57	256
58	128	59	256	5A	8	5B	256	5C	128	5D	256	5E	128	5F	256
60	38	61	256	62	128	63	256	64	128	65	256	66	8	67	256
68	40	69	8	6A	128	6B	256	6C	128	6D	256	6E	128	6F	256
70	38	71	16	72	128	73	256	74	128	75	256	76	128	77	256
78	128	79	256	7A	128	7B	256	7C	128	7D	256	7E	128	7F	256
80	7	81	128	82	19	83	128	84	19	85	128	86	64	87	128
88	7	89	128	8A	19	8B	128	8C	19	8D	128	8E	8	8F	128
90	19	91	128	92	64	93	128	94	64	95	128	96	4	97	128
98	64	99	8	9A	64	9B	128	9C	64	9D	128	9E	64	9F	128
A0	7	A1	128	A2	19	A3	128	A4	64	A5	8	A6	64	A7	128
A8	10	A9	128	AA	3	AB	38	AC	64	AD	128	AE	19	AF	38
B0	19	B1	128	B2	8	B3	128	B4	64	B5	128	B6	64	B7	128
B8	64	B9	128	BA	19	BB	38	BC	64	BD	128	BE	19	BF	38
C0	7	C1	128	C2	64	C3	8	C4	19	C5	128	C6	64	C7	128
C8	10	C9	128	CA	64	CB	128	CC	3	CD	38	CE	19	CF	38
D0	19	D1	128	D2	64	D3	128	D4	8	D5	128	D6	64	D7	128
D8	64	D9	128	DA	64	DB	128	DC	19	DD	38	DE	19	DF	38
E0	10	E1	128	E2	64	E3	128	E4	64	E5	128	E6	64	E7	128
E8	4	E9	40	EA	10	EB	38	EC	10	ED	38	EE	7	EF	38
F0	3	F1	38	F2	19	F3	38	F4	19	F5	38	F6	19	F7	38
F8	10	F9	38	FA	7	FB	38	FC	7	FD	38	FE	7	FF	1

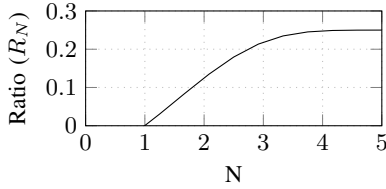Fig. 4. Ratio R_N for different values of N

The ratio (R_N) of Universal Gate count (U_N) to the total gate count (G_N) in an N -variable logic system is given by,

$$R_N = \frac{U_N}{G_N} = \frac{1}{4} - \frac{1}{\sqrt{4G_N}} \quad (4)$$

Thus, from Eq. 3 the Universal Gate count for $N = 3$ is,

$$I_3 = 2^3 = 8, G_3 = 2^{I_3} = 256, U_3 = \frac{256}{4} - \sqrt{\frac{256}{4}} = \mathbf{56}.$$

Similarly, the Universal gate count when $N = 4$ is, $I_4 = 2^4 = 16, G_4 = 2^{I_4} = 65536, U_4 = \frac{65536}{4} - \sqrt{\frac{65536}{4}} = \mathbf{16256}.$

It is observed from Fig. 4 that the ratio R_N saturates to 0.25, as the influence of the second term can be neglected for higher values of N , i.e., from $N > 3$.

III. UNIVERSAL LOGIC GATES IN BINARY INCLUDING LOGIC CONSTANTS 0,1

In this section, the logic constants 0,1 have been incorporated to form a larger set of universal logic gates. A logic gate G which is a part of *Functionally Complete set* in the form $\{G, 0, 1\}$ is considered to be Universal, where, 1 is the logic gate when $F(a_1, a_2, \dots, a_n) = 1$ and 0 is the logic gate which satisfies $F(a_1, a_2, \dots, a_n) = 0$.

A. Universal logic ($N=2$) including the logic constants 0, 1

Table I depicts the number of logic that each gate can implement including logic constants 0 and 1. Gates that are able to implement all 16 outcomes are considered universal.

Inputs of each gate are comprised of the gates that are self-generated, as well as $A, B, All0(0)$ and $All1(F)$. As an example, $NAND(7), NOR(1), A \text{ Imply } B (B), B \text{ Imply } A (D), A \text{ Nimply } B (4),$ and $B \text{ Nimply } A (2)$ gates make up the coalescence of universal gates. This becomes implicit that by adding 0 and F gates as inputs to a gate increased both the number of possible outcomes and the universal gate count by 4. Fig. 5 shows that the number of logic functions created by a gate increases (red colored bars) when 0 and 1 constants are included in the set.

B. Universal logic ($N = 3$) including the logic constants 0, 1

Table VI shows the number of logic implemented by 31 Non-Universal gates including the logic constants 0,1. It is observed that a Non-Universal gate can create a maximum of 20 logic functions out of 256 possible gates. Including the logic constants in the set converted majority of the gates to the universal logic. The additional Non-Universal gates that became part of the Universal count after being a part of Set $\{0, 1, G\}$ are shown in Table VII. For a 3 variable case, out of 256 possible logic outcomes, 225 are found Universal. Consequently, the ratio of Universal Gates to Non-Universal Gates increases dramatically as the number of inputs increase.

IV. DECODING THE CLASS OF A LOGIC USING ITS MULTIPLEXER EQUIVALENT CIRCUITS

In this section, we will examine the multiplexer equivalent circuits of logic gates, which can be further used in determining the class of a logic. Consider a three-variable logic function in which one of the inputs can be assigned either 0 or 1. This can be done by connecting the variable to either $All0$ gate or an $AllF$ gate to switch between the first four and last four gates of the function. Due to the inclusion of 0 and 1 in the entire set, it can therefore function as a combination of two 2-input gates, which can be selected by switching one of the variables. Now, let us consider a 3-variable function with inputs

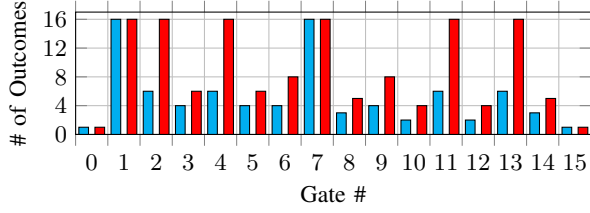


Fig. 5. Increase in the number of logic realized by a gate (shown in red color) for $N = 2$, when logic constants 0, 1 are included in the set.

A , B and C to be implemented using a 2 : 1 Multiplexer with A as the select line. The input value A can be utilised to switch between two distinct functions. It is observed that if any of the gates in the combination is universal that are used as inputs in the multiplexer equivalent circuit is a Universal gate, then the 3-input gate also becomes a Universal gate (*Theorem 2*). This is also true, if two gates in the multiplexer equivalent circuit forms a functionally complete set. They can be combined to create a function that can implement any function, resulting in a Universal logic (using *Property 1*). Logic gates with N -inputs can be constructed using higher order multiplexers involving only 2-input gates, the output of which are connected to input lines of the MUX. Thus, there are $(N - 2)$ select lines in MUX which on receiving an input combination activates a specific minterm at the output.

A. A Fast-Track approach for logic analysis using the Hexadecimal encoding of the gate

A method has been described in this section whereby the hexadecimal representation of a logic gate can be used to infer its property without carrying out rigorous analysis on the logic of universality. Thus, it is possible to deduce, based on the Multiplexer equivalent circuit that all binary gates that consist of any of the six 2-input Universal gates as input of the multiplexer equivalent circuit are Universal. This can also be validated by inspecting the hexadecimal encoding of gates. It is observed that for $N = 2$ there are 6 Universal Gates with hexadecimal values 1, 2, 4, 7, B , and D .

TABLE VI. Non-Universal gates for $N = 3$ with the corresponding number of logic functions that they can implement

Gate#	Out	Gate#	Out	Gate#	Out	Gate#	Out
00	1	0F	8	33	8	3C	16
55	8	5A	16	66	16	69	16
80	9	88	9	96	16	99	16
A0	9	A5	16	A8	20	AA	5
C0	9	C3	16	C8	20	CC	5
E0	20	E8	20	EA	20	EC	20
EE	9	F0	5	F8	20	FA	9
FC	9	FE	9	FF	1		

TABLE VII. List of extra Universal Gates including logic constants 0, 1

02	04	06	08	0A	0C	0E	10	12	14	16	17	18
1A	1C	1E	20	22	24	26	28	2A	2B	2C	2E	30
32	34	36	38	3A	3E	40	42	44	46	48	4A	4C
4D	4E	50	52	54	56	58	5C	5E	60	62	64	68
6A	6C	6E	70	71	72	74	76	78	7A	7C	7E	81
82	83	84	85	86	87	89	8A	8B	8C	8D	8E	8F
90	91	92	93	94	95	97	98	9A	9B	9C	9D	9E
9F	A1	A2	A3	A4	A6	A7	A9	AB	AC	AD	AE	AF
B0	B1	B2	B3	B4	B5	B6	B7	B8	B9	BA	BB	BC
BD	BE	BF	C1	C2	C4	C5	C6	C7	C9	CA	CB	CD
CE	CF	D0	D1	D2	D3	D4	D5	D6	D7	D8	D9	DA
DB	DC	DD	DE	DF	E1	E2	E3	E4	E5	E6	E7	E9
EB	ED	EF	F1	F2	F3	F4	F5	F6	F7	F9	FB	FD

A logic gate in higher order variables ($N > 2$) whose hexadecimal encoding contains any of digits from the given set of 6 hexadecimal values becomes Universal. This is because the presence of any of these values in the final encoding implies that the multiplexer equivalent circuit uses the 2-input universal gate in the input line. Thus, a logic whose encoding contains any of the 6 digits; 1, 2, 4, 7, B and D are Universal. Therefore, from the hexadecimal encoding of the binary gates it can be ascertained that out of 256 possible three-input gates, $(6 \times 16) + (10 \times 6) = 156$ are Universal because all of them contain digits from the set $\{1, 2, 4, 7, B, D\}$.

It is implicit that none of the 31 Non-Universal Gates have any of the 6 hexadecimal digits included in their hexadecimal encoding, as represented in Table VI. The remaining 69 gates, however, are Universal despite the fact that they do not include any of the six gates from the set. This is because they contain digits that make up a set that is functionally complete. This enables the identification of a group of logic connectives that can be combined to form a functionally complete set.

From the Hexadecimal encoding of 4-input binary gates, we can also deduce that $(225 \times 256) + (31 \times 225) = 64575$ are Universal, as they contain the H-E of Universal Gates for $N = 3$. The remaining 961 gates can be investigated in a similar way in forming complete sets in order to locate additional Universal Gates. Without adding the complete set to construct Universal Gates, the ratio of Universal gates to total gate count becomes 37.5% for $N = 2$, 87.89% for $N = 3$, and 98.53% for $N = 4$. Consequently, the increase in N brings the count of Universal Gates closer to 100% when logic constants are included in the set. The class of a particular logic can be deduced using the predetermined set of conditions. Thus, a logic gate can be Universal on its own, Universal in a Complete Set that includes the constants 0 and 1, or entirely Non-Universal. The steps to classify a logic gate is illustrated using case studies IV-B, IV-C, IV-D.

B. 3-Input Gate 85

Consider a 3 input gate 85, which expressed using $F = \overline{A}\overline{C} + ABC$. The truth table given in Table VIII, suggests that the given function does not satisfy $F(1, 1, 1) = 0$, making it a Non-Universal Gate on its own. However, given the set $\{0, 85, FF\}$, the gate becomes Universal. The multiplexer equivalent circuit of gate 85 shown in Fig. 6 accepts two gates as inputs namely; NOT (Gate 5) and AND (Gate 8), that are employed in the 0 and 1 input lines of the MUX respectively. By giving inputs to A which is the select line of the MUX it is possible to switch between the two logic functions. Because additional gates included in the set i.e., gate 0 and FF as well as the fact that $\{AND, NOT\}$ forms a functionally complete set, the gate also behaves as a universal one.

C. 3-Input Gate 46

Consider a 3 input gate 46 which is given by, $F = \overline{A}.\overline{B}.C + B.C$. The truth table given in Table IX, suggests that the given function does not satisfy $F(0, 0, 0) = 1$, making it a Non-Universal Gate on its own. However, given the set $\{0, 46, FF\}$, the gate becomes Universal. This is due to the

fact that its Multiplexer equivalent consists of a Universal Gate i.e., Gate 4 (Nimply). This is possible because of the additional gates in the set i.e., gate 0 and FF . The multiplexer equivalent circuit of gate 46 in Fig. 7 accepts two gates namely; XOR (Gate 6) and Nimply (Gate 4), that are employed in the input lines 0 and 1 of the multiplexer, respectively. By switching select line between 1 and 0 it is possible to switch between these two different functions.

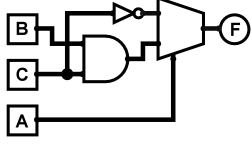


Fig. 6. Multiplexer equivalent circuit of Gate #85

TABLE VIII. Truth table of Gate #85

A	B	C	#85
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

D. 4-Input Gate 4685

In a 4 variable logic there are 65,536 possible logic functions. Let us consider a logic function with 4-input variables whose hexadecimal encoding is 4685 and can be expressed using the following switching function,

$$F = \bar{A}.\bar{B}.\bar{D} + \bar{A}.B.C.D + A.\bar{B}.\bar{C}.D + A.C.\bar{D}.$$

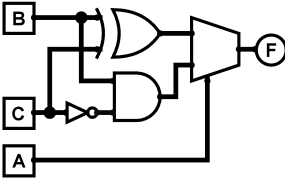


Fig. 7. Multiplexer equivalent circuit of Gate #46

TABLE IX. Truth table of Gate #46

A	B	C	#46
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

The truth table of gate 4685 is given in Table. X shows that the given logic does not exhibit the property of self-dual functions. It is also observed that the gate satisfies both the conditions of 0 and 1 non-preserving functions, i.e., $F(0,0,0,0) = 1$ and $F(1,1,1,1) = 0$. Therefore, this is a Universal gate on its own in compliance with the **Condition 4**. If we introduce the complete set {0000, 4685, FFFF}, it is observed that the gate consists of gates 4 (Nimply), 46 and 85, which are Non-Universal Gates by virtue but translated to universal logic when 0,1 are included in the set. Multiplexer equivalent circuits of the logic gate using a 4 : 1 MUX (considering A and B as the select lines) is shown in Fig. 8. When $A = 0, B = 0$, multiplexer implements NOT gate (gate 5), when $A = 0, B = 1$, multiplexer implements AND gate (gate 8), when $A = 1, B = 0$, multiplexer implements XOR gate (gate 6), when $A = 1, B = 1$, multiplexer implements Nimply gate (gate 4). The same function implemented using 2 : 1 MUX (considering A as the select line) is shown in Fig. 9. A similar foregoing approach can be grabbed to derive the 2 : 1 multiplexer equivalent circuit for the function using logic blocks consisting of gate 85 and 46. If we consider D as the select input and A, B, C as the inputs to the MUX, we can access newly added sets of gates; gate 18 (for $D = 1$) and A3 (for $D = 0$). Thus, the H-E of the logic changes to

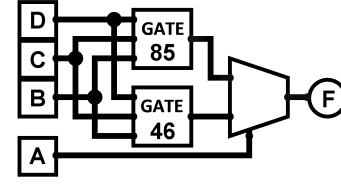


Fig. 9. 2:1 MUX equivalent circuit of Gate #4685

18A3 when D is the select input. However, the the condition of universality does not change, as the H-E consists of 1 (NOR gate) that implies a universal logic. Changing the select line alters the H-E of the accessible gates but does not change the overall nature of the function. A quicker approach to analyse the property of a logic function is presented in **Algorithm 2**.

Algorithm 2 A faster approach to search Universal logic gates

```

1: Input: TruthTable //Truth Table of Function with n inputs.
   Output: Universal or Non-Universal Gate
2: Variable Initialization:
   n = Number of Inputs
   M = 2^n //No. of input logic combinations.
3: TemplateGate[ ] = {1,2,4,7,B,D} //list of universal gates
   obtained from n = 2 as shown in Table I.
4: |.| calculate the cardinality of the array
5: Initialize TT[ ] with the Values from Truth Table in hexadecimal

6: for inputIndx = 3; inputIndx <= n; inputIndx ++ do
7:   for i = 1; i < |TT|; i ++ do
8:     DigitIndx[] = GetDigitComb(TT[i]);
     //denoting each gate for n variable boolean logic ; the
     combination would be till n - 1 digit
9:     CountDigit = |DigitIndx|
10:    for j = 1; j < CountDigit; j ++ do
11:      for k = 1; k < |TemplateGate|; k ++ do
12:        if DigitIndx[j] == |TemplateGate[k]| then
13:          TemplateGate[ ].append = TT[i]
14:        break;
15:      end if
16:    end for
17:  end for
18:  return TemplateGate
19: end for
20: end for

```

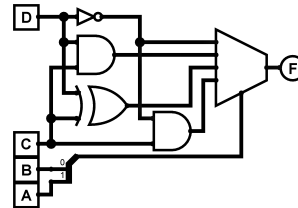


Fig. 8. 4:1 MUX equivalent circuit of universal logic #4685

TABLE X. Truth table of Universal Gate #4685

A	B	C	D	#4685
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

V. APPLICABILITY OF THE UNIVERSAL LOGIC GATES TO CERTAIN APPLICATIONS: A CASE STUDY

NAND and NOR gates are the most fundamental gates that can be created with the least amount of hardware in CMOS


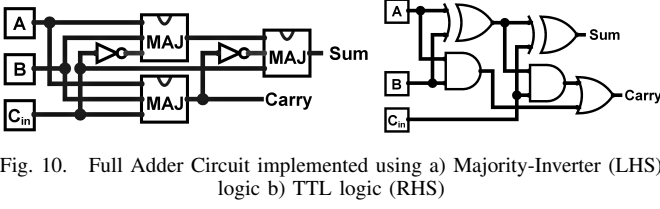


Fig. 11. Full Adder implemented using only NAND Logic

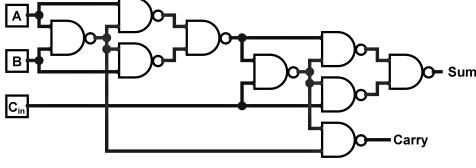

technology. These versatile universal logic gates, which can execute a large number of different logic functions, are playing an increasingly critical role in modern digital systems. As a result, all Boolean Functions are implemented using NAND and NOR equivalent circuits. The amount of hardware needed to generate a function increases if other Universal Gates are employed in CMOS implementation. Whereas, the most fundamental units for TTL-based implementation are AND, OR, and NOT gates; hence, these gates are utilised to construct functions to minimise hardware complexity in a technology.

Low-cost hardware solutions are generally technology-dependent, relying on certain technologies or components to achieve cost-effectiveness. In applications like Quantum Dot Cellular Automata (QCA) [16], [17], Majority Gate and NOT Gate are the most fundamental logic units. Majority gate with H-E E8 is represented by $f = AB + BC + CA$. Employing Majority gate instead of traditional logic gates it is possible to reduce both the number of connections between gates and the total number of gates. For example, to create a Full Adder circuit, Majority and Inverter gates based design shown in Fig. 10a) requires 5 logic Gates (3 Majority and 2 Inverter). Only three gates, including two inverters, are needed to construct a full adder. A Boolean implementation using NAND and NOR gates, on the other hand, necessitates a more complex design with 9 gates (requiring 36 transistors). Thus, Majority-Inverter logic based approach is more hardware efficient than NAND and NOR implementations of the same. A vast majority of other logic functions can be efficiently implemented using majority logic. The other two architectures using only NAND logic and TTL logic are shown in Fig. 11 and 10b) respectively. In essence, the technologies utilised to tackle a problem are not necessarily application independent; rather, attaining a hardware efficient solution is highly dependent on the application domain. As a result, certain basic gates are widely used in implementation technologies in order to reduce the overall hardware needs of the circuit.

VI. CONCLUSION

In this work, a detailed and diverse study on the property of universality of a logic is carried out. Further, the number of Universal logic gates for a given number of input variables

is determined. It is observed that there 56 Universal gates for $N = 3$ and the ratio of Universal Gates to all possible logic gates for $N > 3$ saturates to $\frac{1}{4}$ or 0.25. We have also discussed how the properties of Universal Gates alter when a complete set $\{0, 1, G\}$ is considered. Introducing the Multiplexer equivalent property of a logic, the reasoning behind the universality of a complete set is demonstrated. The number of universal logic is increased from 2 to 6 for $N = 2$ and 56 to 225 for $N = 3$. The increased availability of Universal Gates in the future makes such data extremely useful for logic synthesis of a specified function. By deducing the logic for minimising a function with the included set of Universal gates, one can go on to design cheaper arithmetic circuits. The applicability of the newly found universal logic has been discussed in great detail with the aim to reduce the hardware in specific applications. The presented logic analysis can be extrapolated to larger base number systems to locate the Universal gates. In future, we move forward for further logic minimization methods employing these gates. Also, we will try to explore the characteristics of the newly found universal logic gates and investigate their potential uses with respect to logic design and synthesis in certain fields of study.

REFERENCES

- [1] Zhang, W. & Wu, N. Smart Universal Multiple-Valued Logic Gates by Transferring Single Electrons. *IEEE Transactions On Nanotechnology*. 7, 440-450 (2008)
- [2] Jiao, S., Feng, J., Zhang, L., Wu, D. & Shen, Y. Optical Logic Gate Operations With Single-Pixel Imaging. *IEEE Journal Of Selected Topics In Quantum Electronics*. 29, 1-8 (2023)
- [3] Kolay, S., Bandyopadhyay, M. & Chattopadhyay, S. Design and Testing of Digital Logic Gates Using HCS Macro-Model. *IEEE Transactions On Circuits And Systems II: Express Briefs*. 70, 1134-1138 (2023)
- [4] Charlot, N. & Gauthier, D. Sensitivity of a Chaotic Logic Gate. *IEEE Transactions On Circuits And Systems II: Express Briefs*. 69, 3339-3343 (2022)
- [5] Lin, C. & Marek-Sadowska, M. On designing universal logic blocks and their application to FPGA design. *IEEE Transactions On Computer-Aided Design Of Integrated Circuits And Systems*. 16, 519-527 (1997)
- [6] Liu, L., Liu, P., Ga, L. & Ai, J. Advances in applications of molecular logic gates. *ACS Omega*. 6, 30189-30204 (2021,11)
- [7] Noiri, A., Takeda, K., Nakajima, T., Kobayashi, T., Sammak, A., Scappucci, G. & Tarucha, S. Fast universal quantum gate above the fault-tolerance threshold in silicon. *Nature*. 601, 338-342 (2022,1), <https://doi.org/10.1038/s41586-021-04182-y>
- [8] Lima, F., Johann, M., Guntzel, J., Carro, L. & Reis, R. A tool for analysis of universal logic gates functionality. *Proceedings. XII Symposium On Integrated Circuits And Systems Design (Cat. No.PR00387)*. pp. 184-187 (1999)
- [9] Church, A. Introduction to Mathematical Logic. (Princeton University Press,1956)
- [10] Friedman, A. & Menon, P. Theory and Design of Switching Circuits. (Computer Science Press, Woodland Hills,1975)
- [11] Mitra, S., Goenka, A. & Naskar, M. A Low Latency and Compact GCD Design using an Intelligent Seed-Selection Scheme of LL-PRNG. *IEEE Transactions On Computer-Aided Design Of Integrated Circuits And Systems*. (2023)
- [12] Klir, G. Introduction to the Methodology of Switching Circuits. (van Nostrand, New York,1972)
- [13] Mukhopadhyay, A. Complete sets of logic primitives. (Academic Press, New York,1971)
- [14] Jevons, W. Pure Logic. (London,1864)
- [15] Post, E. The Two-Valued Iterative Systems of Mathematical Logic. (Princeton University Press, Princeton, NJ,1941)
- [16] Reis, D., Campos, C., Soares, T., Neto, O. & Torres, F. A Methodology for Standard Cell Design for QCA. *2016 IEEE International Symposium On Circuits And Systems (ISCAS)*. pp. 2114-2117 (2016)
- [17] Farrelly, T. A review of Quantum Cellular Automata. *Quantum*. 4 pp. 368 (2020,11), <https://doi.org/10.22331/q-2020-11-30-368>