

# Analog Computer Understanding of Hamiltonian Paths

Bryce M. Kim

04/20/2015

## Abstract

This paper explores finding existence of undirected hamiltonian paths in a graph using classical analog circuits, specifically low-pass filters. While other alternatives are possible, a first-order RC low-pass filter is chosen to describe the process. The paper proposes a way of obtaining time complexity for checking existence, and then shows that the time complexity of the circuits is around  $O(n \log n)$  where  $n$  is the number of vertices in a graph.

## 1 Introduction: Undirected Hamiltonian Path Existence Problem

Graph  $G = (V, E)$  is defined with a set  $V$  of vertices along with a set  $E$  of undirected edges connecting vertices. We will denote a path by the following formalism:  $a - b - c$  where  $a, b, c$  are vertices and  $-$  represents edges. Generally,  $a, b, c$  will be represented with positive integers. Unlike convention, we will also include the case where a loop or a self-loop exists as part of a path. That is,  $a - b - a$ ,  $b - c - d - e - c - a$  or  $b - c - d - e - c - b$  is considered as a path.  $n = n_v$  is the cardinality of  $V$ ,  $n_e$  is the cardinality of  $E$ . A  $n$ -path is defined to be a path with  $n$  vertices. This is the only class of paths we will have interests in this paper.

We will re-interpret Hamiltonian path existence problem using a  $n \times n$  grid and others.

**Definition 1.1.** The grid contains  $n$  vertical columns. Each column contains  $n$  vertices, and the vertices in the same column are not connected by wires.

**Definition 1.2.** All vertices are numbered with positive integers greater than 1.

**Definition 1.3.** Each wire transmits a voltage signal  $f(t)$ . For our consideration, location does not matter, so all of our signals are solely function of time. These signals can be transformed into the Fourier transform frequency representation.

**Definition 1.4.** Like in digital consideration, we will assume that wires have no time delay. (ideal wire)

**Definition 1.5.** For each vertex  $x$  at column  $a > 1$ , if vertex  $y$  satisfies  $(x, y) \in E$  or  $(y, x) \in E$ , vertex  $y$  frequency multiplier (or oscillator, in case of  $a - 1 = 1$ ) at column  $a - 1$  is connected by a wire to the sum operator at vertex  $x$ /column  $a$ .

**Definition 1.6.** As we allow self-loops, while  $(x, x) \notin E$ , vertex  $x$  at column  $a - 1$  is connected by a wire to the sum operator at vertex  $x$ /column  $a$ .

**Definition 1.7.** Each vertex  $x$  at column 1, the first column, only has an ideal oscillator, transmitting  $e^{ixt}$  to wires connected to the second column.

**Definition 1.8.** A sum operator just sums up the signals transmitted by wires.

**Definition 1.9.** Each sum operator at vertex  $x$ /column  $a$  is connected by frequency multiplier, with frequency multiplication factor of  $x$ . Frequency multiplier transforms  $e^{iw_1t} + e^{iw_2t} + \dots$  into  $e^{ixw_1t} + e^{ixw_2t} + \dots$

**Definition 1.10.** At column  $n$ , after a signal passes through frequency multipliers connected to sum operators, any wire incident from column  $n$  is connected to a final sum operator, which produces the final signal  $y(t)$ .

Thus it is clear that we need  $n(n - 1) + 1$  sum operators (or adders, equivalently) and  $n(n - 1)$  frequency multipliers for the grid above. The number of wires are dependent on  $E$ , but the maximum number of wires required is  $n^2(n - 1) + n(n - 1) + n$ , where the last  $n$  comes the wires that connect column  $n$  to the last sum operator, and  $n(n - 1)$  comes from the wires that connect a single sum operator to a single frequency multipliers.

The output of the circuit grid defined above is  $y(t)$ , as mentioned above. Let  $V = \{v_1, v_2, \dots, v_n\}$ .

**Definition 1.11.** The final sum operator, which produces the signal  $y(t)$  is connected to the ideal mixer  $M$ , which outputs the product of  $y(t)$  with  $e^{-iut}$  where  $u = v_1v_2v_3\dots v_n$ . In Fourier transform, this is equivalent to converting  $Y(\omega)$  with  $Y(\omega + u)$ , where  $Y(\omega)$  is Fourier transform of  $y(t)$ . Let the output of  $M$  be  $k(t)$ .

From the above, it is clear that  $Ce^{iut}$  inside  $y(t)$  represents hamiltonian paths, with  $C$  representing the number of hamiltonian paths. In  $k(t)$ , frequency 0 represents hamiltonian paths, as all frequencies are shifted left by  $u$ .

Because our chosen low-pass filter will be first-order, we will also pass  $k(t)$  to a frequency multiplier that multiplies frequencies by  $v_n^{4n}$  where  $v_n$  is the greatest-numbered vertex, to ensure that the frequencies other than zero frequency parts of  $k(t)$  will be sufficiently high frequencies. (Multiplying zero by  $v_n^{4n}$  is zero) For higher-order filters, like third-order filter, this additional frequency-multiplying process will not be needed. We will call the resulting signal  $j(t)$ .

As a side note, instead of having input tape in Turing machine, we have to re-wire  $n \times n$  grid every time graph input changes. This  $n \times n$  grid serves as an input to the system involving a low-pass filter.

## 2 Low-pass Filter

Now that we defined the final output  $k(t)$ , the question is how we process  $k(t)$  to give us some information about the number of hamiltonian paths, or  $C$ . To do this, we pass it to a low-pass filter. But we cannot simply assume an ideal low-pass filter, represented by  $H(\omega) = \text{rect}(\omega)$ , where  $\text{rect}(\omega) = 1$  for  $-0.5 < \omega < 0.5$  and  $\text{rect}(\omega) = 0$  otherwise, because there is no such an ideal filter even to the approximate level.

Thus we will choose a simple physical first-order RC low-pass filter, described in figure 1.

By Kirchoff's Voltage Law, the low-pass filter in figure 1 has the ODE of:

$$\frac{dV_{out}}{dt} + \frac{V_{out}}{\tau} = \frac{V_{in}}{\tau}$$

where  $\tau = RC$ . As this ODE is linear, to figure out the behavior of this low-pass filter, we first consider  $V_{in} = De^{i\omega t}$ , where  $\omega$  is some arbitrary frequency.

Using initial capacitor voltage condition at the starting time  $t = 0$  as  $V_{out:t=0} = 0$ ,

$$V_{out} = \frac{D}{1 + i\omega\tau} \left[ e^{i\omega t} - e^{-t/\tau} \right]$$

Assume that  $v_n = n + 1$ . Also for calculation convenience, assume that  $\tau = RC = 1$ . In steady state  $t = \infty$ , because every  $\omega$  of  $j(t)$  except zero is greater than/equal to  $(n + 1)^{4n}$ , and the total number of paths in  $G$  with  $n$  total vertices can only have maximum of  $n^n$   $n$ -paths,  $j(\infty)$ 's value mostly comes from the hamiltonian/zero-frequency part. Other frequency parts only contribute less than  $1/n^{3n}$  in magnitude. Thus at time  $\infty$ , the number of hamiltonian paths is discovered from the magnitude of  $j(\infty)$ ,  $|j(\infty)|$ . However, calculations must be done on finite time, so the steady-state case only forms a background for our discussions, not the main part.

Note that in ordinary signal processing, keeping phase errors small is very important, but for the use of signal processing tools to analyze hamiltonian paths, phase errors are not of any concern.

### 2.1 Time Complexity of the Circuit

But moving to the finite time is simple: figure out the time when  $e^{-t/\tau}$  decays to  $1/n^{4n}$ . Then high frequency parts only contribute a negligible value to  $j(t)$ . Now since  $\tau = 1$  assumption is made, set equality  $e^{-t_c} = 1/n^{4n}$ . Taking the natural log to each side,  $t_c = 4n \ln n < 4n^2$ . Thus, the critical time, which is when the exponential decaying factor decays to  $1/n^{4n}$ , increases approximately linearly as the size of input  $n$  increases.

After this critical value, the value of  $|j(t)|$  can simply be sampled by a digital computer to get the number of hamiltonian paths. Note that theoretically only one sample is required to measure the number of hamiltonian paths. This is because frequency 0 does not have any oscillating part, and thus will have constant offset relative to 0.

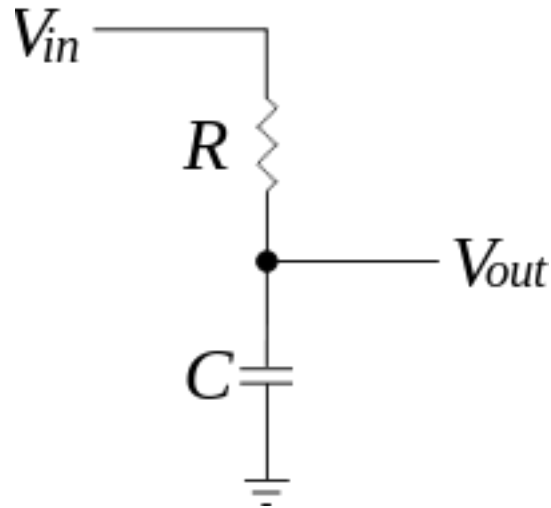


Figure 1: A first-order RC low-pass filter

Thus time complexity of the circuit to solve the number of hamiltonian paths is  $O(n \log n)$ , which is smaller than  $O(n^2)$ .

## 2.2 Size and Time Complexity

The above demonstrates that the number of needed components and needed time does not grow exponentially as the input graph size increase. All the values used in the circuit does not require exponentially-growing number of digits in a digital computer, as the graph size increases.

## 2.3 Real Deviations

While the system described above is a physical system, not just a logical system, it is nevertheless still an ideal system. Oscillators are not perfect oscillators, resistors and capacitors are not ideal ones, wires have extra resistances, even of time-varying ones. Thermal effects may change system properties.

We will leave these questions to future papers. However, note that if errors introduced by real deviations affect the zero-frequency part below a certain threshold, they may safely be ignored. For example, multiplying by  $e^{-iut}$  may not shift frequency  $u$  to 0 in real-time systems. Usually, however, frequencies do spread out, and often 0 frequency part is not emptied.

While there are many non-ideal issues that affect oscillators (and possibly for mixers and frequency multipliers too), if we assume time-decaying realistic oscillators, Q-factor may be used to gauge this performance part. Assume that this decaying time is associated with our measurement time also - which means that measurement time is just enough to allow us computation before signals

almost disappear completely. More theoretically, Gabor limit is there:

$$\sigma_t \sigma_f \geq \frac{1}{4\pi}$$

While the above formula only gives the bound, assume that every system has equal  $\sigma_t \sigma_f$ . If our measurement time increases, so must decaying times. Representing this as increase in  $\sigma_t$ ,  $\sigma_f$  will decrease. In case of an oscillator, this is equal to becoming close to an ideal oscillator. Thus increasing necessary decaying time will help the performance of oscillators. As thus, the size of input is not an extra constraint for Q factor problems of real-time systems.

### 3 Conclusion

This paper introduces an analog circuit, involving a  $n \times n$  grid (subcircuit) and a low-pass filter that allows us to compute the number of hamiltonian paths in an ideal physical environment, with the assumption of ideal oscillators/mixers/frequency multipliers. Then the paper formulates time complexity of such a circuit and concludes that it is  $O(n \log n)$ , with non-exponential space complexity.

## 4 References

Baumgardner, J. et al. (2009). 'Solving a Hamiltonian Path Problem with a bacterial computer', *Journal of Biological Engineering*, 3(11): 109–124.

Haist, T. et al. (2007). 'An Optical Solution For The Traveling Salesman Problem'. *Optics Express*, 15(16): 10473–10482.

Sartakhti, J. et al. (2013). 'A new light-based solution to the Hamiltonian path problem'. *Future Generation Computer Systems*, 29(2): 520-527.