

# Experimenting with RC and RL series circuits using smartphones as function generators and oscilloscopes

Ives Torriente-García<sup>1</sup>, Francisco M. Muñoz-Pérez<sup>1</sup>, Arturo C. Martí<sup>2</sup>, Martín Monteiro<sup>3</sup>, Juan C. Castro-Palacio<sup>1</sup>, Juan A. Monsoriu<sup>1,\*</sup>

<sup>1</sup>Centro de Tecnologías Físicas, Universitat Politècnica de València, 46022 València, Spain.

<sup>2</sup> Instituto de Física, Universidad de la República, 11400 Montevideo, Uruguay.

<sup>3</sup> Universidad ORT Uruguay, 11100 Montevideo, Uruguay.

\*Correspondence: jmonsori@fis.upv.es

**Abstract.** Simple, portable and low-cost experiments as RC and RL series circuits are proposed as examples to experiment with DC circuits. Very common elements are used: few electronics components (resistors, capacitors, coils and connecting wires) and two smartphones. We consider the charging and discharging of a capacitor in the RC circuit and also that of coil in the RL circuit. Using a smartphone as a oscilloscope we observe voltages variations which are the transient response to a square signal generated in the second smartphone. These voltage variations are directly related to the electrostatic or magnetic energy stored in the circuits. The experimental data have been collected with the smartphone used as an oscilloscope. This approach which avoids the use of expensive signal generators, oscilloscopes, or any specialized hardware can be performed in less-favored contexts and even as a home assignment.

**Keywords**— smartphones, function generator, oscilloscope, RC circuit, RL circuit

Date: 30 March 2023

## 1. Introduction

Although smartphones became popular only a decade ago their use in physics laboratories at all levels has become commonplace [1]. The experiments where they are used cover all areas of physics, but in some of them, such as mechanics or waves, it happens more often. In some areas such as electromagnetism their use has focused on experiments involving the measurement of magnetic fields [2, 3, 4]. However, experiments involving electrical circuits have received less attention (see for example [5, 6]). In this paper we propose a set of experiments about simple circuits using a minimal set of electronic components and two smartphones.

Direct current (DC) circuits combining resistors, capacitors and coils such as the RC series circuits or the RL series circuit are a central topic in introductory physics courses. In experimental courses these circuits are approached using function generators, oscilloscopes and multimeters. These instruments are not always available in all institutions, nor is it common for students to have them at home. The experiments proposed here present the advantage

that they can be instrumented in less-favored contexts, but they can also be proposed with a minimum of additional materials as a home assignment for students.

Several ingenious proposals for experiments on simple circuits can be found in the literature. Among them we can highlight [7] which proposed an experiment to study the charge and discharge of a capacitor in an *RC* circuit using a digital voltmeter, a stopwatch and a smartphone as a high-speed camera. Using video analysis it is possible to capture simultaneously the readings of both the voltage across the capacitor and the time elapsed. In another proposal [6] a capacitor is discharged through a resistor and a buzzer. The intensity of the sound produced by the buzzer can be easily related to the voltage across the capacitor and the sound level can be used to estimate the time constant of the circuit. Another approach to *LR*-circuits was recently proposed in [8] using the magnetic field sensor of a smartphone to measure the magnetic field of a coil. It is also worth mentioning another experimental proposal which combines the use of video analysis and analog instruments to experiment with *DC* circuits [9].

The role of smartphones as oscilloscopes was first proposed by Forinash and Wisman [5] using the headphone port designed for connecting an external microphone and speakers to receive data from an external circuit. Other alternative to transform smartphones into oscilloscopes takes the advantage of using Arduino boards to communicate with a smartphone using the Bluetooth interface [10]. This approach can be used even in the case of smartphones which do not include headphone port. It is also worth mentioning the ability to transform a smartphone in an arbitrary function generator as proposed in [11].

Here, we propose an experiment which uses only a smartphone as a measuring device. Another smartphone is used as a signal generator. The outline of the article is as follows. In Section 2 we recall the basic concepts about *DC* circuits. We describe the experimental setup to study *RC* and *RL* series circuits in Section 3. In Section 4 we present and discuss the experimental data. Finally, we devote Section 5 to the final remarks and perspectives.

## 2. Theory on *RC* and *RL* series circuits

Due to their simplicity, *DC* circuits are customarily introduced in introductory physics courses, in particular, they play an important role in almost all the introductory laboratories dealing with electromagnetism. The more typical examples are circuits composed by voltage sources, resistors, capacitors, and coils disposed in a specific configuration. The first cases to be studied are usually the *RC* and *RL* series circuits, that is a resistor connected to a capacitor or coil as shown in Figs. 1 and 2.


It results convenient to study *RC* or *RL* circuits using a square wave as an input signal. When the input voltage is in the maximum value, the capacitor stores energy while when the input voltage is zero this energy is released. The voltage in the capacitor is proportional to the electric field generated which in turn is readily related to electrostatic energy density. The mathematical expressions for the voltage of a charging capacitor in a *RC* series circuit can be easily deduced using the Kirchhoff's first law

$$V_C(t) = V_{mC}(1 - e^{-t/\tau_{RC}}), \quad (1)$$

where  $\tau_{RC} = RC$  is the characteristic time and  $V_{mC}$  is the maximum voltage reached at the capacitor. On the other hand, the discharging of the capacitor is expressed as,

$$V_C(t) = V_{mC}e^{-t/\tau_{RC}}. \quad (2)$$

Analogously, using again a square wave as input signal, we will also study the charge and discharge of the *RL* circuit. While in the *RC* circuit we measure the voltage at the capacitor in

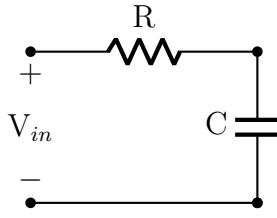

**Figure 1.** Electrical diagram of a  $RC$  series circuit.


the  $RL$  we measure the voltage at the resistor. This contrast is due to the fact that in the  $RC$  the stored energy occurs in the capacitor and the electric field is proportional to the voltage at the capacitor while in the  $RL$  circuit the energy stored in the magnetic field is proportional to the current intensity which in turn is proportional to the voltage at the resistor. The increase of the voltage at the resistor when the square wave reaches its maximum value is be expressed as

$$V_R(t) = V_{mR}(1 - e^{-t/\tau_{RL}}), \quad (3)$$

where in this case the characteristic time is  $\tau_{RL} = L/R$  and  $V_{mR}$  is the maximum voltage reached at the resistor. Likewise, the decay of the voltage at the resistor when the square wave reaches its minimum value is expressed as

$$V_R(t) = V_{mR}e^{-t/\tau_{RL}}. \quad (4)$$

By fitting Eq. 2 and Eq. 4 to the experimental data of the voltage at the capacitor ( $RC$  circuit) during its discharging and to the experimental data of the voltage at the resistor ( $RL$  circuit), the time constants ( $\tau_{RC}$  and  $\tau_{RL}$ ) can be determined and used to calculate the capacitance and inductance, respectively.

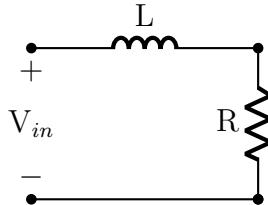


**Figure 2.** Electrical diagram of a  $RL$  series circuit.


### 3. Experiments

The experimental setup is composed by a simple circuit, as mentioned in the previous section a  $RC$  or a  $RL$  and two smartphones. One acts as a function generator and the other as an oscilloscope. The function generator is achieved using the tone generator provided by the free Android app Physics Toolbox Suite [12]. The other smartphone was used as an oscilloscope by means of free Android app Phyphox [13]. Smartphone data that can be analyzed directly on the smartphone or downloaded to a computer using the aforementioned apps.

The charging and discharging of the capacitor (Figs. 1 and 3) is performed by using a square signal whose period contains several time constants. The same idea is used for the  $RL$  series circuit (Figs. 2 and 4). Figs. 3 and 4 show screenshots of the tone generator option of

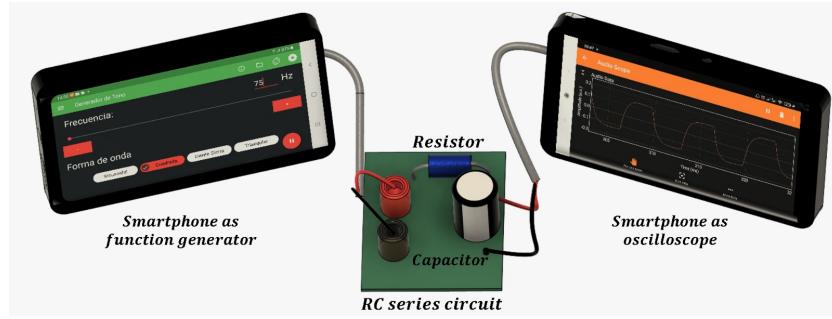

**Figure 3.** Schematic representation of the experimental setup to study  $RC$  circuits used in this work.

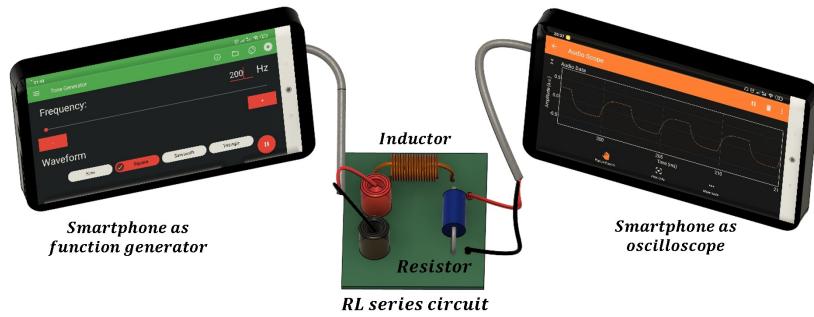

**Figure 4.** Experimental setup corresponding to the  $RL$  circuit studied.

Physics Sensors Toolbox Suite app. which enables the smartphone as a function generator and of Audio Amplitude option of Phyphox app which converts the smartphone to an oscilloscope. The data for both circuits are collected with the Phyphox app.


An important aspect is how to connect the different elements securely. It is possible to make the connections using a TRRS four-conductor jack connector readily available in electronics stores or even by disassembling an old audio cable. Figs. 5 shows the type of jack connector used in this work to allow the electric signals out and in the smartphone through the audio and microphone connections. Observe that the left speaker contact of the first smartphone is connected to the resistor, the ground cables of each smartphone are connected to the capacitor while the microphone terminal connects the second smartphone to the junction of the capacitor and the resistor.

#### 4. Results and discussion

The voltages registered with Phyphox app. are expressed in arbitrary units and time in milliseconds. We are interested in the relative variation of time which is used to determine the circuit time constants ( $\tau_{RC}$  and  $\tau_{RL}$ ) by means of a fitting of Eq. 2 and Eq. 4 to the collected data. Figure 6 shows the voltage *versus* time at the capacitor in the  $RC$  series circuit (Fig. 1) for charging and discharging of the capacitor. The red line indicates the fit curve of the data using Eq. 2. The resulting characteristic time from the fitting is  $\tau_{RC} = 0.4651(24)$  ms. Using this value and the manufacturer value for the resistance  $R = 470(24)$   $\Omega$  the capacitance can be obtained as  $C = \tau_{RC}/R = 0.99(5)$   $\mu\text{F}$ . The manufacturer value for the capacitance is  $1.0(1)$   $\mu\text{F}$ . Therefore, the agreement between the value calculated from the experimental measurements




**Figure 5.** TRRS four-conductor jack connector and wiring diagram.

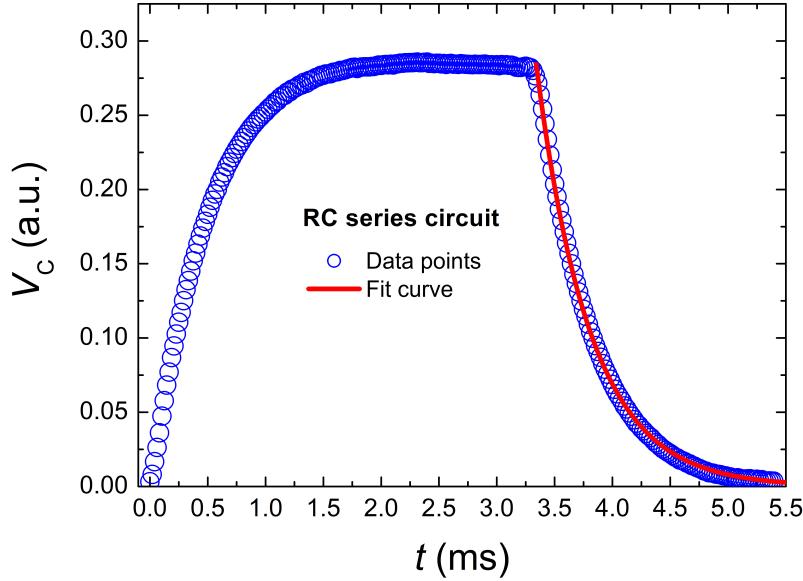

**Figure 6.** Voltage at the capacitor in the  $RC$  series circuit as a function of time.

and that provided by the manufacturer is remarkable.

Similarly, Fig. 7 shows the voltage *versus* time at the resistor in the  $RL$  series circuit (Fig. 2) for the cases when the circuit is switched on and off, respectively. The behavior of the voltage at the resistor is linear with the behavior of the current in the circuit as  $V_R(t) = I(t)R$ . The red line indicates the fit curve of the data using Eq. 4. The resulting characteristic time from the fitting is  $\tau_{RL} = 0.3593(20)$  ms. Combining this value and the manufacturer value for the resistance  $R = 275(14)$   $\Omega$  the inductance can be obtained as  $L = \tau_{RL}R = 0.099(9)$  H. The manufacturer value for the inductance is 0.10(1) H. Therefore, a percentage deviation of 1 % between the calculated and manufacturer values is obtained.

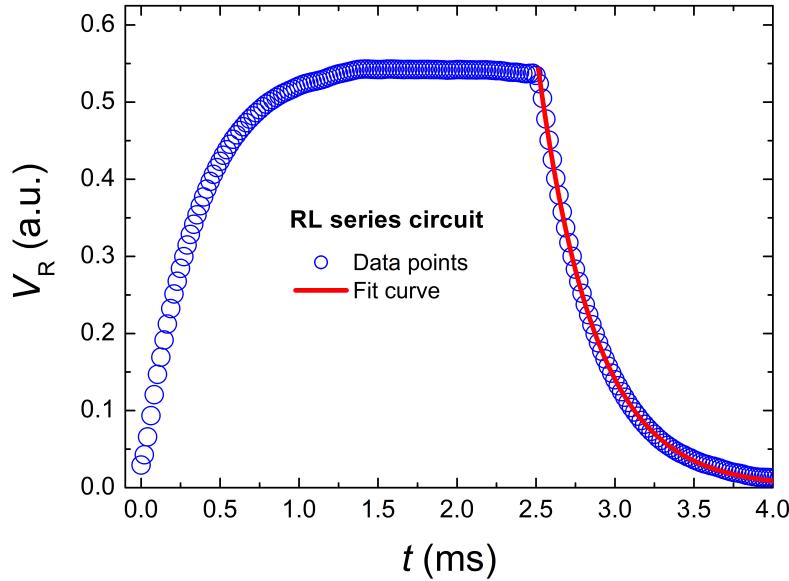

**Figure 7.** Voltage at the resistor in the RL series circuit as a function of time.

## 5. Final remarks and perspectives

We have proposed an experiment to investigate simple DC circuits and in particular  $RC$  and  $RL$  series circuits. The only elements needed for our experiments were common electronic components (resistors, coils and capacitors), connecting wires, a couple of dismantled jack connectors and two smartphones, one used as a signal generator and the other as an oscilloscope. It is also worth highlighting that, in contrast to other approaches like [14], our experimental setup does not require any additional hardware or specialized electronic device.

Results for the charging and discharging of a capacitor in an  $RC$  series circuit yield a 1% of percentage difference when the calculated value of capacitance (obtained from the fitted time constant) is compared with the manufacturer value. As for the  $RL$  series constant, the inductance of the coil was calculated from the corresponding time constant, yielding a 1% of percentage deviation with respect to the manufacturer value.

This proposal has the advantage of being portable and low-cost as it requires a minimum set of materials. It can be proposed in a wide range of socio-cultural contexts and can even be proposed to students as a challenge to be implemented at home if they have only a minimal set of electronic components and their own smartphones.

The use of smartphones as a function generator with possibility of choosing among different types of signals (i.e. square, triangular, sinusoidal, saw-tooth) and also as an oscilloscope to visualize variable voltages, opens up the scenario for a variety of teaching innovations on this topic. For instance,  $RLC$  circuits operating with sinusoidal signals as input can be studied. Similarly, other components such as diodes when incorporated to simple circuits (e.g. low- and high-pass filters) can be addressed as well with this approach.

## 6. Acknowledgments

J.A.M. and J.C.C.P. would like to thank the Instituto de Ciencias de la Educación (Institute of Education Sciences) at the Universitat Politècnica de València (UPV) for its support to the teaching innovation group MSEL.

## References

- [1] Monteiro M and Martí A C 2022 *American Journal of Physics* **90** 328–343
- [2] Arribas E, Escobar I, Suarez C P, Najera A and Beléndez A 2015 *European Journal of Physics* **36** 065002 URL <http://stacks.iop.org/0143-0807/36/i=6/a=065002>
- [3] Monteiro M, Stari C, Cabeza C and Martí A C 2017 *The Physics Teacher* **55** 580–581
- [4] Monteiro M, Organtini G and Martí A C 2020 *The Physics Teacher* **58** 600–601
- [5] Forinash K and Wisman R F 2012 *The Physics Teacher* **50** 242–243
- [6] Groff J R 2019 *The Physics Teacher* **57** 393–396 (Preprint <https://doi.org/10.1119/1.5124280>) URL <https://doi.org/10.1119/1.5124280>
- [7] Pili U, Violanda R and Pili J 2019 *Physics Education* **54** 033004
- [8] Westermann N, Staacks S, Heinke H and Möhrke P 2022 *Physics Education* **57** 065024
- [9] Aguilar-Marín P, Chavez-Bacilio M and Jáuregui-Rosas S 2018 *European Journal of Physics* **39** 035204
- [10] Ballesta S V, Saez R, Iglesias J and Vernet A 2020 *The Physics Teacher* **58** 663–665
- [11] Mathew E, Karamchandani S and Biradar M T 2015 *Procedia Computer Science* **49** 229–234
- [12] Sotware V 2020 Physics toolbox URL <https://www.vieyrasoftware.net/>
- [13] Staacks S, Hütz S, Heinke H and Stampfer C 2018 *Physics Education* **53** 045009
- [14] Ramos R and Devers C 2020 *Physics Education* **55** 023003 URL <https://dx.doi.org/10.1088/1361-6552/ab606b>