

# AMSBENCH: A COMPREHENSIVE BENCHMARK FOR EVALUATING MLLM CAPABILITIES IN AMS CIRCUITS

Yichen Shi<sup>\*1,5</sup>, Ze Zhang<sup>\*4,5</sup>, Hongyang Wang<sup>\*5</sup>, Zhuofu Tao<sup>2</sup>, Li Huang<sup>1,5</sup>, Zhongyi Li<sup>5</sup>  
 Bingyu Chen<sup>2</sup>, Yaxin Wang<sup>2</sup>, Zhen Huang<sup>5</sup>, Xuhua Liu<sup>4,5</sup>, Quan Chen<sup>4</sup>, Zhiping Yu<sup>3</sup>  
 Ting-Jung Lin<sup>†5</sup>, Lei He<sup>†2,5</sup>

<sup>1</sup> Shanghai Jiao Tong University   <sup>2</sup>University of California, Los Angeles

<sup>3</sup>Tsinghua University   <sup>4</sup> Southern University of Science and Technology

<sup>5</sup> Eastern Institute of Technology, Ningbo

project page: <https://amsbench.github.io/>

## ABSTRACT

Analog/Mixed-Signal (AMS) circuits play a critical role in the integrated circuit (IC) industry. However, automating Analog/Mixed-Signal (AMS) circuit design has remained a longstanding challenge due to its difficulty and complexity. Although recent advances in Multi-modal Large Language Models (MLLMs) offer promising potential for supporting AMS circuit analysis and design, current research typically evaluates MLLMs on isolated tasks within the domain, lacking a comprehensive benchmark that systematically assesses model capabilities across diverse AMS-related challenges. To address this gap, we introduce AMSbench, a benchmark suite designed to evaluate MLLM performance across critical tasks including circuit schematic perception, circuit analysis, and circuit design. AMSbench comprises approximately 8000 test questions spanning multiple difficulty levels and assesses eight prominent models, encompassing both open-source and proprietary solutions such as Qwen 2.5-VL and Gemini 2.5 Pro. Our evaluation highlights significant limitations in current MLLMs, particularly in complex multi-modal reasoning and sophisticated circuit design tasks. These results underscore the necessity of advancing MLLMs’ understanding and effective application of circuit-specific knowledge, thereby narrowing the existing performance gap relative to human expertise and moving toward fully automated AMS circuit design workflows. Our data is released at this URL.

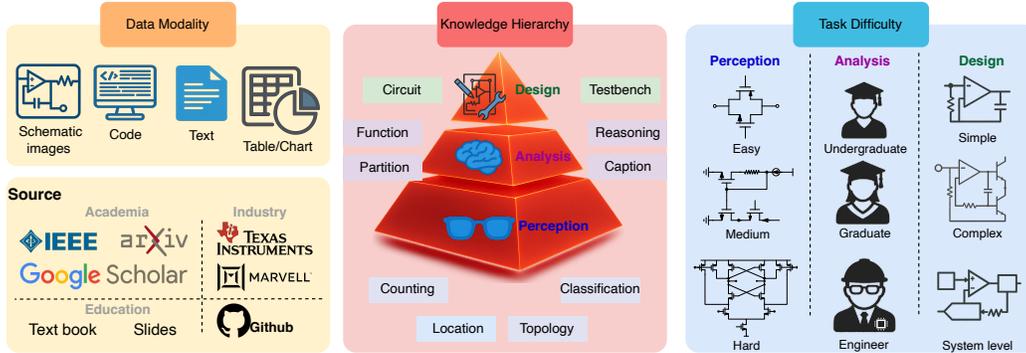


Figure 1: **Overview of AMSbench.** AMSbench includes multimodal question-answer pairs collected from both academia and industry. The tasks are divided into schematic perception, circuit analysis, and circuit design.

# 1 INTRODUCTION

The rapid advancement of large language models (LLMs) and multimodal large language models (MLLMs) has led to significant breakthroughs across diverse domains, including autonomous driving (Cui et al., 2024), scientific research (Hao et al., 2025; Yue et al., 2024), mathematics (Zhang et al., 2024; Lu et al., 2023; Yang et al., 2024b), and programming (Zhong & Wang, 2024). In the domain of Electronic Design Automation (EDA), these models have shown promise, particularly in the automated design of digital circuits (Bhandari et al., 2025). On the contrary, automating analog/mixed-signal (AMS) circuit design has been a longstanding challenge for its reliance on human experience. Today’s AI-driven automatic AMS design still faces considerable challenges due to the scarcity of high-quality data and the intrinsic complexity of multi-modal data. As a result, the exploration and application of LLMs in AMS circuit design remain limited and exhibit relatively poor performance (Gao et al., 2025; Lai et al., 2025; Chen et al., 2024). Furthermore, current applications focus on verbal information, while AMS circuits rely on other modalities as well, such as schematics, plots, and charts.

A primary obstacle lies in the limited capability of existing MLLMs to accurately interpret circuit schematics. Unlike netlists, schematics convey richer and more nuanced structural information beyond abstract connectivity. Recent work (Tao et al., 2024; Bhandari et al., 2025) has recognized this limitation and introduced tools capable of automatically converting schematics into netlists, thereby enabling the creation of large-scale, high-quality datasets suitable for training models. Recent advances in the visual capabilities of MLLMs (e.g., GPT-4o (Hurst et al., 2024) and Qwen2.5 (Yang et al., 2024a)) have significantly improved schematic recognition accuracy, laying a solid foundation for the automated analysis and design of AMS circuits. Despite these advancements, current applications often focus on isolated tasks—such as netlist generation (Lai et al., 2025; Liu et al., 2024) and error identification (Chaudhuri et al., 2025)—while lacking comprehensive evaluation frameworks.

In particular, there has been little systematic investigation into the following three fundamental questions:

1. How accurately can models recognize and interpret AMS circuit schematics?
2. What is the upper bound of domain-specific knowledge that models can attain in AMS circuit analysis and design?
3. To what degree are models capable of supporting the automation of AMS circuit design?

To address these questions and bridge the existing research gaps, we propose AMSbench, a comprehensive benchmark designed to evaluate the capabilities of advanced models in the context of AMS circuit design. AMSbench assesses model performance across three key dimensions: **perception, analysis, and design**.

In the perception task, the objective is to evaluate how accurately MLLMs can generate netlists directly from circuit schematics, reflecting their schematic recognition capabilities. This is a non-trivial challenge due to the large number of components and their intricate interconnections. We further decompose this task into sub-tasks such as component counting, component classification, and interconnect recognition, culminating in the primary goal of accurate netlist generation. The analysis task examines the models’ understanding of circuit-related images, ability to identify critical building blocks, and comprehension of trade-offs among performance metrics—key aspects in AMS circuit design and verification. Finally, the design task investigates whether models can synthesize circuits that satisfy given specifications. We also evaluate their ability to generate appropriate testbenches to assess circuit performance across multiple criteria.

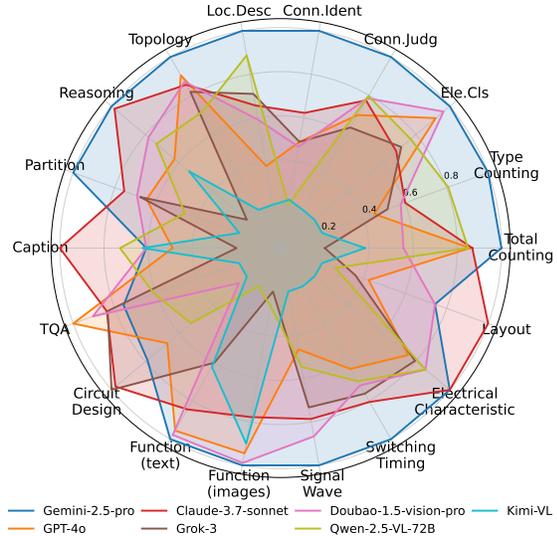


Figure 2: Comparison of top MLLMs on 18 sub-tasks(w/o DeepSeek-R1 on VQA tasks, which lacks visual processing capability)

To the best of our knowledge, AMSbench is the first holistic benchmark that systematically evaluates the performance of advanced models in AMS circuits. The overall benchmarking results of state-of-the-art models using AMSbench are illustrated in Fig. 2. Our contributions are summarized as follows:

- We construct **AMSbench**, a large-scale, high-quality multimodal benchmark designed to rigorously evaluate the perception, analysis, and design capabilities of MLLMs in the AMS circuit domain. AMSbench consists of three major components: AMS-Perception (6k), AMS-Analysis (2k), and AMS-Design (68).
- We conduct a comprehensive evaluation of both open-source and proprietary models on AMSbench, providing detailed comparisons and performance insights across all tasks. Furthermore, we present in-depth analyses highlighting the key challenges that must be addressed to enhance the applicability of (M)LLMs in the AMS circuit domain, and we further discuss several potential solutions and research directions to overcome these challenges.
- We release the AMSbench dataset at the provided URL, fostering transparency and reproducibility in this emerging research area.

Table 1: Comparison between existing AMS datasets and benchmarks. *Task* includes three categories: P (Perception), A (Analysis), and D (Design). Q&A stands for Question and Answer.

Dataset/Benchmark	Modality	Task	Size	Label Type	Difficulty Level
AMSnet (Tao et al., 2024)	Image-only	P	1K	Netlist	✗
Masala-CHI (Bhandari et al., 2025)	Text & Image	P	6K	Netlist, Caption	✗
AnalogGenie (Gao et al., 2025)	Text & Image	D	3K	Netlist	✗
Analogcoder (Lai et al., 2025)	Text-only	D	24	Netlist	✓
MMCircuitEval (Zhao et al., 2025)	Text & Image	P&A&D	3k	Q & A	✓
<b>AMSbench(Ours)</b>	<b>Text &amp; Image</b>	<b>P&amp;A&amp;D</b>	<b>8K</b>	<b>Netlist, Caption, Q &amp; A</b>	<b>✓</b>

## 2 RELATED WORK

### 2.1 LLM FOR CIRCUIT DESIGN

LLMs have demonstrated remarkable potential in the field of EDA, excelling in tasks related to system-level design (Yan et al., 2023), RTL (Blocklove et al., 2023; Fu et al., 2023), synthesis and physical design of digital circuits. This success is primarily due to the modular nature of digital circuit descriptions, which resemble software languages. However, AMS circuit designs, with their transistor-level descriptions, pose a significantly greater challenge for LLMs in terms of accurate understanding and description. Some exploratory work has been undertaken in AMS circuit design (Pan et al., 2025; Fang et al., 2025). Artisan (Chen et al., 2024) develops a LLM that automatically generates operational amplifiers by combining advanced prompt engineering techniques like Supervised Fine-Tuning (SFT) and Tree of Thought. Analogcoder (Lai et al., 2025) proposes using LLMs with predefined sub-circuit libraries to achieve an iterative design and optimization flow. AnalogGenie (Gao et al., 2025) converts circuit topologies into Eulerian circuit representations and uses SFT for synthesizing circuits based on the design requirements. To ensure that the generated circuits can meet specifications, AnalogGenie applies Reinforcement Learning with Human Feedback (RLHF) (Ouyang et al., 2022) as a post-training technique. ADO-LLM (Yin et al., 2024) combines LLMs with Bayesian optimization to generate higher-quality candidate design samples, enhancing efficiency in the transistor sizing process. Layout Copilot uses multiple intelligent agents to improve the efficiency and performance of automated layout generation. AMSnet-KG (Shi et al., 2024) employs a knowledge graph-based RAG (Retrieval-Augmented Generation) approach, based on a large-scale, pre-constructed circuit database, to select and generate circuit topologies that meet specifications. However, it is worth noting that these studies mainly focus on purely language-based LLMs, while circuit design often relies heavily on schematic diagrams. Both Masala-CHAI (Bhandari et al., 2025) and AMSnet (Tao et al., 2024) have pointed out that existing MLLMs still lack the capability to effectively recognize circuit schematics.

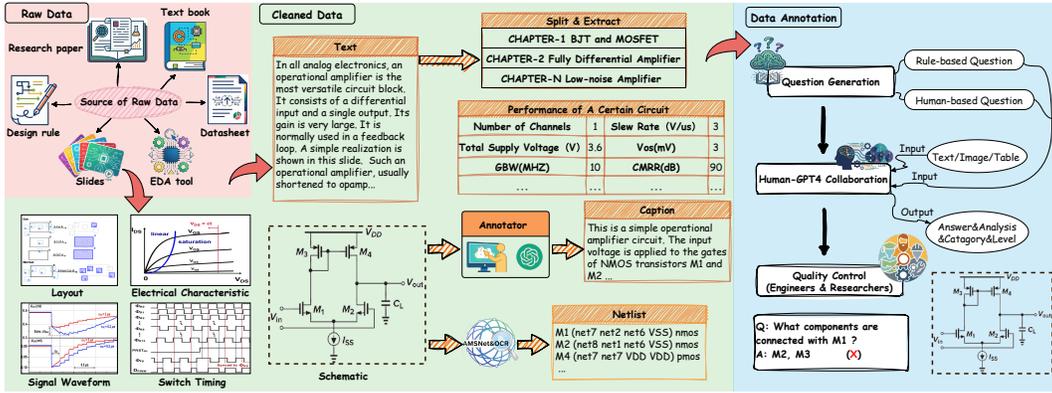


Figure 3: Pipeline of AMSbench construction process.

## 2.2 BENCHMARKING FOR EDA

The academic infrastructure for LLM research in EDA has made significant progress. Abundant available benchmarks and datasets have facilitated effective development of LLMs in EDA. VerilogEval (Liu et al., 2023) and RTLLM (Lu et al., 2024) introduce benchmarks for evaluating RTL code generation. However, these benchmarks focus primarily on digital circuits. Due to the complexity and irregularity of analog circuits, AMS circuit design is highly experience-driven, making it difficult to establish fair evaluation methods. Hence, benchmarks in the analog circuit domain remain scarce. We summarize the existing datasets and benchmarks for AMS circuits in Table 1. Analogcoder (Lai et al., 2025) proposes a benchmark to evaluate LLMs in AMS circuit design, categorizing circuits into three levels: easy, medium, and hard. However, it is limited to the main circuits and did not touch any testbench. Currently, benchmarks in the AMS circuit and EDA domains are limited to verbal questions. However, AMS circuit design is naturally multi-modal, as designers are required to recognize, understand, and reason about circuit schematics.

## 3 AMSBENCH CONSTRUCTION


### 3.1 DATA COLLECTION AND CURATION

To cover a wide range of knowledge and typical question types in the AMS circuit domain, we gather a diverse collection of research papers, textbooks (Razavi, 2005; Gray et al., 2009; Allen & Holberg, 2011; Sansen, 2007), commercial circuit datasheets and EDA tool. We convert all documents from PDF to Markdown format using MinerU (Wang et al., 2024), enabling efficient extraction of embedded visual elements such as circuit schematics. For schematic-to-netlist translation, we utilize AMSnet (Tao et al., 2024) and OCR, which allows us to accurately recover component-level connectivity and circuit topology. To enrich the dataset with semantic information, we use a combination of manual annotations from field experts and outputs from state-of-the-art MLLMs (Hurst et al., 2024; Yang et al., 2024a). We then apply carefully crafted prompt engineering and filter strategies to generate detailed schematic captions. This process yields high-quality pairs of <circuit schematic, caption>. For textbook-derived data, we organize content according to the logical structure and chapter alignment of each source. For datasheet content, we extract structured performance specifications associated with each circuit.

Based on the extracted information, we build a question–answer dataset, where questions are generated through rules and manual design, and answers are obtained from both human experts and LLMs. We adopted a multi-stage data quality control process, relying on professional circuit engineers as well as doctoral and master’s students in circuit-related fields to filter and refine the generated data, thereby assisting in the construction and quality assurance of AMSbench, as illustrated in Fig. 4.
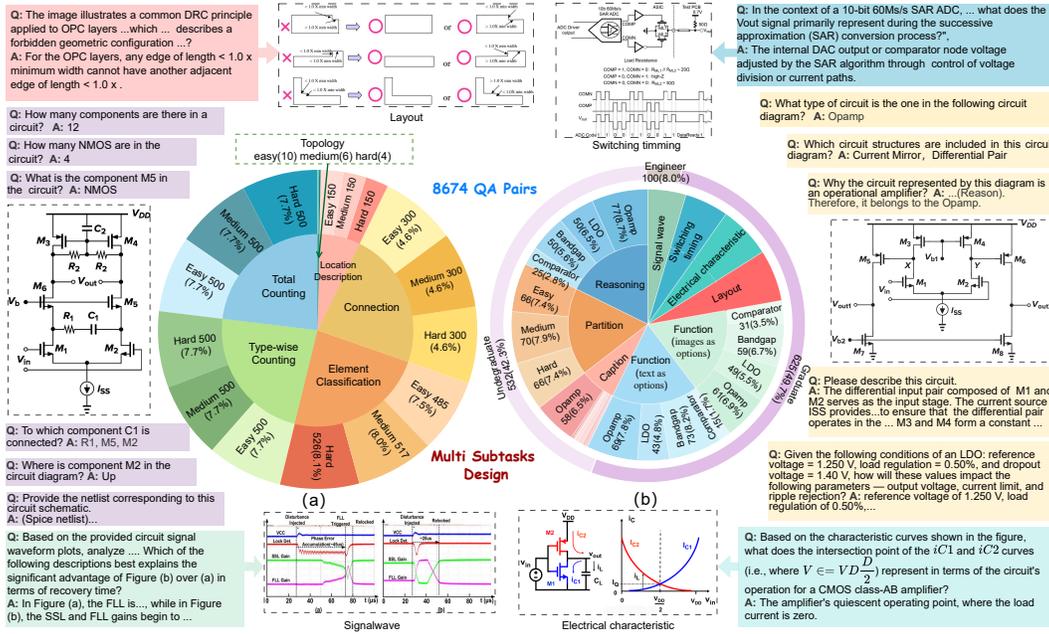
### 3.2 EVALUATION

The goal of AMSbench is to thoroughly evaluate MLLMs on the potential applications and tasks in the AMS circuit domain, as shown in Fig. 1. For the design of specific problems, we develop a multi-



The **analysis** tasks in AMSbench primarily assess the MLLMs’ comprehension of circuit schematics. This includes recognizing and analyzing the functions of circuits, as well as identifying key functional building blocks within them, as illustrated in Fig. 4. Beyond schematic understanding, the analysis tasks also cover other critical aspects of circuit design, such as interpreting signal waveforms, evaluating switching timing, and analyzing layout-related information. Additionally, we evaluate the understanding of AMS circuits, such as trade-offs between different circuit performance metrics by both LLMs and MLLMs. Accurately analyzing a circuit and its corresponding performance metrics is the foundation for ensuring accurate and effective circuit design.

The **design** tasks in our study consider both circuit design and testbench design, as shown in Fig. 5. Proper circuit design ensures that the functionality meets specifications, while effective testbench design guarantees that the circuit’s performance can be accurately measured and validated. These two tasks are central to the AI-driven automation of AMS circuit design. In setting up the circuit design tasks, we adopt and expand upon the benchmark established by AnalogCoder (Lai et al., 2025).

**Difficulty Levels** We classify the questions into three difficulty levels. Specifically, for the **perception** task, we categorize the difficulty based on the number of elements in the circuit: simple (num < 9), medium (9 < num < 16), and difficult (num > 16). For circuit functionality **analysis**, we classify the problems according to the circuit type and group them into two levels based on their appearance in educational stages: undergraduate and graduate levels. For testing the trade-offs between circuit performances, we assign a classification suitable for engineers. For the **design** task, we classify the circuits based on their complexity into three levels: simple, complex, and system-level circuits.

Table 2: Circuit design tasks. Number of (simple / complex / system-level) tasks are shown for each circuit type.

Circuit Type	# of Tasks	Circuit Type	# of Tasks	Circuit Type	# of Tasks	Circuit Type	# of Tasks
Amplifier	7 / 0 / 0	Oscillator	0 / 2 / 0	Subtractor	0 / 1 / 0	LDO	0 / 1 / 0
Inverter	2 / 0 / 0	Integrator	0 / 1 / 0	Schmitt trigger	0 / 1 / 0	Comparator	0 / 1 / 0
Current mirror	2 / 0 / 0	Differentiator	0 / 1 / 0	VCO	0 / 1 / 0	PLL	0 / 0 / 1
Op-amp	2 / 2 / 0	Adder	0 / 1 / 0	Bandgap	0 / 1 / 0	SAR-ADC	0 / 0 / 1

Table 3: Testbench design tasks with number of metrics required per testbench suite.

ID	Circuit Type	# of Metrics	ID	Circuit Type	# of Metrics	ID	Circuit Type	# of Metrics
1	Cross-coupled differential amplifier	7	5	PLL	2	9	Unit capacitor	1
2	Comparator	2	6	MOS_Ron	1	10	Folded cascode OTA	5
3	Bootstrap	1	7	LDO	7	11	SAR-ADC	1
4	Telescopic cascode OTA	7	8	VCO	2	12	Bandgap	4

### 3.3 AMSBENCH STATISTICS

Fig. 4(a) illustrates the subtasks involved in the perception task along with the number of questions at varying difficulty levels. Fig. 4(b) presents statistical information for the analysis task and its various subtasks. The VQA tasks focus on evaluating the MLLM’s ability to interpret circuit-related images, while the TQA tasks assess the model’s understanding of circuit knowledge and its awareness of performance trade-offs. Table 2 and 25 present an overview of the design tasks for circuits and testbenches, respectively. For the circuit design section, we incorporated the benchmarks provided by AnalogCoder (Lai et al., 2025) and further extended them with additional circuit tasks, including system-level circuit design. The testbench design tasks address a notable gap in the current community by introducing a previously underexplored category.

## 4 EXPERIMENTS

### 4.1 MODELS

We perform experiments on mainstream closed-source MLLMs: GPT-4o (Hurst et al., 2024), Grok-3 (gro, 2025), Gemini-2.5-pro (Team et al., 2023), Claude3.7 sonnet (Anthropic, 2024), Doubao-1.5-vision-pro-32k (Guo et al., 2025b), and powerful open-source models: Kimi-VL (Team et al., 2025), Qwen2.5-VL 72B (Yang et al., 2024a), DeepSeek-R1 (Guo et al., 2025a). We evaluate both TQA tasks on all models, and VQA tasks on all models except DeepSeek-R1. We use all open-source models with default parameters and deploy on up to 8 A100 GPUs.

## 4.2 METRICS

For multiple-choice questions, we adopt accuracy (ACC) as the evaluation metric. For multiple-selection questions, we use the F1 score. For netlist recognition tasks, we define a Netlist Edit Distance (NED) as the evaluation metric, with the calculation procedure illustrated in Fig. 6. The NED for each schematic image is normalized as shown in (1):

$$\text{NED}_{norm} = \frac{|\text{GT} \cup \text{Pred}| - |\text{GT} \cap \text{Pred}|}{|\text{GT}|} \quad (1)$$

For evaluating the circuit design tasks, we use  $\text{pass}@k$  as the primary metric to measure the success rate of model-generated circuits.  $\text{Syntax}@k$  and  $\text{Metric}@k$  are employed to evaluate the generated testbenches.  $\text{Syntax}@k$  examines the presence of syntactic errors that hinder simulation, and  $\text{Metric}@k$  verifies the functional correctness of the corresponding test circuits.

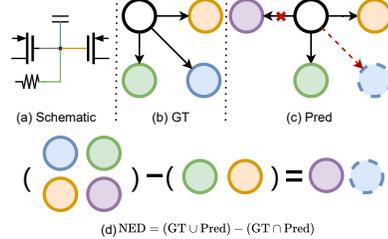


Figure 6: Edit distance computation between the GT and the predicted netlist.

## 4.3 EXPERIMENTAL RESULTS

**Perception Tasks:** Table 4 presents the models’ performance on fundamental circuit schematic recognition tasks. Specifically, component counting and classification, both of which are essential for accurate netlist extraction. Gemini achieves the best overall results. However, due to the complexity and diversity of component types, the models show limitations in accurate counting. For element type classification, Gemini performs well, reaching 94% accuracy. Among open-source models, Qwen2.5-VL achieves 86%, suggesting that open-source models still have room for improvement in component type recognition.

The lower part of Table 4 presents the accuracy of MLLMs in identifying inter-device connectivity. While the models can produce reasonably accurate predictions for local connections, they fall short in reconstructing the complete netlist. Even netlists produced by the best-performing model, Gemini, require substantial modifications to align with the ground truth. Closed-source models perform significantly better on these tasks, whereas Kimi-VL fail to produce outputs in the correct format.

Table 4: Comprehensive comparison of models across perception tasks and circuit interconnect recognition. Abbreviations adopted: Ele. Cls = Element Classification, Loc. Desc = Location Description, Conn. Judg = Connection Judgment, Conn. Ident = Connection Identification.

Models	Total Counting	Total Counting	Type Counting	Type Counting	Ele. Cls
	ACC (↑)	MSE (↓)	ACC (↑)	MSE (↓)	ACC (↑)
Gemini-2.5-pro	<b>0.65</b>	<b>10.02</b>	<b>0.64</b>	<b>13.41</b>	<b>0.94</b>
GPT-4o	0.51	19.05	0.54	28.18	0.91
Claude-3.7-sonnet	0.36	18.38	0.55	24.18	0.83
Grok-3	0.22	60.71	0.50	26.48	0.84
Doubao-1.5-vision-pro	0.24	38.13	0.51	24.76	0.93
Kimi-VL-A3B	0.15	49.19	0.44	34.96	0.66
Qwen2.5-VL-72B	0.43	19.59	0.49	18.59	0.86
Models	Loc. Desc	Conn. Judg	Conn. Ident	Topology	–
	ACC (↑)	ACC (↑)	F1 (↑)	NED (↓)	–
Gemini-2.5-pro	<b>0.61</b>	<b>0.85</b>	<b>0.88</b>	<b>0.91</b>	–
GPT-4o	0.37	0.73	0.65	1.40	–
Claude-3.7-sonnet	0.48	0.76	0.71	1.65	–
Grok-3	0.50	0.70	0.65	1.84	–
Doubao-1.5-vision-pro	0.45	0.76	0.64	1.57	–
Kimi-VL-A3B	0.31	0.53	0.53	–	–
Qwen2.5-VL-72B	0.56	0.77	0.52	2.38	–

**Analysis Tasks:** Table 5 summarizes the models’ capabilities of analyzing AMS circuits. In schematic interpretation (*Reasoning, Partition, Caption, Function*), different MLLMs exhibit distinct

Table 5: Comparison of models on analysis tasks

Models	Reasoning	Signal wave	Switching timing	Electrical characteristic	Layout
	ACC (↑)	ACC (↑)	ACC (↑)	ACC (↑)	ACC (↑)
Gemini-2.5-pro	<b>0.92</b>	<b>0.94</b>	<b>0.96</b>	<b>0.92</b>	0.75
GPT-4o	0.77	0.74	0.79	0.80	0.65
Claude-3.7-sonnet	0.91	0.86	0.87	<b>0.92</b>	<b>0.83</b>
Grok-3	0.61	0.84	0.85	0.82	0.63
Doubao-1.5-vision-pro	0.83	0.89	0.83	0.85	0.75
Kimi-VL-A3B	0.74	0.64	0.59	0.53	0.58
Qwen2.5-VL-72B	0.82	0.77	0.82	0.85	0.60
Models	Partition	Caption	Function (text)	Function (image)	TQA
	F1 (↑)	ACC (↑)	ACC (↑)	ACC (↑)	ACC (↑)
Gemini-2.5-pro	<b>0.80</b>	0.70	<b>0.95</b>	<b>0.94</b>	0.72
GPT-4o	0.57	0.61	0.93	0.89	<b>0.78</b>
Claude-3.7-sonnet	0.64	<b>0.98</b>	0.88	0.74	0.74
Grok-3	0.59	0.41	0.77	0.22	0.74
Doubao-1.5-vision-pro	0.60	0.70	0.94	0.93	0.76
Kimi-VL-A3B	0.25	0.71	0.59	0.28	0.59
Qwen2.5-VL-72B	0.45	0.78	0.78	0.85	0.69

strengths: Gemini demonstrates the highest accuracy in identifying and analyzing functional building blocks, while Claude-Sonnet provides more accurate overall descriptions of circuit behavior. Gemini also demonstrated strong performance on other circuit-related images. Table 16 shows that current models can achieve relatively high accuracy in analyzing circuit knowledge designed for undergraduate and graduate education. However, they perform poorly in understanding the trade-offs between circuit performance metrics commonly encountered in industry. Even the best-performing model, GPT-4o, only achieves 58% accuracy, indicating that LLMs currently lack a clear understanding of the expected performance characteristics of each circuit in the design process.

**Design Tasks:** Table 6 shows the performance of the models in circuit design and testbench design tasks. For circuit design, Grok-3 and Claude-Sonnet achieve the best results. However, for testbench design, none of the current models can directly generate syntactically correct testbenches, with only occasionally exceptions of GPT-4o. One possible reason is that the current pretraining data lacks sufficient testbench-related knowledge. Additionally, the metrics that need to be measured vary across different circuits, making testbench generation highly challenging.

Table 6: Comparison of models and circuit design and testbench design tasks. The data presents the average results of all the circuits listed in Table 2. Detailed results are available in the appendix in Tables 18-27. *Syntax*: generated testbench is syntactically correct to run simulation. *Metric*: generated testbench is topologically and parametrically correct and produces the correct performance metric.

Model	Circuit Design			Testbench Design	
	Pass@3	Pass@5	Pass@10	Syntax@5	Metric@5
Gemini-2.5-pro	0.57	0.54	0.43	0	0
GPT-4o	0.47	0.49	0.42	<b>0.084</b>	0
Claude-3.7-sonnet	0.63	<b>0.64</b>	0.50	0	0
Grok-3	<b>0.65</b>	0.54	<b>0.61</b>	0	0
Doubao-1.5-vision-pro	0.45	0.24	0.15	0	0
Qwen2.5-VL-72B	0.47	0.41	0.33	0	0
Kimi-VL-A3B	0.41	0.25	0.13	0	0
DeepSeek-R1	0.55	0.51	0.45	-	-

## 5 CHALLENGES AND POSSIBLE IMPROVEMENTS

**Challenges of MLLMs in the interpretation of circuit-related images.** Existing MLLMs remain limited in accurately interpreting circuit schematics. Although some models can capture localized connectivity patterns, their performance degrades when extracting complete netlists. A key challenge lies in the domain gap between circuit schematics and the natural images typically used in MLLM pretraining, which leads to misclassification of components—for example, failing to distinguish

---

between PMOS and NMOS transistors. In addition, MLLMs often struggle to correctly associate pins and ports with their parent components, resulting in connectivity errors.

To enhance model’s recognition capability, one approach is to combine MLLMs with specialized vision models such as object detection (Bhandari et al., 2025) or OCR, which improves baseline component recognition but does not fundamentally advance the MLLMs themselves. A more promising direction is the construction of large-scale circuit-specific multimodal datasets, enabling continual pretraining and post-training. We have conducted experiments on component grounding, and the results show that MLLMs trained with such data exhibit improved perception of circuit schematics, as illustrated in the Fig. 37.

**Hallucinations in circuit analysis.** In circuit analysis tasks, one major reason for poor performance lies in the inability of the vision encoder to accurately and comprehensively embed visual information, as discussed earlier. Another reason is the insufficient circuit-related knowledge of the models themselves, which is also evident in text-only evaluation tasks. In existing works that combine LLMs with AMS circuit design, LLMs are typically employed as analysis tools for downstream design (Yin et al., 2024; Wei et al., 2025). A model with strong circuit analysis capabilities can significantly reduce the parameter search space and partition the circuit into macros, thereby enabling efficient layout generation. However, current models still lack the ability to accurately quantify the trade-offs between circuit performance metrics, which limits their capability to recommend appropriate circuit topologies under given target specifications.

One possible solution to enhance model performance in analysis tasks is to construct high-quality datasets for training. However, due to the scarcity of documents related to circuit analysis and design, training outcomes cannot be guaranteed. Another promising approach is to adopt Retrieval-Augmented Generation (RAG), which dynamically collects high-quality multimodal data, cleans it, and stores it in a vector database. During circuit analysis, the model can then retrieve relevant knowledge from this database to support its reasoning and responses.

**Struggles in AMS circuit design.** Applying LLMs to AMS design involves three key stages: topology design, testbench generation, and circuit sizing. End-to-end generation of directly usable circuits remains highly challenging. For **topology design**, the primary requirement is to generate novel yet functional circuits. Possible solutions include continual training of LLMs, combined with prompt engineering. However, for complex and system-level circuits, directly producing a correct design remains extremely challenging, as illustrated in Fig. 35. A divide-and-conquer strategy, where submodules are designed and validated individually before integration, offers a more feasible path. For **testbench generation**, the process is relatively standardized. Although it is still difficult to directly generate usable testbenches, one feasible approach is leveraging predefined libraries and letting LLMs perform targeted modifications. For **circuit sizing**, it is extremely difficult for an LLM to directly produce circuits with desired sizing. One potential solution is to combine LLMs with traditional black-box optimization algorithms, embedding domain knowledge into the optimization process to accelerate convergence. Another promising approach is the use of multi-agent systems, where LLMs emulate the workflow of human engineers. The former approach enables exploration of a broader design space, albeit at the expense of efficiency, while the latter offers improved interpretability and transparency, but the accumulation of hallucinations from each agent may negatively affect the final performance.

## 6 CONCLUSION

This paper introduces AMSbench, a benchmark designed to evaluate the capabilities of MLLMs in the AMS circuit domain. The benchmark comprehensively assesses model performance across three key dimensions—schematic perception, circuit analysis, and circuit design—covering a variety of tasks. AMSbench reveals significant limitations in current MLLMs, especially in schematic perception and complex circuit design. While certain models perform adequately in basic component recognition and simpler circuit analysis tasks, they notably struggle with advanced tasks, including accurate schematic interpretation and system-level circuit design. Given the increasing interest in applying MLLMs to automate AMS design processes, AMSbench provides an essential evaluation framework, establishing a robust foundation for future advancements in this field. Achieving high-performance scores on AMSbench would signify substantial progress and tangible benefits in the automation

---

of AMS circuit design. Future research will prioritize the expansion of datasets to enhance the robustness and generalizability of multimodal models. It will investigate advanced methodologies, such as RAG and RLHF, to augment design capabilities.

---

## REFERENCES

- Grok 3 beta—the age of reasoning agents. <https://x.ai/blog/grok-3>, 2025. Accessed: 2025-05-14.
- Phillip E Allen and Douglas R Holberg. *CMOS Analog Circuit Design*. Elsevier, 2011.
- Anthropic. Introducing claude 3.7 sonnet. <https://www.anthropic.com/news/>, 2024. Accessed: 2025-05-14.
- Jitendra Bhandari, Vineet Bhat, Yuheng He, Hamed Rahmani, Siddharth Garg, and Ramesh Karri. Masala-chai: A large-scale spice netlist dataset for analog circuits by harnessing ai, 2025. URL <https://arxiv.org/abs/2411.14299>.
- Jason Blocklove, Siddharth Garg, Ramesh Karri, and Hammond Pearce. Chip-chat: Challenges and opportunities in conversational hardware design. In *2023 ACM/IEEE 5th Workshop on Machine Learning for CAD (MLCAD)*, pp. 1–6. IEEE, 2023.
- Jayeeta Chaudhuri, Dhruv Thapar, Arjun Chaudhuri, Farshad Firouzi, and Krishnendu Chakrabarty. SPICED+: Syntactical Bug Pattern Identification and Correction of Trojans in A/MS Circuits Using LLM-Enhanced Detection. *IEEE Transactions on Very Large Scale Integration (VLSI) Systems*, 2025.
- Zihao Chen, Jiangli Huang, Yiting Liu, Fan Yang, Li Shang, Dian Zhou, and Xuan Zeng. Artisan: Automated Operational Amplifier Design via Domain-specific Large Language Model. In *2024 61th ACM/IEEE Design Automation Conference (DAC)*, pp. 1–6, 2024.
- Can Cui, Yunsheng Ma, Xu Cao, Wenqian Ye, Yang Zhou, Kaizhao Liang, Jintai Chen, Juanwu Lu, Zichong Yang, Kuei-Da Liao, et al. A Survey on Multimodal Large Language Models for Autonomous Driving. In *Proceedings of the IEEE/CVF Winter Conference on Applications of Computer Vision*, pp. 958–979, 2024.
- Wenji Fang, Jing Wang, Yao Lu, Shang Liu, Yuchao Wu, Yuzhe Ma, and Zhiyao Xie. A survey of circuit foundation model: Foundation ai models for vlsi circuit design and eda. *arXiv preprint arXiv:2504.03711*, 2025.
- Yonggan Fu, Yongan Zhang, Zhongzhi Yu, Sixu Li, Zhifan Ye, Chaojian Li, Cheng Wan, and Yingyan Celine Lin. Gpt4aigchip: Towards next-generation ai accelerator design automation via large language models. In *2023 IEEE/ACM International Conference on Computer Aided Design (ICCAD)*, pp. 1–9. IEEE, 2023.
- Jian Gao, Weidong Cao, Junyi Yang, and Xuan Zhang. AnalogGenie: A Generative Engine for Automatic Discovery of Analog Circuit Topologies. *arXiv preprint arXiv:2503.00205*, 2025.
- Paul R Gray, Paul J Hurst, Stephen H Lewis, and Robert G Meyer. *Analysis and Design of Analog Integrated Circuits*. John Wiley & Sons, 2009.
- Daya Guo, Dejian Yang, Haowei Zhang, Junxiao Song, Ruoyu Zhang, Runxin Xu, Qihao Zhu, Shirong Ma, Peiyi Wang, Xiao Bi, et al. Deepseek-r1: Incentivizing reasoning capability in llms via reinforcement learning. *arXiv preprint arXiv:2501.12948*, 2025a.
- Dong Guo, Faming Wu, Feida Zhu, Fuxing Leng, Guang Shi, Haobin Chen, Haoqi Fan, Jian Wang, Jianyu Jiang, Jiawei Wang, et al. Seed1. 5-VL Technical Report. *arXiv preprint arXiv:2505.07062*, 2025b.
- Yunzhuo Hao, Jiawei Gu, Huichen Will Wang, Linjie Li, Zhengyuan Yang, Lijuan Wang, and Yu Cheng. Can MLLMs Reason in Multimodality? EMMA: An Enhanced MultiModal Reasoning Benchmark. *arXiv preprint arXiv:2501.05444*, 2025.
- Aaron Hurst, Adam Lerer, Adam P Goucher, Adam Perelman, Aditya Ramesh, Aidan Clark, AJ Ostrow, Akila Welihinda, Alan Hayes, Alec Radford, et al. Gpt-4o system card. *arXiv preprint arXiv:2410.21276*, 2024.

- 
- Yao Lai, Sungyoung Lee, Guojin Chen, Souradip Poddar, Mengkang Hu, David Z Pan, and Ping Luo. Analogocoder: Analog circuit design via training-free code generation. In *Proceedings of the AAAI Conference on Artificial Intelligence*, volume 39, pp. 379–387, 2025.
- Chengjie Liu, Weiyu Chen, Anlan Peng, Yuan Du, Li Du, and Jun Yang. AmpAgent: An LLM-based Multi-Agent System for Multi-stage Amplifier Schematic Design from Literature for Process and Performance Porting. *arXiv preprint arXiv:2409.14739*, 2024.
- Mingjie Liu, Nathaniel Pinckney, Brucek Khailany, and Haoxing Ren. VerilogEval: Evaluating Large Language Models for Verilog Code Generation. In *2023 IEEE/ACM International Conference on Computer-Aided Design (ICCAD)*, 2023.
- Pan Lu, Hritik Bansal, Tony Xia, Jiacheng Liu, Chunyuan Li, Hannaneh Hajishirzi, Hao Cheng, Kai-Wei Chang, Michel Galley, and Jianfeng Gao. MathVista: Evaluating Math Reasoning in Visual Contexts with GPT-4V, Bard, and Other Large Multimodal Models. *CoRR*, 2023.
- Yao Lu, Shang Liu, Qijun Zhang, and Zhiyao Xie. RTLLM: An Open-Source Benchmark for Design RTL Generation with Large Language Model. In *2024 29th Asia and South Pacific Design Automation Conference (ASP-DAC)*, pp. 722–727. IEEE, 2024.
- Long Ouyang, Jeffrey Wu, Xu Jiang, Diogo Almeida, Carroll Wainwright, Pamela Mishkin, Chong Zhang, Sandhini Agarwal, Katarina Slama, Alex Ray, et al. Training language models to follow instructions with human feedback. *Advances in neural information processing systems*, 35:27730–27744, 2022.
- Jingyu Pan, Guanglei Zhou, Chen-Chia Chang, Isaac Jacobson, Jiang Hu, and Yiran Chen. A Survey of Research in Large Language Models for Electronic Design Automation. *ACM Transactions on Design Automation of Electronic Systems*, 2025.
- Behzad Razavi. *Design of Analog CMOS Integrated Circuits*. McGraw-Hill Higher Education, 2005.
- Willy M Sansen. *Analog Design Essentials*, volume 859. Springer Science & Business Media, 2007.
- Yichen Shi, Zhuofu Tao, Yuhao Gao, Tianjia Zhou, Cheng Chang, Yaxing Wang, Bingyu Chen, Genhao Zhang, Alvin Liu, Zhiping Yu, et al. AMSnet-KG: A Netlist Dataset for LLM-based AMS Circuit Auto-Design Using Knowledge Graph RAG. *arXiv preprint arXiv:2411.13560*, 2024.
- Zhuofu Tao, Yichen Shi, Yiru Huo, Rui Ye, Zonghang Li, Li Huang, Chen Wu, Na Bai, Zhiping Yu, Ting-Jung Lin, et al. Amsnet: Netlist dataset for ams circuits. In *2024 IEEE LLM Aided Design Workshop (LAD)*, pp. 1–5. IEEE, 2024.
- Gemini Team, Rohan Anil, Sebastian Borgeaud, Jean-Baptiste Alayrac, Jiahui Yu, Radu Soriccut, Johan Schalkwyk, Andrew M Dai, Anja Hauth, Katie Millican, et al. Gemini: a family of highly capable multimodal models. *arXiv preprint arXiv:2312.11805*, 2023.
- Kimi Team, Angang Du, Bohong Yin, Bowei Xing, Bowen Qu, Bowen Wang, Cheng Chen, Chenlin Zhang, Chenzhuang Du, Chu Wei, et al. Kimi-VL Technical Report. *arXiv preprint arXiv:2504.07491*, 2025.
- Bin Wang, Chao Xu, Xiaomeng Zhao, Linke Ouyang, Fan Wu, Zhiyuan Zhao, Rui Xu, Kaiwen Liu, Yuan Qu, Fukai Shang, et al. Mineru: An open-source solution for precise document content extraction, 2024. URL <https://arxiv.org/abs/2409.18839>.
- Ziming Wei, Zichen Kong, Yuan Wang, David Z Pan, and Xiyuan Tang. Toposizing: An llm-aided framework of topology-based understanding and sizing for ams circuits. *arXiv preprint arXiv:2509.14169*, 2025.
- Zheyu Yan, Yifan Qin, Xiaobo Sharon Hu, and Yiyu Shi. On the viability of using llms for sw/hw co-design: An example in designing cim dnn accelerators. In *2023 IEEE 36th International System-on-Chip Conference (SOCC)*, pp. 1–6. IEEE, 2023.
- An Yang, Baosong Yang, Beichen Zhang, Binyuan Hui, Bo Zheng, Bowen Yu, Chengyuan Li, Dayiheng Liu, Fei Huang, Haoran Wei, et al. Qwen2. 5 technical report. *arXiv preprint arXiv:2412.15115*, 2024a.

- 
- An Yang, Beichen Zhang, Binyuan Hui, Bofei Gao, Bowen Yu, Chengpeng Li, Dayiheng Liu, Jianhong Tu, Jingren Zhou, Junyang Lin, et al. Qwen2. 5-Math Technical Report: Toward Mathematical Expert Model via Self-Improvement. *arXiv preprint arXiv:2409.12122*, 2024b.
- Yuxuan Yin, Yu Wang, Boxun Xu, and Peng Li. ADO-LLM: Analog Design Bayesian Optimization with In-Context Learning of Large Language Models. *arXiv preprint arXiv:2406.18770*, 2024.
- Xiang Yue, Yuansheng Ni, Tianyu Zheng, Kai Zhang, Ruoqi Liu, Ge Zhang, Samuel Stevens, Dongfu Jiang, Weiming Ren, Yuxuan Sun, et al. MMMU: A Massive Multi-Discipline Multimodal Understanding and Reasoning Benchmark for Expert AGI. In *Proceedings of the IEEE/CVF Conference on Computer Vision and Pattern Recognition*, pp. 9556–9567, 2024.
- Renrui Zhang, Dongzhi Jiang, Yichi Zhang, Haokun Lin, Ziyu Guo, Pengshuo Qiu, Aojun Zhou, Pan Lu, Kai-Wei Chang, Yu Qiao, et al. MathVerse: Does Your Multi-modal LLM Truly See the Diagrams in Visual Math Problems? In *European Conference on Computer Vision*, pp. 169–186. Springer, 2024.
- Chenchen Zhao, Zhengyuan Shi, Xiangyu Wen, Chengjie Liu, Yi Liu, Yunhao Zhou, Yuxiang Zhao, Hefei Feng, Yanan Zhu, Gwok-Waa Wan, et al. Mmcircuiteval: A comprehensive multimodal circuit-focused benchmark for evaluating llms. *arXiv preprint arXiv:2507.19525*, 2025.
- Li Zhong and Zilong Wang. Can LLM Replace Stack Overflow? A Study on Robustness and Reliability of Large Language Model Code Generation. In *Proceedings of the AAAI Conference on Artificial Intelligence*, volume 38, pp. 21841–21849, 2024.

## A THE USE OF LARGE LANGUAGE MODELS (LLMs)

This research employed multiple large language models as test subjects for benchmark development and validation. Additionally, LLMs were used minimally for sentence-level language refinement and polishing to improve clarity of expression. All core research contributions, methodology, and analysis were conducted independently by the authors without AI assistance.

## B DETAILED EXPERIMENT RESULTS

### B.1 RESULTS OF PERCEPTION TASKS

Models	Metric	Counting Task							
		Total Counting				Type-wise Counting			
		Easy	Medium	Hard	Total	Easy	Medium	Hard	Total
Gemini-2.5-pro	ACC ( $\uparrow$ )	<b>0.88</b>	<b>0.65</b>	<b>0.45</b>	<b>0.65</b>	<b>0.83</b>	0.63	0.46	0.64
	MSE ( $\downarrow$ )	<b>0.39</b>	<b>2.30</b>	<b>27.36</b>	<b>10.02</b>	<b>0.67</b>	<b>3.75</b>	35.81	13.41
GPT-4o	ACC ( $\uparrow$ )	0.75	0.51	0.26	0.51	0.76	0.57	0.30	0.54
	MSE ( $\downarrow$ )	0.80	2.63	53.72	19.05	2.15	6.96	75.44	28.18
Claude-3.7-sonnet	ACC ( $\uparrow$ )	0.72	0.27	0.01	0.36	0.73	0.57	<b>0.35</b>	<b>0.55</b>
	MSE ( $\downarrow$ )	0.56	3.63	50.96	18.38	2.29	<b>6.67</b>	63.57	24.18
Grok-3	ACC ( $\uparrow$ )	0.47	0.14	0.04	0.22	0.70	0.53	0.27	0.50
	MSE ( $\downarrow$ )	3.58	21.50	157.05	60.71	2.49	6.92	68.51	26.48
Doubao-1.5-vision-pro	ACC ( $\uparrow$ )	0.60	0.10	0.01	0.24	0.71	0.53	0.30	0.51
	MSE ( $\downarrow$ )	0.67	5.93	107.78	38.13	2.56	9.14	<b>62.59</b>	<b>24.76</b>
Kimi-VL-A3B	ACC ( $\uparrow$ )	0.23	0.13	0.08	0.15	0.63	0.46	0.23	0.44
	MSE ( $\downarrow$ )	15.68	28.04	103.86	49.19	2.86	13.44	94.38	34.96
Qwen2.5-VL-72B	ACC ( $\uparrow$ )	0.67	0.42	0.21	0.43	0.68	0.47	0.31	0.49
	MSE ( $\downarrow$ )	1.09	3.98	<b>53.90</b>	<b>19.59</b>	1.87	<b>6.55</b>	<b>47.35</b>	<b>18.59</b>

Table 7: Counting Task Performance Across Different Models

Models	Element Classification Task (ACC $\uparrow$ )			
	Easy	Medium	Hard	Total
Gemini-2.5-pro	<b>0.96</b>	<b>0.94</b>	<b>0.91</b>	<b>0.94</b>
GPT-4o	0.93	0.93	0.88	0.91
Claude-3.7-sonnet	0.90	0.87	0.84	0.83
Grok-3	0.84	0.84	0.83	0.84
Doubao-1.5-vision-pro	0.94	0.93	<b>0.91</b>	0.93
Kimi-VL-A3B	0.69	0.65	0.63	0.66
Qwen2.5-VL-72B	0.88	0.86	0.83	0.86

Table 8: Element Classification Task Performance Across Different Models (in decimals)

Models	Metric	Interconnect Perception Task							
		Connection Judgment				Connection Identification			
		Easy	Medium	Hard	Total	Easy	Medium	Hard	Total
Gemini-2.5-pro	ACC ( $\uparrow$ )	<b>0.86</b>	<b>0.83</b>	<b>0.85</b>	<b>0.85</b>	<b>0.78</b>	<b>0.51</b>	<b>0.50</b>	<b>0.60</b>
	F1 ( $\uparrow$ )	-	-	-	-	<b>0.93</b>	<b>0.86</b>	<b>0.86</b>	<b>0.88</b>
GPT-4o	ACC ( $\uparrow$ )	0.74	0.71	0.74	0.73	0.27	0.12	0.10	0.16
	F1 ( $\uparrow$ )	-	-	-	-	0.74	0.61	0.59	0.65
Claude-3.7-sonnet	ACC ( $\uparrow$ )	0.74	0.76	0.77	0.76	0.36	0.25	0.22	0.27
	F1 ( $\uparrow$ )	-	-	-	-	0.74	0.71	0.68	0.71
Grok-3	ACC ( $\uparrow$ )	0.72	0.72	0.67	0.70	0.25	0.16	0.13	0.18
	F1 ( $\uparrow$ )	-	-	-	-	0.70	0.63	0.62	0.65
Doubao-1.5-vision-pro	ACC ( $\uparrow$ )	0.78	0.74	0.77	0.76	0.30	0.13	0.14	0.19
	F1 ( $\uparrow$ )	-	-	-	-	0.72	0.60	0.59	0.64
Kimi-VL-A3B	ACC ( $\uparrow$ )	0.55	0.54	0.51	0.53	0.13	0.09	0.10	0.10
	F1 ( $\uparrow$ )	-	-	-	-	0.57	0.51	0.52	0.53
Qwen2.5-VL-72B	ACC ( $\uparrow$ )	0.75	0.78	0.77	0.77	0.20	0.10	0.13	0.14
	F1 ( $\uparrow$ )	-	-	-	-	0.56	0.48	0.53	0.52

Table 9: Interconnect Perception Task Performance Across Different Models

Models	Location Description Task (ACC $\uparrow$ )			
	Easy	Medium	Hard	Total
Gemini-2.5-pro	<b>0.61</b>	<b>0.60</b>	<b>0.61</b>	<b>0.61</b>
GPT-4o	0.44	0.31	0.37	0.37
Claude-3.7-sonnet	0.49	0.45	0.50	0.48
Grok-3	0.45	0.55	0.49	0.50
Doubao-1.5-vision-pro	0.51	0.47	0.38	0.45
Kimi-VL-A3B	0.32	0.33	0.27	0.31
Qwen2.5-VL-72B	0.57	0.59	0.53	0.56

Table 10: Location Description Task Performance Across Different Models

Models	Topology Generation Task (NED $\downarrow$ )			
	Easy	Medium	Hard	Total
Gemini-2.5-pro	<b>0.73</b>	<b>0.95</b>	<b>1.34</b>	<b>0.91</b>
GPT-4o	1.31	1.56	1.46	1.40
Claude-3.7-sonnet	1.72	1.64	1.51	1.65
Grok-3	2.08	1.71	1.37	1.84
Doubao-1.5-vision-pro	1.54	1.52	1.68	1.57
Kimi-VL-A3B	-	-	-	-
Qwen2.5-VL-72B	2.65	2.14	1.95	2.38

Table 11: Topology Generation Task Performance Across Different Models

## B.2 RESULTS OF ANALYSIS TASKS

Models	Function Identification Task (ACC $\uparrow$ )	
	Function (text as options)	Function (image as options)
Gemini-2.5-pro	<b>0.95</b>	<b>0.94</b>
GPT-4o	0.93	0.89
Claude-3.7-sonnet	0.88	0.74
Grok-3	0.77	0.22
Doubao-1.5-vision-pro	0.94	0.93
Kimi-VL-A3B	0.59	0.28
Qwen2.5-VL-72B	0.78	0.85

Table 12: Function Identification Task Performance Across Different Models

Models	Circuit Partition Task							
	Easy		Medium		Hard		Overall	
	ACC $\uparrow$	F1 $\uparrow$	ACC $\uparrow$	F1 $\uparrow$	ACC $\uparrow$	F1 $\uparrow$	ACC $\uparrow$	F1 $\uparrow$
Gemini-2.5-pro	<b>0.52</b>	<b>0.81</b>	<b>0.33</b>	<b>0.81</b>	<b>0.20</b>	<b>0.78</b>	<b>0.35</b>	<b>0.80</b>
GPT-4o	0.21	0.55	0.07	0.59	0.06	0.57	0.11	0.57
Claude-3.7-sonnet	0.29	0.66	0.11	0.62	0.08	0.62	0.16	0.64
Grok-3	0.26	0.59	0.17	0.63	0.03	0.56	0.15	0.59
Doubao-1.5-vision-pro	0.26	0.63	0.04	0.61	0.03	0.54	0.11	0.60
Kimi-VL-A3B	0.03	0.29	0.00	0.00	0.00	0.00	0.00	0.28
Qwen2.5-VL-72B	0.06	0.44	0.00	0.49	0.00	0.43	0.02	0.45

Table 13: Circuit Partition Task Performance Across Different Models

Models	Reasoning Task (ACC $\uparrow$ )			
	Op-amp	LDO	Bandgap	Comparator
Gemini-2.5-pro	0.94	0.90	0.88	<b>0.96</b>
GPT-4o	0.78	0.84	0.64	0.84
Claude-3.7-sonnet	<b>0.95</b>	<b>0.96</b>	0.78	<b>0.96</b>
Grok-3	0.60	0.72	0.52	0.60
Doubao-1.5-vision-pro	0.90	0.84	0.80	0.80
Kimi-VL-A3B	0.81	0.46	<b>0.86</b>	0.84
Qwen2.5-VL-72B	0.81	0.90	0.72	0.84

Table 14: Reasoning Task Performance Across Different Models

Models	Caption Generation Task(ACC ↑)		
	Undergraduate	Graduate	Total
Gemini-2.5-pro	0.63	0.72	0.70
GPT-4o	0.58	0.63	0.61
Claude-3.7-sonnet	<b>0.89</b>	<b>1.00</b>	<b>0.98</b>
Grok-3	0.21	0.47	0.41
Doubao-1.5-vision-pro	0.74	0.69	0.70
Kimi-VL-A3B	0.74	0.70	0.71
Qwen2.5-VL-72B	<b>0.89</b>	0.75	0.78

Table 15: Caption Generation Task Performance Across Different Models

Models	TQA Task(ACC ↑)			
	Undergraduate	Graduate	Engineer	Total
Gemini-2.5-pro	0.89	0.89	0.39	0.72
GPT-4o	0.88	0.88	<b>0.58</b>	<b>0.78</b>
Claude-3.7-sonnet	<b>0.90</b>	0.88	0.45	0.74
Grok-3	0.86	0.84	0.53	0.74
Doubao-1.5-vision-pro	0.88	0.88	0.52	0.76
Kimi-VL-A3B	0.80	0.82	0.16	0.59
Qwen2.5-VL-72B	0.85	0.85	0.37	0.69
DeepSeek-R1	0.89	<b>0.90</b>	<b>0.58</b>	0.77

Table 16: TQA Task Performance Across Different Models (Decimal Format)

### B.3 RESULTS OF DESIGN TASKS

#### B.3.1 CIRCUIT DESIGN TASK

<b>Id</b>	<b>Type</b>	<b>Circuit Description</b>	<b>Id</b>	<b>Type</b>	<b>Circuit Description</b>
1	Amplifier	Single-stage common-source amp. with R load	15	Op-amp	Telescopic cascode op-amp
2	Amplifier	3-stage common-source amp. with R load	16	Oscillator	RC phase-shift oscillator
3	Amplifier	Common-drain amp. with R load	17	Oscillator	A Wien bridge oscillator
4	Amplifier	Single-stage common-gate amp. with R load	18	Integrator	Op-amp integrator
5	Amplifier	Single-stage cascode amp. with R load	19	Differentiator	Op-amp differentiator
6	Inverter	NMOS inverter with R load	20	Adder	Op-amp adder
7	Inverter	Logical inverter with NMOS and PMOS	21	Subtractor	Op-amp subtractor
8	Current mirror	NMOS constant current source with R load	22	Schmitt trigger	Non-inverting Schmitt trigger
9	Amplifier	2-stage amp. with Miller compensation	23	VCO	Voltage-controlled oscillator
10	Amplifier	Common-source amp. with diode-connected load	24	Bandgap	A classic brokaw bandgap reference
11	Op-amp	Differential op-amp with current mirror load	25	Comparator	A low offset voltage dual comparator
12	Current mirror	Cascode current mirror	26	LDO	1A low dropout voltage regulator
13	Op-amp	Single-stage common-source op-amp with R loads	27	PLL	Phase-locked loop
14	Op-amp	2-stage differential op-amp with active loads	28	SAR-ADC	Successive approximation register ADC

Table 17: Circuit block library (two parallel lists), with column-specific background coloring (blue means simple, green means complex, red means system level)

<b>Models</b>	<b>1. Amplifier</b>			<b>2. Amplifier</b>			<b>3. Amplifier</b>			<b>4. Amplifier</b>		
	p@3	p@5	p@10									
Gemini-2.5-pro	1	1	1	1	1	1	0.67	0.67	0.67	1	1	1
Gpt-4o	1	1	1	1	1	1	0	1	1	0.33	0.33	0.33
Claude-3.7-sonnet	1	1	1	1	1	1	0.33	0.67	1	0.67	0.67	0.67
Grok-3	1	1	1	1	1	1	0	1	1	0.67	0.67	0.67
Doubao-1.5-vision-pro	0.67	0.67	0.67	0.43	0.43	0.43	0.33	0.33	0.33	0.13	0.13	0.13
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 18: Per-circuit pass@k scores (k = 3, 5, 10) for CKT1–CKT4 across multiple models

<b>Models</b>	<b>5. Amplifier</b>			<b>6. Inverter</b>			<b>7. Inverter</b>			<b>8. Current mirror</b>		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	1	1	1	1	1	1	1	1	1	1	1	1
GPT-4o	1	1	1	1	1	1	1	1	1	1	1	1
Claude-3.7-sonnet	1	1	1	1	1	1	1	1	1	1	1	1
Grok-3	1	1	1	1	1	1	1	1	1	1	1	1
Doubao-1.5-vision-pro	0.23	0.23	0.23	0.23	0.23	0.23	0.49	0.49	0.49	1	1	1
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 19: Per-circuit pass@k scores (k = 3, 5, 10) for CKT5–CKT8 across multiple models

Model	9. Amplifier			10. Amplifier			11. Op-amp			12. Current mirror		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	1	1	1	0.61	0.61	0.61	0.48	0.48	0.48	0.24	0.24	0.24
GPT-4o	1	1	1	0.43	0.43	0.43	0.22	0.22	0.22	0	0	0
Claude-3.7-sonnet	1	1	1	0.87	0.87	0.87	0.65	0.65	0.65	0.62	0.62	0.62
Grok-3	1	1	1	0.86	0.86	0.86	0.29	0.29	0.29	0.33	0.33	0.33
Doubao-1.5-vision-pro	0.27	0.27	0.27	0.61	0.61	0.61	0.33	0.33	0.33	0.31	0.31	0.31
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 20: Per-circuit pass@k scores (k = 3, 5, 10) for CKT9–CKT12 across multiple models

Model	13. Op-amp			14. Op-amp			15. Op-amp			16. Oscillator		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	0.43	0.43	0.43	1	1	1	0.33	0.4	0.1	0	0	0
GPT-4o	0.32	0.32	0.32	0.21	0.21	0.21	0	0.2	0.1	0.33	0.6	0.3
Claude-3.7-sonnet	1	1	1	0.71	0.71	0.71	1	1	0.9	0	0	0
Grok-3	0.69	0.69	0.69	0.89	0.89	0.89	1	1	1	0	0	0
Doubao-1.5-vision-pro	0.68	0.68	0.68	0	0	0	0.33	0.2	0.1	0.33	0.2	0.1
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 21: Per-circuit pass@k scores (k = 3, 5, 10) for CKT13–CKT16 across multiple models

Model	17. Oscillator			18. Integrator			19. Differentiator			20. Adder		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	0	0	0	0.33	0.4	0.1	0.2	0.1	0.33	0.4	0.1	0.33
GPT-4o	1	0.2	0.1	0.33	0.6	0.1	0.4	0.1	0	0.4	0.5	0.33
Claude-3.7-sonnet	0.33	1	0.3	0.33	0.2	0.1	0.33	0.2	0.1	1	0.6	0.1
Grok-3	0.33	0.6	0.3	0.67	0	0.3	0.67	0.8	0.1	0.33	0.4	0.2
Doubao-1.5-vision-pro	0.33	0.2	0.1	1	0.2	0.4	0.67	0.2	0.1	0.33	0.2	0.1
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 22: Per-circuit pass@k scores (k = 3, 5, 10) for CKT17–CKT20 across multiple models

Model	21. Subtractor			22. Schmitt trigger			23. VCO			24. Bandgap		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	0.4	0.1	0.33	0.33	0.4	0.1	0.67	1	0.9	0	0	0
GPT-4o	0.6	0.2	0.33	0.2	0.33	0.4	0.5	0.33	0.6	0	0	0
Claude-3.7-sonnet	1	0.8	0.2	0.33	0.4	0.1	0.33	0.2	0.2	0	0	0
Grok-3	0.33	0.2	1	0.33	0.2	0.1	0.6	0.5	0.33	0	0	0
Doubao-1.5-vision-pro	0.33	0.2	0.1	0.33	0.2	0.1	0.67	0.2	0.1	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 23: Per-circuit pass@k scores (k = 3, 5, 10) for CKT21–CKT24 across multiple models

Model	25. Comparator			26. LDO			27. PLL			28. SAR-ADC		
	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10	p@3	p@5	p@10
Gemini-2.5-pro	0	0	0	0	0	0	0	0	0	0	0	0
GPT-4o	0	0	0	0	0	0	0	0	0	0	0	0
Claude-3.7-sonnet	0	0	0	0	0	0	0	0	0	0	0	0
Grok-3	0	0	0	0	0	0	0	0	0	0	0	0
Doubao-1.5-vision-pro	0	0	0	0	0	0	0	0	0	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0	0	0

Table 24: Per-circuit pass@k scores (k = 3, 5, 10) for CKT25–CKT28 across multiple models

### B.3.2 TESTBENCH DESIGN TASK

ID	Circuit Type	# Metrics	ID	Circuit Type	# Metrics
1	Cross-coupled differential amplifier	CMRR, DC gain, GBW, Phase margin, Power, PSR, SR	7	LDO	LDR, LNR, Drop voltage, DC gain, Phase margin, PSR, Offset
2	Comparator	Delay, Offset	8	VCO	Jitter, Phase noise
3	Bootstrap	ENOB	9	Unit capacitor	MC-mismatch
4	Telescopic cascode OTA	CMRR, DC gain, GBW, Phase margin, Power, PSR, SR	10	Folded cascode OTA	DC gain, SR, Phase margin, GBW, Power
5	PLL	Jitter, Phase noise	11	SAR-ADC	ENOB
6	MOS_Ron	Ron	12	Bandgap	BuildingupV, Noise, PSR, TC

Table 25: Testbench design tasks with metrics to be simulated.

Models	1. Cross-coupled differential amplifier							2. Comparator		3. Boot-strap
	CMRR	DC gain	GBW	Phase margin	Power	PSR	SR	Delay	Offset	ENOB
Gemini-2.5-pro	0	0	0	0	0	0	0	0	0	0
GPT-4o	<b>0 (1)</b>	0	0	0	<b>0(4)</b>	<b>0(2)</b>	0	<b>0(2)</b>	<b>0(2)</b>	0
Claude-3.7-sonnet	0	0	0	0	0	0	0	0	0	0
Grok-3	0	0	0	0	0	0	0	0	0	0
Doubao-1.5-vision-pro	0	0	0	0	0	0	0	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0

Table 26: Cross-coupled differential amplifier, Comparator, and Bootstrap Circuit Design Performance Across Different Models

Models	4. Telescopic cascode OTA							5. PLL		6. MOS_Ron
	CMRR	DC gain	GBW	Phase margin	Power	PSR	SR	Jitter	Phase noise	Ron
Gemini-2.5-pro	0	0	0	0	0	0	0	0	0	0
GPT-4o	0	0	0	0	0	0	0	0	0	0
Claude-3.7-sonnet	0	0	0	0	0	0	0	0	0	0
Grok-3	0	0	0	0	0	0	0	0	0	0
Doubao-1.5-vision-pro	0	0	0	0	0	0	0	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0

Table 27: Telescopic cascode OTA, PLL, and MOS\_Ron Performance Across Different Models

Models	7. LDO							8. VCO		9. Unit capacitor
	LDR	LNR	Drop voltage	DC gain	Phase margin	PSR	Offset	Jitter	Phase noise	MC-mismatch
Gemini-2.5-pro	0	0	0	0	0	0	0	0	0	0
GPT-4o	0	0	0	0	0	0	0	0	0	<b>0(3)</b>
Claude-3.7-sonnet	0	0	0	0	0	0	0	0	0	0
Grok-3	0	0	0	0	0	0	0	0	0	0
Doubao-1.5-vision-pro	0	0	0	0	0	0	0	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0

Table 28: LDO, VCO, and Unit Capacitor Performance Across Different Models

Models	10. Folded cascode OTA					11. SAR-ADC	12. Bandgap			
	DC gain	SR	Phase margin	GBW	Power	ENOB	BuildiupV	Noise	PSR	TC
Gemini-2.5-pro	0	0	0	0	0	0	0	0	0	0
GPT-4o	0	0	0	0	0	0	0	<b>0(1)</b>	0	0
Claude-3.7-sonnet	0	0	0	0	0	0	0	0	0	0
Grok-3	0	0	0	0	0	0	0	0	0	0
Doubao-1.5-vision-pro	0	0	0	0	0	0	0	0	0	0
Kimi-VL-A3B	0	0	0	0	0	0	0	0	0	0
Qwen2.5-VL-72B	0	0	0	0	0	0	0	0	0	0

Table 29: Folded Cascode OTA, SAR-ADC, and Bandgap Performance Across Different Models

## C TEST EXAMPLES

### C.1 EXAMPLES OF PERCEPTION TASKS



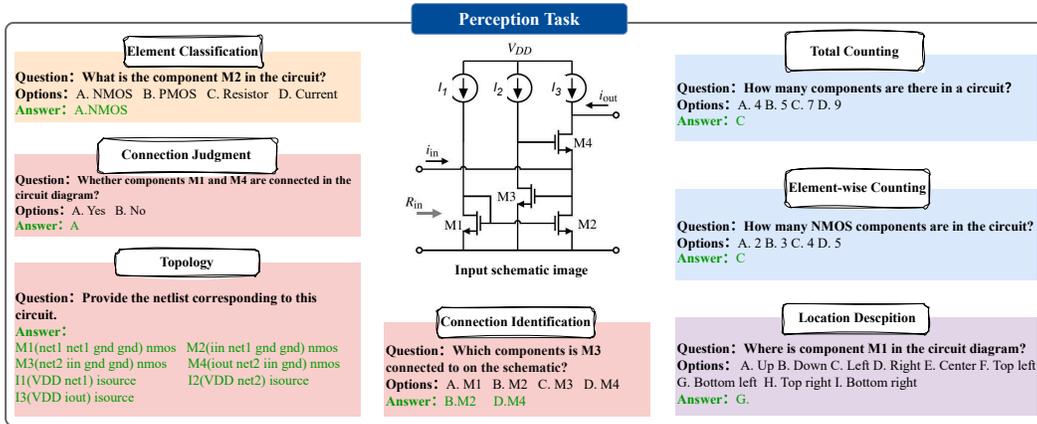


Figure 7: Example of **Perception** task in AMSbench

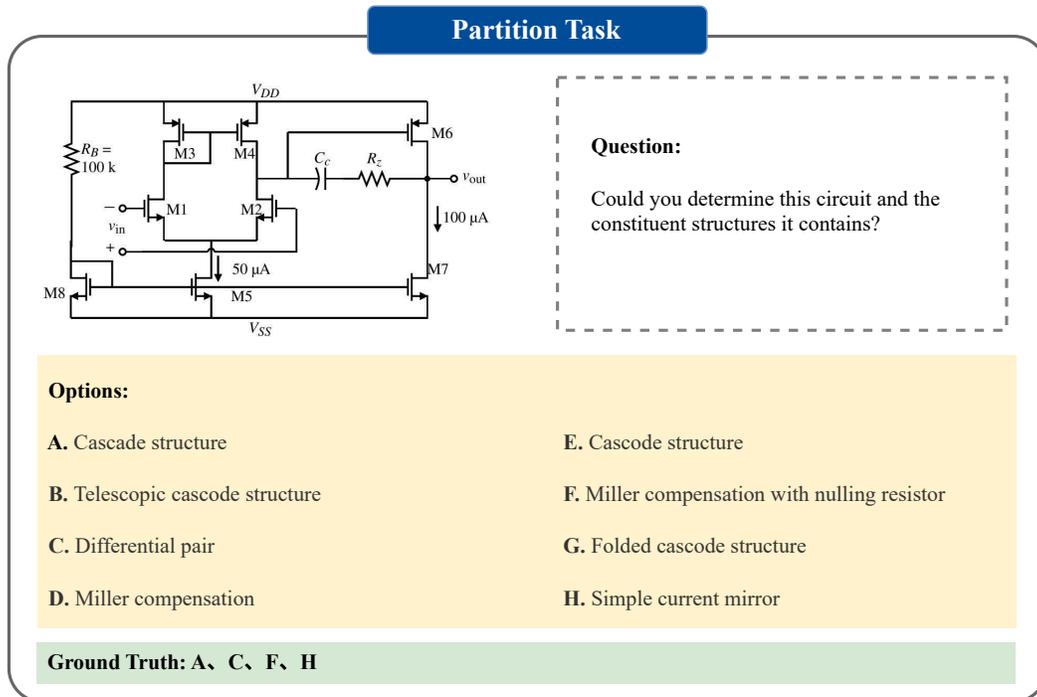

## C.2 EXAMPLES OF ANALYSIS TASKS

Reasoning Task

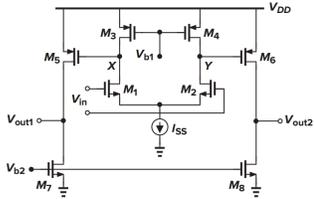

**Question:**

According to the following circuit diagram, tell me why the circuit represented by this diagram is an operational amplifier?

**Options:**

**A.** Through the coordination of the differential input stage, the high-gain intermediate stage and the output stage, high voltage gain and differential signal processing capabilities are achieved, which conforms to the core characteristics of an operational amplifier, namely "high gain, differential input, and signal amplification ability". Therefore, it belongs to the operational amplifier circuit.

**B.** This circuit does not meet the typical structural requirements of an operational amplifier: An operational amplifier usually consists of an input stage (differential amplification), a high-gain intermediate stage, and an output stage (such as a push-pull structure), and it needs to have characteristics such as high gain and frequency compensation. However, this circuit only exhibits a differential input structure (M1, M2), lacking the crucial intermediate high-gain amplification stage and the standard output stage (such as a push-pull output circuit), and it also does not have components related to frequency compensation. As a result, it cannot achieve the core functions required for an operational amplifier, such as high gain, low output impedance, and stable amplification. Therefore, it does not belong to an operational amplifier circuit.

**C.** An operational amplifier needs to have a complete frequency compensation mechanism to ensure the stability of the circuit (for example, by implementing phase margin adjustment through a Miller capacitor, etc.). However, this circuit has not designed any structure related to frequency compensation. It cannot effectively suppress self-excited oscillation under different input signal frequencies, nor can it ensure the stability during closed-loop operation. This is a clear deficiency compared to the stable amplification characteristics (including the stability of the frequency response) that an operational amplifier must meet. Therefore, it does not belong to an operational amplifier circuit.


**D.** The circuit diagram does not represent an operational amplifier because it lacks the key characteristics of an operational amplifier, such as the feedback mechanism, multi-stage amplification, and buffered output structures. Its output stage is simple and cannot achieve the high gain and stable performance required by an operational amplifier.

Ground Truth: A


Figure 9: Examples of **Reasoning** task in AMSbench

Function Task


**A**

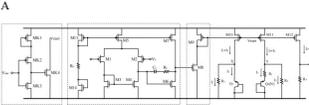


**B**

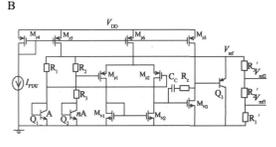

**C**

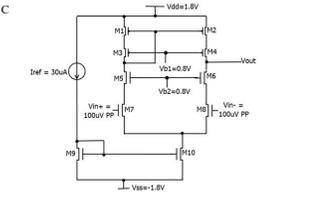

**D**

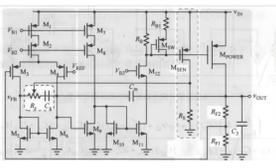


**Question:**

What is the intended function of the circuit in the diagram?

Ground Truth: D

Figure 10: Example of **Function(image as options)** task in AMSbench

### Function Task

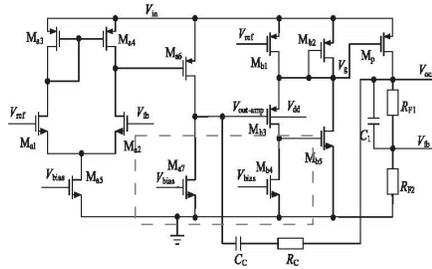

**Question:**

What is the intended function of the circuit in the diagram?


**Options:**

- A. Op-amp
- B. LDO
- C. Comparator
- D. Bandgap

**Ground Truth: B**

Figure 11: Example of **Function(text as options)** task in AMSbench

### Caption Task

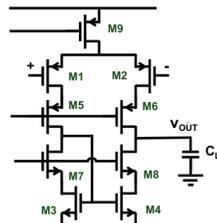

**Question:**

There is a circuit diagram below, please describe this circuit in detail.


**Options:**

- A. In this folded cascode amplifier, cascode transistors M5–M8 are stacked in series with the current mirror and input devices to compensate for the low intrinsic gain of nanometer MOSFETs. The feedback loop around transistor M2 includes cascode M8, which extends the output swing by regulating the drain voltage of M2. The telescopic topology increases output impedance, thereby improving gain without affecting GBW. However, the cascode configuration necessitates a higher supply voltage to maintain proper biasing, resulting in a marginal rise in overall power dissipation.
- B. The gain of this voltage amplifier is constrained by the low intrinsic gain of cascode transistors in nanometer MOSFETs. To enhance performance, four cascode devices (M5–M8) are placed in parallel with the input pair and current mirror. Cascode M5 is integrated into the feedback loop around transistor M1, which stabilizes the gain while maximizing output swing. This telescopic configuration significantly boosts both the output impedance and the gain-bandwidth product (GBW) due to improved loop gain, though the additional cascode stages introduce a slight increase in power consumption from elevated bias currents.
- C. The gain of such a voltage amplifier is rather limited as the gain per transistor can be quite small for nanometer MOS devices. This is why cascodes are better added. Four cascode MOS transistors are added M5–8 in series with the input devices and current mirror, as shown in this slide. Note that cascode M7 is included in the feedback loop around transistor M3, which allows a larger output swing. This is called the telescopic CMOS OTA. The impedance at the output node increases considerably, but not the GBW.
- D. This telescopic CMOS OTA addresses limited per-stage gain by incorporating cascode transistors M5–M8 in series with the differential input pair. Cascode M6 is embedded within the feedback loop surrounding transistor M4, enabling wider output swing and higher DC gain. The elevated output impedance directly enhances the GBW, as the cascodes reduce parasitic capacitance at the output node. Despite the added complexity, power consumption remains unchanged because the cascode devices operate in the saturation region without altering the bias current.

**Ground Truth: A**

Figure 12: Example of **Caption** task in AMSbench

### Electrical\_Characteristic Task

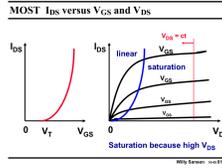

#### Question:

Based on the  $I_{DS}$ - $V_{GS}$  characteristic curve on the left, what important circuit characteristic does the MOSFET's threshold voltage ( $V_T$ ) represent?


#### Options:

- A. It signifies the gate-source voltage ( $V_{GS}$ ) at which the MOSFET begins to conduct current, marking the transition from off to on state.
- B. It represents the gate-source voltage ( $V_{GS}$ ) below which the drain-source current ( $I_{DS}$ ) is negligible, indicating the device is in the cut-off state.
- C. It indicates the gate-source voltage ( $V_{GS}$ ) required for the MOSFET to operate in the saturation region, where  $I_{DS}$  is largely independent of  $V_{DS}$ .
- D. It defines the maximum drain-source current ( $I_{DS}$ ) that the MOSFET can conduct when fully turned on.

**Ground Truth: B**

Figure 13: Example of **Electrical Characteristic** task in AMSbench

### Switching\_Timing Task

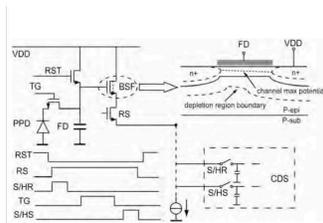

#### Question:

Case (a) is preferable for applications requiring a more dynamic response, as its larger  $V_{CF}$  and  $V_{EA}$ . Based on the provided timing diagram, in the CMOS image sensor pixel readout process, the S/HR (reset sampling) pulse occurs before the TG (transfer gate) pulse, while the S/HS (signal sampling) pulse occurs after the TG pulse. What is the main purpose of this timing arrangement?


#### Options:

- A. To ensure that the photodiode has completed its charge integration cycle before the signal is read out, maximizing light sensitivity.
- B. To implement Correlated Double Sampling (CDS) function, by capturing the noise and bias voltage of the Floating Diffusion (FD) node before charge transfer, and then capturing the signal plus noise level after charge transfer.
- C. To prevent charge blooming by ensuring the transfer gate is fully closed before the signal is sampled, thus maintaining pixel isolation.
- D. To optimize the pixel readout speed and reduce latency by sequentially activating the sampling switches at precise intervals.

**Ground Truth: B**

Figure 14: Example of **Switching Timing** task in AMSbench

### Signal\_Wave Task

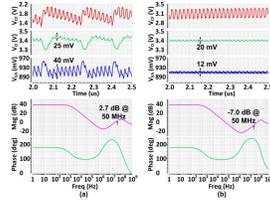

#### Question:

Observe the two sets of waveforms and frequency response curves in (a) and (b). From the perspective of circuit performance and stability, which case exhibits superior steady-state output characteristics and control loop stability?


#### Options:

- A. Case (a) is superior because its frequency response shows a positive gain of 2.7 dB at 50 MHz, which implies a higher gain-bandwidth product and faster response, despite slightly larger output ripple.
- B. Case (b) is superior because its output voltage  $V_O$  and error amplifier output  $V_{EA}$  ripple amplitudes are significantly reduced, and its frequency response shows an attenuation of -7.0 dB at 50 MHz, indicating better noise suppression capability and loop damping.
- C. Both cases exhibit similar control loop stability, as indicated by their comparable phase responses. The choice between (a) and (b) would depend on specific application requirements for output ripple versus control signal amplitude.
- D. Case (a) is preferable for applications requiring a more dynamic response, as its larger  $V_{CF}$  and  $V_{EA}$  ripples suggest a more active control loop, and the peaking in its frequency response indicates a higher resonant frequency for faster transient recovery.

**Ground Truth: B**

Figure 15: Example of **Signal Wave** task in AMSbench

### Layout Task

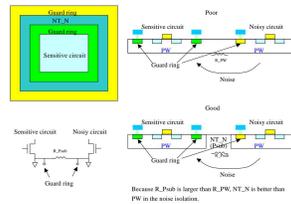

#### Question:

Based on the provided layout diagrams and the principles of noise isolation in integrated circuits, which of the following statements accurately describes the recommended use and properties of the NT\_N layer for effective substrate noise reduction?

#### Options:

- A. Use NT\_N layer (width  $\geq 1 \mu\text{m}$ ) as a high resistance region to isolate high-frequency circuits, reducing substrate noise coupling. Minimize signal lines crossing this region and use upper-level metals above it to maximize distance from the substrate.
- B. Use NT\_N layer (width  $< 1 \mu\text{m}$ ) as a low resistance region to connect low-frequency circuits, enhancing substrate signal propagation. Maximize signal lines crossing this region and use lower-level metals above it to minimize distance from the substrate.
- C. Use NT\_N layer as a primary guard ring for latch-up prevention, ensuring it is tied to a stable power supply. Critical signal lines should be routed within the NT\_N region for improved current carrying capacity.
- D. Use NT\_N layer (width  $\geq 1 \mu\text{m}$ ) as a conductive path to shunt noise currents directly to ground, thereby improving signal integrity. It is beneficial to place sensitive analog blocks directly on top of the NT\_N layer for better shielding.

**Ground Truth: A**

Figure 16: Example of **Layout** task in AMSbench

## C.3 EXAMPLES OF DESIGN TASKS

User	Assistant (Circuit Design Prompt)
<p>You are an analog integrated circuits expert.</p>	<p><b>Task 2</b>            from PySpice.Spice.Netlist import Circuit            from PySpice.Unit import *</p> <p>circuit = Circuit('Two-Stage Amplifier')            # Define the MOSFET models            circuit.model('nmos_model', 'nmos', level=1, kp=100e-6, vto=0.5)            circuit.model('pmos_model', 'pmos', level=1, kp=50e-6, vto=-0.5)</p> <p># Power Supplies for the power and input signal</p> <p>circuit.V('dd', 'Vdd', circuit.gnd, 5.0) # 5V power supply            circuit.V('in', 'Vin', circuit.gnd, 1.0) # 1V input for bias voltage            circuit.V('bias', 'Vbias', circuit.gnd, 4.0) # 4V input for bias voltage</p> <p># First Stage: Common-Source with Active Load            # parameters: name, drain, gate, source, bulk, model, w, l            circuit.MOSFET('1', 'Drain1', 'Vin', circuit.gnd, circuit.gnd,            model='nmos_model', w=50e-6, l=1e-6)            circuit.MOSFET('2', 'Drain1', 'Vbias', 'Vdd', 'Vdd', model='pmos_model',            w=100e-6, l=1e-6)</p> <p># Second Stage: Common-Source with Resistor Load            circuit.MOSFET('3', 'Vout', 'Drain1', circuit.gnd, circuit.gnd,            model='nmos_model', w=100e-6, l=1e-6)            circuit.R('1', 'Vout', 'Vdd', 1@u_kΩ)</p> <p># Analysis Part            simulator = circuit.simulator()</p> <p>As you have seen, the output of your designed topology should consist of two tasks:</p> <ol style="list-style-type: none"> <li>1. Give a detailed design plan about all devices and their interconnectivity nodes and properties.</li> <li>2. Write a complete Python code, describing the topology of integrated analog circuits according to the design plan.</li> </ol> <p>Please make sure your Python code is compatible with PySpice.            Please give the runnable code without any placeholders.            Do not write other redundant codes after 'simulator = circuit.simulator()'.</p> <p>There are some tips you should remember all the time:</p> <ol style="list-style-type: none"> <li>1. For the MOSFET definition circuit.MOSFET(name, drain, gate, source, bulk, model, w=w1,l=l1), be careful about the parameter sequence.</li> <li>2. You should connect the bulk of a MOSFET to its source.</li> <li>3. Please use the MOSFET threshold voltage, when setting the bias voltage.</li> <li>4. Avoid giving any AC voltage in the sources, just consider the operating points.</li> <li>5. Make sure the input and output node names appear in the circuit.</li> <li>6. Avoid using subcircuits.</li> <li>7. Use nominal transistor sizing.</li> <li>8. Assume the Vdd = 5.0 V.</li> </ol> <p><b>Question:</b>            Design [TASK].            Input node name: [INPUT].            Output node name: [OUTPUT].</p> <p><b>Answer:</b> (.....)</p>
Assistant (Circuit Design Prompt)	<p>You aim to design a topology for a given circuit described in the text. Please ensure your designed circuit topology works properly and achieves the design requirements.</p> <p>Here is an example:</p> <p><b>Question:</b>            Design a 2-stage amplifier (first stage: a common-source stage with current-source load, second stage: a common-source stage with resistor load).</p> <p>Input node name: Vin, Vbias.            Output node name: Vout.</p> <p><b>Answer:</b></p> <p><b>Task 1</b></p> <p><b>Components Needed</b></p> <ul style="list-style-type: none"> <li>- <b>NMOS Transistors:</b> M1 and M3</li> <li>- <b>PMOS Transistors:</b> M2 (used as the current source in the first stage)</li> <li>- <b>Resistors:</b> R1 for the second stage load</li> <li>- <b>Power Supply:</b> Vdd for DC supply</li> <li>- <b>Input Signal Source:</b> Vin, Vbias for biasing and signal input</li> <li>- <b>Capacitors:</b> Not specified but can be included for coupling and bypass applications if required</li> </ul> <p><b>Stage 1: Common-Source Amplifier with Current Source Load</b></p> <ol style="list-style-type: none"> <li>1. <b>Transistor Setup:</b> <ul style="list-style-type: none"> <li>- <b>M1</b> (NMOS) as the main amplifying transistor.</li> <li>- Gate of <b>M1</b> is connected to the input node <b>Vin</b>.</li> <li>- Source of <b>M1</b> connected to the ground.</li> <li>- Drain of <b>M1</b> connected to the drain of <b>M2</b>.</li> </ul> </li> <li>2. <b>Biasing:</b> <ul style="list-style-type: none"> <li>- <b>Vin</b> provides the input signal.</li> <li>- <b>Vbias</b> is used to bias <b>M2</b> (PMOS), ensuring it operates as a current source.</li> </ul> </li> <li>3. <b>Current Source Load (M2):</b> <ul style="list-style-type: none"> <li>- <b>M2</b>, a PMOS transistor, is configured as a current source.</li> <li>- The source of <b>M2</b> is connected to <b>Vdd</b>, and its gate is connected to <b>Vbias</b>.</li> <li>- Drain of <b>M2</b> is connected to the drain of <b>M1</b>, providing a high-impedance load.</li> </ul> </li> </ol> <p><b>Stage 2: Common-Source Amplifier with Resistor Load</b></p> <ol style="list-style-type: none"> <li>1. <b>Transistor Setup:</b> <ul style="list-style-type: none"> <li>- <b>M3</b> (NMOS) as the main amplifying transistor for the second stage.</li> <li>- Gate of <b>M3</b> connected to the drain of <b>M1</b>.</li> <li>- Source of <b>M3</b> connected to the ground.</li> <li>- Drain of <b>M3</b> connected to <b>Vout</b> through resistor <b>R1</b>.</li> </ul> </li> <li>2. <b>Load and Coupling:</b> <ul style="list-style-type: none"> <li>- <b>R1</b> connects the drain of <b>M3</b> to <b>Vdd</b>. This resistor converts the current through <b>M3</b> into an output voltage.</li> </ul> </li> </ol>

Figure 17: Prompt of Circuit Design task in AMSbench

**User**

You are an analog integrated circuits expert.

**Assistant (Testbench Design Prompt)**

You are an analog circuit design engineer with over 10 years of experience, familiar with the Cadence Spectre simulation environment, CMOS circuit modeling, and various circuit performance testing methods.

I will provide a netlist file and schematic diagram of a "certain circuit" (given in both text and image formats). Based on the netlist file, please write a complete Spectre simulation input file (.cir format) to test the "certain performance" of the circuit, while keeping the core structure of the circuit unchanged.

**Requirements:**

Add the necessary excitation sources (such as voltage sources, current sources, etc.) and appropriate simulation analysis statements (such as ac, dc, tran, noise, etc.) to test the target performance.

The generated .cir file should be directly runnable in Spectre without any additional modifications.

Briefly explain your test configuration approach (including input signals, biasing methods, load, power supply, etc.).

**Please output exactly five separate Spectre testbench code blocks. Each block must be wrapped in triple backticks, like:**

```
// testbench #1
...
// testbench #2
...
```

**The example of the writing format of the testbench is referred to as follows:**  
<testbench\_format.cir>

Figure 18: Prompt of **Testbench Design** task in AMSbench

## D CASE STUDY

### D.1 PERCEPTION TASK FOR ERROR ANALYSIS

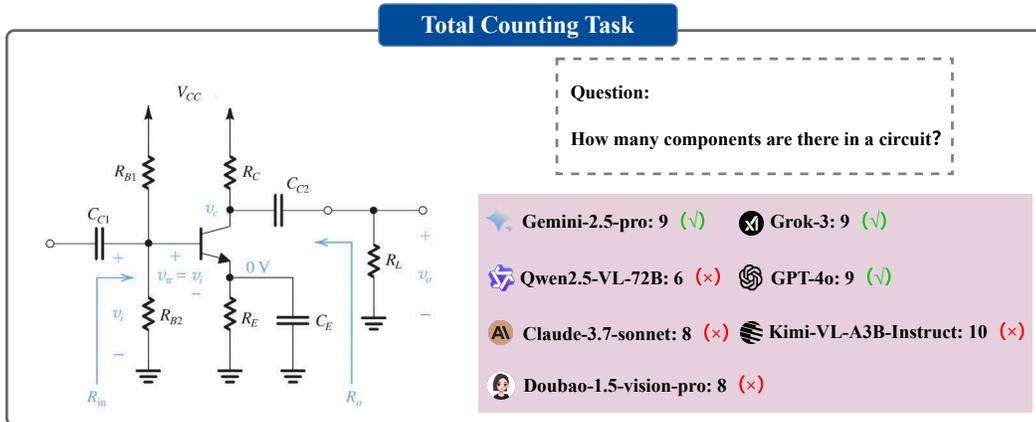


Figure 19: Example of **Total Counting** task across models

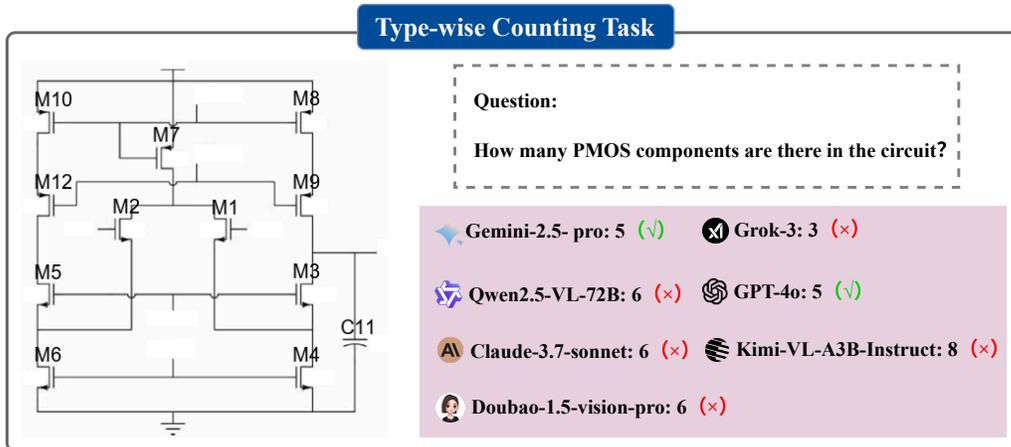


Figure 20: Example of **Type-wise Counting** task across models

### Element Classification Task

**Question:**

What is the component M2 in the circuit?

**Options:**

A. Current Source	B. Single-end Amp
C. PMOS	D. NMOS

**Ground Truth : D**

<p> Gemini-2.5-pro: <b>D</b></p> <p> Qwen2.5-VL-72B: <b>D</b></p> <p> Claude-3.7-sonnet: <b>D</b></p> <p> Doubao-1.5-vision-pro: <b>C</b></p>	<p> Grok-3: <b>D</b></p> <p> GPT-4o: <b>C</b></p> <p> Kimi-VL-A3B-Instruct: <b>D</b></p>
---	--

Figure 21: Example of **Element Classification** task across models

### Connection Judgment Task

**Question:**

Is M12 connected to R6?

**Options:**

A. Yes	B. No
--------	-------

**Ground Truth : B**

<p> Gemini-2.5-pro: <b>A</b></p> <p> Qwen2.5-VL-72B: <b>B</b></p> <p> Claude-3.7-sonnet: <b>B</b></p> <p> Doubao-1.5-vision-pro: <b>A</b></p>	<p> Grok-3: <b>A</b></p> <p> GPT-4o: <b>B</b></p> <p> Kimi-VL-A3B-Instruct: <b>A</b></p>
---	--

Figure 22: Example of **Connection Judgment** task across models

### Connection Identification Task

**Question:**

Which components is R15 connected to?

**Options:**

A. "Q9"	B. "R3"
C. "C2"	D. "Q28"
E. "Q31"	F. "R17"
G. "R18"	H. "R15"

**Ground Truth : A, E, G**

<p> <b>Gemini-2.5-pro: A, E, G</b></p> <p> <b>Qwen2.5-VL-72B: G</b></p> <p> <b>Claude-3.7-sonnet: A, E, G</b></p> <p> <b>Kimi-VL-A3B-Instruct: A, D, E, F, G, H</b></p>	<p> <b>Grok-3: A, G</b></p> <p> <b>GPT-4o: B, F, G</b></p> <p> <b>Doubao-1.5-vision-pro: A, E, G</b></p>
---	--

Figure 23: Example of **Connection Identification** task across models

### Location Description Task

**Question:**

What part of the circuit does the C4 occupy?

**Options:**

A. Bottom	B. Center
C. Bottom Left	D. Right
E. Top right	F. Left
G. Top left	H. Top

**Ground Truth : A**

<p> <b>Gemini-2.5-pro: I</b></p> <p> <b>Qwen2.5-VL-72B: A</b></p> <p> <b>Claude-3.7-sonnet: I</b></p> <p> <b>Kimi-VL-A3B-Instruct: C</b></p>	<p> <b>Grok-3: A</b></p> <p> <b>GPT-4o: C</b></p> <p> <b>Doubao-1.5-vision-pro: B</b></p>
--	---

Figure 24: Example of **Location Description** task across models


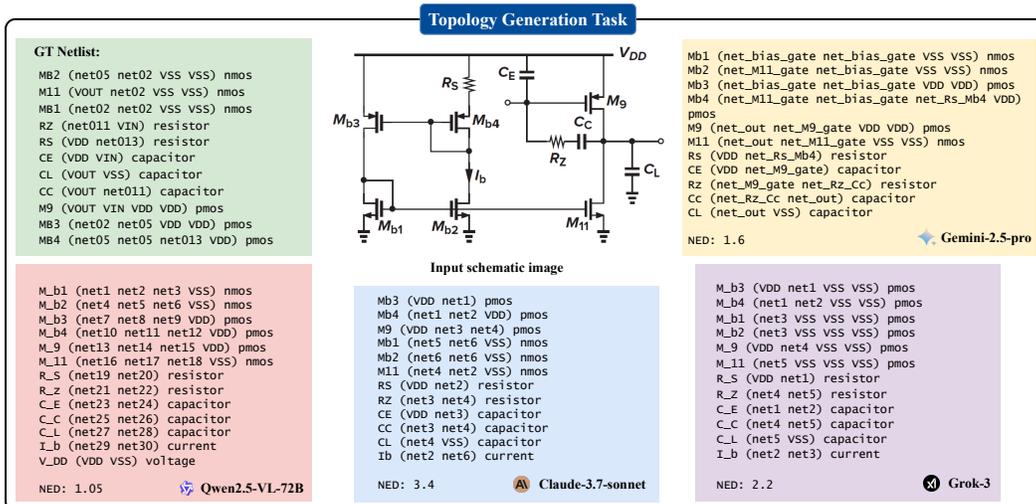


Figure 25: Example of **Topology Generation** task across models

D.2 ANALYSIS TASK FOR ERROR ANALYSIS

**Function(Text) Task**

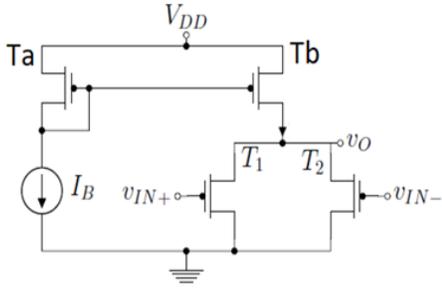

The diagram shows a differential pair of transistors  $T_1$  and  $T_2$  with a common emitter current source  $I_B$ . The bases are connected to  $v_{IN+}$  and  $v_{IN-}$ . The collectors are connected to  $V_{DD}$  through load resistors  $T_a$  and  $T_b$ . The output  $v_O$  is taken from the collector of  $T_2$ .

**Question:**

What is the circuit's primary functional type in the diagram?

**Options:**

A. LDO	B. Op-amp
C. Comparator	D. Bandgap

**Ground Truth : B**

<p>🌟 Gemini-2.5-pro: <b>B</b></p> <p>🌀 Qwen2.5-VL-72B: <b>B</b></p> <p>🏠 Claude-3.7-sonnet: <b>C</b></p> <p>🌀 Kimi-VL-A3B-Instruct: <b>B</b></p>	<p>🌟 Grok-3: <b>B</b></p> <p>🌀 GPT-4o: <b>C</b></p> <p>🏠 Doubao-1.5-vision-pro: <b>C</b></p>
--	--


Figure 26: Example of **Function Text** task across models


**Function(Image)Task**


**Question:**


Choose the schematic that represents a comparator.

**Options:**

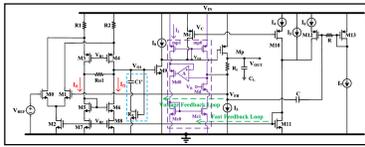A. 

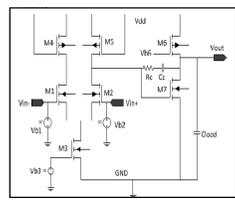B. 

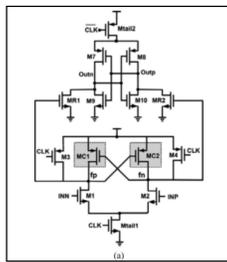
C. 

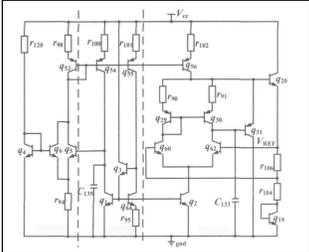D. 

<p>🌟 Gemini-2.5-pro: <b>C</b></p> <p>🌀 Qwen2.5-VL-72B: <b>B</b></p> <p>🏠 Claude-3.7-sonnet: <b>B</b></p> <p>🌀 Kimi-VL-A3B-Instruct: <b>C</b></p> <p>🏠 Doubao-1.5-vision-pro: <b>C</b></p>	<p>🌟 Grok-3: <b>A</b></p> <p>🌀 GPT-4o: <b>C</b></p>
---	---

Figure 27: Example of **Function Image** task across models

### Partition Task

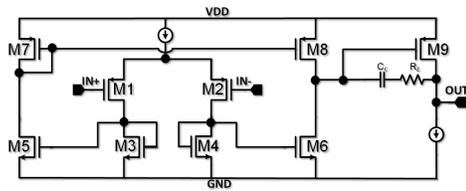

#### Question:

Which structural elements does the circuit include?

#### Options:

- A. Diode-connected load
- B. Wilson current mirror
- C. Cascode current mirror
- D. Source degenerated differential pair
- E. Active load(current mirror load) .
- F. Differential pair .
- G. Simple current mirror.
- H. Common-source amplifier .

**Ground Truth: A, E, F, G, H**

🔹 Gemini-2.5-pro: **E, F, G, H**

🔹 Grok-3: **E, F**

🔹 Qwen2.5-VL-72B: **A, C, D, E**

🔹 GPT-4o: **E, F, H**


🔹 Claude-3.7-sonnet: **C, F**

🔹 Kimi-VL-A3B-Instruct: **D**

🔹 Doubao-1.5-vision-pro: **E, F**

Figure 28: Example of **Partition Identification** task across models

### Reasoning Task

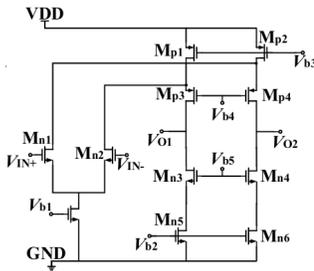

#### Question:

What distinguishes this circuit as an operational amplifier in the given diagram?

#### Ground Truth:

This circuit qualifies as an operational amplifier because: The circuit includes a differential input stage formed by transistors Mn1 and Mn2, which is a fundamental feature of any operational amplifier. These transistors receive differential signals at their gates (VIN+ and VIN-), enabling differential signal amplification. Tail current sources are implemented using transistors Mp1 and Mp2, which help to set a proper operating point for Mp3-Mp4. The transistors Mn3-Mn6 form a cascode current source, indicated by the bias voltage Vb2 and Vb5, which can increase output impedance. A gain stage is built with transistors Mp3, Mp4, which function as a cascode and further amplify the signal. The outputs VO1 and VO2 suggest a differential output configuration, which is common in fully differential op-amp designs. Multiple bias voltages (Vb1, Vb2, Vb3, Vb4, and Vb5) are used to properly bias various stages of the circuit, which is a typical approach in analog integrated op-amp design to maintain correct operating points.

#### ✘ Grok-3:

The circuit is an operational amplifier primarily due to its differential pair Mn1 and Mn2, which amplify the input voltage difference through a resistive load formed by Mp3 and Mp4. A current source at the tail of the input stage, implemented by Mn5 and Mn6 under Vb2 control, sets the quiescent current. The cascode stage Mp1 and Mp2 provides voltage gain by stacking transistors, while Mp5 and Mp6 serve as active loads for the output stage, producing the differential outputs VO1 and VO2. The bias voltages (Vb1-Vb5) are critical for adjusting the transconductance of the input stage and tuning the cascode's gain, which aligns with conventional op-amp architectures that prioritize high open-loop gain and differential signal processing. (✘)

#### 🟡 Claude-3.7-sonnet:

This circuit qualifies as an operational amplifier because: The circuit includes a differential input stage formed by transistors Mn1 and Mn2, which is a fundamental feature of any operational amplifier. These transistors receive differential signals at their gates (VIN+ and VIN-), enabling differential signal amplification. Tail current sources are implemented using transistors Mp1 and Mp2, which help to set a proper operating point for Mp3-Mp4. The transistors Mn3-Mn6 form a cascode current source, indicated by the bias voltage Vb2 and Vb5, which can increase output impedance. A gain stage is built with transistors Mp3, Mp4, which function as a cascode and further amplify the signal. The outputs VO1 and VO2 suggest a differential output configuration, which is common in fully differential op-amp designs. Multiple bias voltages (Vb1, Vb2, Vb3, Vb4, and Vb5) are used to properly bias various stages of the circuit, which is a typical approach in analog integrated op-amp design to maintain correct operating points. (✔)

#### 🔹 Gemini-2.5-pro:

This circuit qualifies as an operational amplifier because: The circuit includes a differential input stage formed by transistors Mn1 and Mn2, which is a fundamental feature of any operational amplifier. These transistors receive differential signals at their gates (VIN+ and VIN-), enabling differential signal amplification. Tail current sources are implemented using transistors Mp1 and Mp2, which help to set a proper operating point for Mp3-Mp4. The transistors Mn3-Mn6 form a cascode current source, indicated by the bias voltage Vb2 and Vb5, which can increase output impedance. A gain stage is built with transistors Mp3, Mp4, which function as a cascode and further amplify the signal. The outputs VO1 and VO2 suggest a differential output configuration, which is common in fully differential op-amp designs. Multiple bias voltages (Vb1, Vb2, Vb3, Vb4, and Vb5) are used to properly bias various stages of the circuit, which is a typical approach in analog integrated op-amp design to maintain correct operating points. (✔)

#### 🔹 Qwen2.5-VL-72B:

This circuit qualifies as an operational amplifier because: The circuit includes a differential input stage formed by transistors Mn1 and Mn2, which is a fundamental feature of any operational amplifier. These transistors receive differential signals at their gates (VIN+ and VIN-), enabling differential signal amplification. Tail current sources are implemented using transistors Mp1 and Mp2, which help to set a proper operating point for Mp3-Mp4. The transistors Mn3-Mn6 form a cascode current source, indicated by the bias voltage Vb2 and Vb5, which can increase output impedance. A gain stage is built with transistors Mp3, Mp4, which function as a cascode and further amplify the signal. The outputs VO1 and VO2 suggest a differential output configuration, which is common in fully differential op-amp designs. Multiple bias voltages (Vb1, Vb2, Vb3, Vb4, and Vb5) are used to properly bias various stages of the circuit, which is a typical approach in analog integrated op-amp design to maintain correct operating points. (✔)

#### 🟡 GPT-4o:

The circuit is an operational amplifier primarily due to its differential pair Mn1 and Mn2, which amplify the input voltage difference through a resistive load formed by Mp3 and Mp4. A current source at the tail of the input stage, implemented by Mn5 and Mn6 under Vb2 control, sets the quiescent current. The cascode stage Mp1 and Mp2 provides voltage gain by stacking transistors, while Mp5 and Mp6 serve as active loads for the output stage, producing the differential outputs VO1 and VO2. The bias voltages (Vb1-Vb5) are critical for adjusting the transconductance of the input stage and tuning the cascode's gain, which aligns with conventional op-amp architectures that prioritize high open-loop gain and differential signal processing. (✘)

#### 🟡 Kimi-VL-A3B-Instruct:


The circuit is an operational amplifier primarily due to its differential pair Mn1 and Mn2, which amplify the input voltage difference through a resistive load formed by Mp3 and Mp4. A current source at the tail of the input stage, implemented by Mn5 and Mn6 under Vb2 control, sets the quiescent current. The cascode stage Mp1 and Mp2 provides voltage gain by stacking transistors, while Mp5 and Mp6 serve as active loads for the output stage, producing the differential outputs VO1 and VO2. The bias voltages (Vb1-Vb5) are critical for adjusting the transconductance of the input stage and tuning the cascode's gain, which aligns with conventional op-amp architectures that prioritize high open-loop gain and differential signal processing. (✘)

#### 🟡 Doubao-1.5-vision-pro:

This circuit qualifies as an operational amplifier because: The circuit includes a differential input stage formed by transistors Mn1 and Mn2, which is a fundamental feature of any operational amplifier. These transistors receive differential signals at their gates (VIN+ and VIN-), enabling differential signal amplification. Tail current sources are implemented using transistors Mp1 and Mp2, which help to set a proper operating point for Mp3-Mp4. The transistors Mn3-Mn6 form a cascode current source, indicated by the bias voltage Vb2 and Vb5, which can increase output impedance. A gain stage is built with transistors Mp3, Mp4, which function as a cascode and further amplify the signal. The outputs VO1 and VO2 suggest a differential output configuration, which is common in fully differential op-amp designs. Multiple bias voltages (Vb1, Vb2, Vb3, Vb4, and Vb5) are used to properly bias various stages of the circuit, which is a typical approach in analog integrated op-amp design to maintain correct operating points. (✔)

Figure 29: Example of Reasoning task across models

### Caption Generation Task

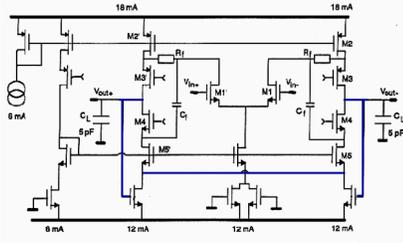

#### Question:

Give a detailed description of the following circuit.

#### Ground Truth:

An example of CMFB with MOS transistors in the linear region is shown in this diagram. It is a high-speed amplifier. A GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads can be reached thanks to the large currents, despite the old  $1.2\text{ }\mu\text{m}$  CMOS technology. It is a folded cascode for a differential operation. The only additional feature is the feedforward around the slower PMOS cascode through capacitors  $C_1$ . The outputs are around  $0\text{ V}$ , because the gates of the NMOSs providing DC current to the input pair are at zero ground.

#### Grok-3:

This high-speed folded cascode amplifier employs a  $1.2\text{ }\mu\text{m}$  CMOS process to achieve a GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads, primarily due to the low threshold voltages of the transistors. The CMFB circuit uses NMOS devices in the triode region to adjust the tail current, while feedforward capacitors  $C_1$  are connected around the NMOS cascode transistors to bypass their high-impedance nodes. The output DC level is stabilized at  $0\text{ V}$  because the PMOS current mirror gates are referenced to ground, ensuring proper biasing. The design avoids slow PMOS cascode by relying on dynamic current steering through the feedforward path. (x)

#### Claude-3.7-sonnet:

An example of CMFB with MOS transistors in the linear region is shown in this diagram. It is a high-speed amplifier. A GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads can be reached thanks to the large currents, despite the old  $1.2\text{ }\mu\text{m}$  CMOS technology. It is a folded cascode for a differential operation. The only additional feature is the feedforward around the slower PMOS cascode through capacitors  $C_1$ . The outputs are around  $0\text{ V}$ , because the gates of the NMOSs providing DC current to the input pair are at zero ground. (v)

#### Gemini-2.5-pro:

An example of CMFB with MOS transistors in the linear region is shown in this diagram. It is a high-speed amplifier. A GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads can be reached thanks to the large currents, despite the old  $1.2\text{ }\mu\text{m}$  CMOS technology. It is a folded cascode for a differential operation. The only additional feature is the feedforward around the slower PMOS cascode through capacitors  $C_1$ . The outputs are around  $0\text{ V}$ , because the gates of the NMOSs providing DC current to the input pair are at zero ground. (v)

#### Qwen2.5-VL-72B:

This high-speed folded cascode amplifier employs a  $1.2\text{ }\mu\text{m}$  CMOS process to achieve a GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads, primarily due to the low threshold voltages of the transistors. The CMFB circuit uses NMOS devices in the triode region to adjust the tail current, while feedforward capacitors  $C_1$  are connected around the NMOS cascode transistors to bypass their high-impedance nodes. The output DC level is stabilized at  $0\text{ V}$  because the PMOS current mirror gates are referenced to ground, ensuring proper biasing. The design avoids slow PMOS cascode by relying on dynamic current steering through the feedforward path. (x)

#### GPT-4o:

This high-speed folded cascode amplifier employs a  $1.2\text{ }\mu\text{m}$  CMOS process to achieve a GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads, primarily due to the low threshold voltages of the transistors. The CMFB circuit uses NMOS devices in the triode region to adjust the tail current, while feedforward capacitors  $C_1$  are connected around the NMOS cascode transistors to bypass their high-impedance nodes. The output DC level is stabilized at  $0\text{ V}$  because the PMOS current mirror gates are referenced to ground, ensuring proper biasing. The design avoids slow PMOS cascode by relying on dynamic current steering through the feedforward path. (x)

#### Kimi-VL-A3B-Instruct:


This circuit implements a folded cascode operational amplifier optimized for high-speed performance, achieving a GBW of  $850\text{ MHz}$  with two  $5\text{ pF}$  loads, primarily due to the use of advanced biasing techniques in a  $1.2\text{ }\mu\text{m}$  CMOS process. The common-mode feedback (CMFB) mechanism employs NMOS transistors operating in the saturation region to stabilize the output common-mode voltage. A key feature is the feedforward path through capacitors  $C_1$  by bypassing the slower NMOS cascode transistors, which enhances phase margin. The output DC level is maintained near  $0\text{ V}$  because the gates of the PMOS current sources are biased at the supply voltage, ensuring symmetric current distribution. (x)

#### Doubao-1.5-vision-pro:

This high-speed folded cascode amplifier employs a  $1.2\text{ }\mu\text{m}$  CMOS process to achieve a GBW of  $850\text{ MHz}$  with  $5\text{ pF}$  loads, primarily due to the low threshold voltages of the transistors. The CMFB circuitry uses NMOS devices in the triode region to adjust the tail current, while feedforward capacitors  $C_1$  are connected around the NMOS cascode transistors to bypass their high-impedance nodes. The output DC level is stabilized at  $0\text{ V}$  because the PMOS current mirror gates are referenced to ground, ensuring proper biasing. The design avoids slow PMOS cascodes by relying on dynamic current steering through the feedforward path. (x)

Figure 30: Example of Caption Generation task across models

## Electrical\_Characteristic Task

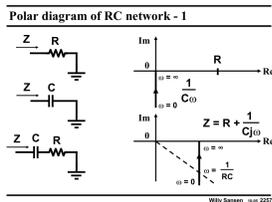

### Question:

Observe the impedance polar plot of the series RC circuit ( $Z = R + 1/(j\omega C)$ ) in the figure. As the angular frequency  $\omega$  increases from 0 to infinity, how does the impedance  $Z$  of this circuit change its trajectory on the complex plane?

### Options:

- A. The trajectory moves vertically upwards from the point  $(R, 0)$  on the complex plane, eventually reaching the point  $(R, +\infty)$ .
- B. The trajectory moves vertically downwards from the point  $R$  on the real axis, eventually reaching the point  $(R, -\infty)$ .
- C. The trajectory moves vertically upwards from the point  $(R, -\infty)$  on the complex plane, eventually reaching the point  $R$  on the real axis.
- D. The trajectory forms a semicircle in the lower half of the complex plane, starting from the origin  $(0,0)$  and ending at the point  $(R,0)$ .

**Groud Truth: C**

🌟 Gemini-2.5-pro: **C**

📧 Grok-3: **C**

🔗 Qwen2.5-VL-72B: **C**

🌀 GPT-4o: **D**


🍷 Claude-3.7-sonnet: **C**

🌐 Kimi-VL-A3B-Instruct: **D**

👤 Doubao-1.5-vision-pro: **B**

Figure 31: Example of **ElectricalCharacteristic** task across models

## Signal Wave Task

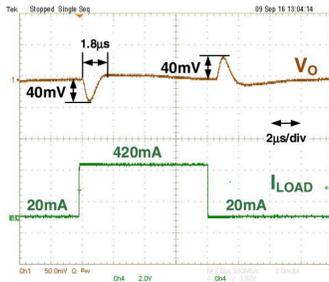

### Question:

Based on the provided waveform plot, what is the peak-to-peak output voltage deviation observed for this voltage regulator during load transient changes?

### Options:

- A. 40mV.
- B. 80mV.
- C. 20mV.
- D. 60mV.

**Ground Truth: B**

◆ Gemini-2.5-pro: **B**

⊗ Grok-3: **A**

⚡ Qwen2.5-VL-72B: **B**

⊗ GPT-4o: **A**


Ⓐ Claude-3.7-sonnet: **B**

⊗ Kimi-VL-A3B-Instruct: **A**

👤 Doubao-1.5-vision-pro: **B**

Figure 32: Example of **Signal Wave** task across models

## Switch Timing Task

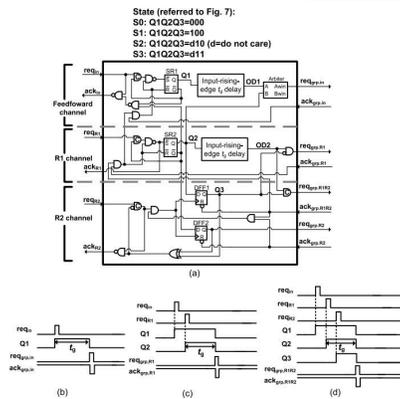

### Question:

In timing diagrams (b), (c), and (d), the delay labeled  $t_g$  exists between the rising edge of signals  $Q1$ ,  $Q2$ , or  $Q3$  and the rising edge of their corresponding  $req_{grp}$  signals (e.g.,  $req_{grp} \in$ ,  $req_{grp} \cdot R1$ , or  $req_{grp} \cdot R1R2$ ). Analyzing circuit diagram (a), what role does this  $t_g$  delay play in the circuit?

### Options:

- A. It signifies the delay from the rising edge of the input request signal ( $req_e$ ,  $req_{R1}$ ,  $req_{R2}$ ) until the internal state signals ( $Q1$ ,  $Q2$ ,  $Q3$ ) begin to change.
- B. It represents the inherent processing delay required for the circuit to generate the external request signal after the internal state signals ( $Q1$ ,  $Q2$ ,  $Q3$ ) have stabilized.
- C. It is merely the cumulative propagation delay of the combinational logic gates ( $OD1$ ,  $OD2$ , and others) that directly follow the  $Q$  signals to produce the  $req_{grp}$  outputs.
- D. It is a fixed delay added to prevent race conditions between the  $req_{grp}$  signals and their corresponding  $ack_{grp}$  signals in the handshake protocol.

**Ground Truth: B**

🌟 Gemini-2.5-pro: **B**

🌟 Grok-3: **B**

🌟 Qwen2.5-VL-72B: **B**

🌟 GPT-4o: **B**

🌟 Claude-3.7-sonnet: **C**

🌟 Kimi-VL-A3B-Instruct: **A**

🌟 Doubao-1.5-vision-pro: **C**

Figure 33: Example of **Switching Timing** task across models

**Layout Task**

**Question:**

The provided image illustrates a common Design Rule Check (DRC) principle applied to OPC (Optical Proximity Correction) layers in integrated circuit layout. Based on the visual examples and typical DRC considerations for manufacturability, which of the following statements accurately describes a forbidden geometric configuration for these layers??

**Options:**

- A. For the OPC layers, any edge of length  $< 1.0 \times$  minimum width must be adjacent to an edge of length greater than  $1.0 \times$  minimum width.
- B. For the OPC layers, any edge of length  $< 1.0 \times$  minimum width cannot have another adjacent edge of length  $< 1.0 \times$  minimum width.
- C. For the OPC layers, any edge of length  $< 1.0 \times$  minimum width cannot have more than one adjacent edge of length  $< 1.0 \times$  minimum width.
- D. For the OPC layers, any edge of length  $< 1.0 \times$  minimum width cannot have another adjacent edge of length equal to or greater than  $1.0 \times$  minimum width.

**Ground Truth: B**

Gemini-2.5-pro: **B**

Grok-3: **B**

Qwen2.5-VL-72B: **B**

GPT-4o: **B**

Claude-3.7-sonnet: **B, C**

Kimi-VL-A3B-Instruct: **B**

Doubao-1.5-vision-pro: **B**

Figure 34: Example of **Layout** task across models



#### D.4 EXAMPLE OF DEVICE GROUNDING

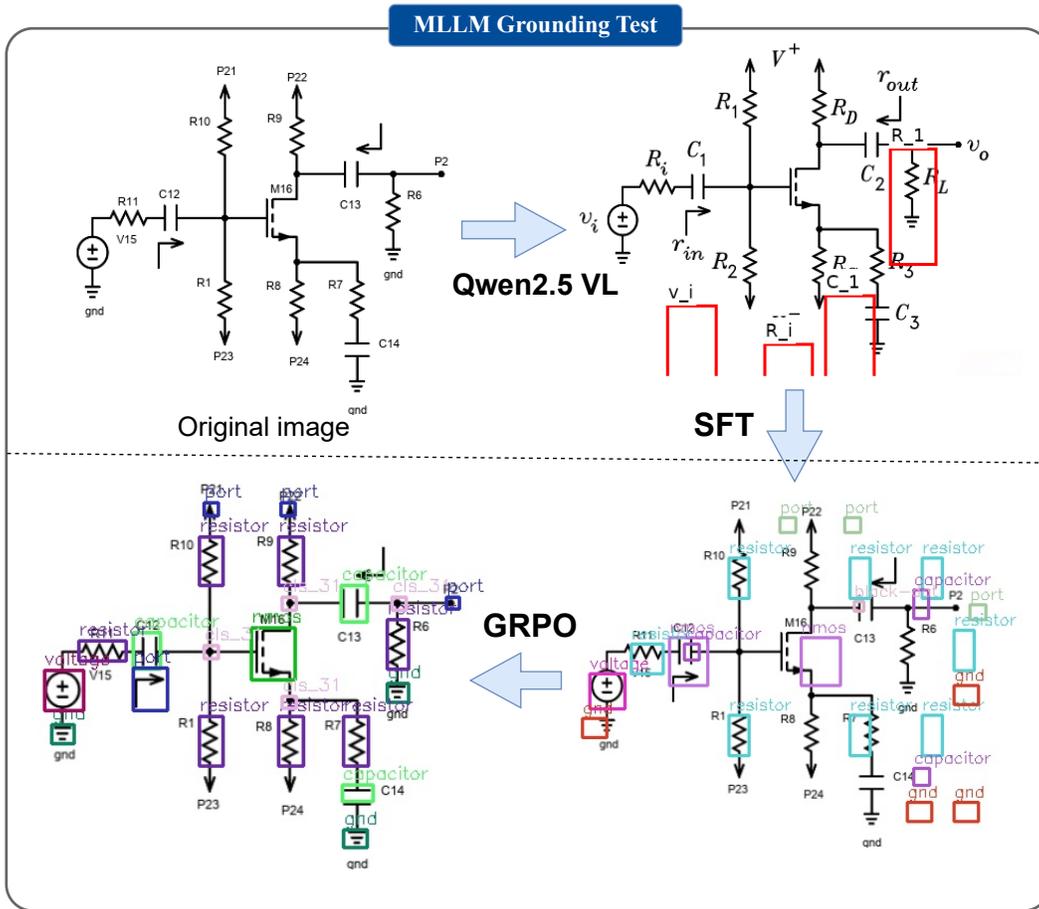


Figure 37: Example of Post-training with Qwen on device grounding.