

# Exploring closed-loop feedback control using experiments in optics

K. A. Jensen, R. J. Larson, and S. D. Bergeson\*

Department of Physics and Astronomy,  
Brigham Young University, Provo, UT 84602

E. F. McCormack†

Department of Physics,  
Bryn Mawr College, 101 N. Merion Ave., Bryn Mawr, PA 19010-2899

November 13, 2018

## Abstract

We present two experiments in closed-loop feedback control. In the first experiment, students control the pointing angle of a laser to “lock” the laser onto a “target.” In the second, students stabilize the pathlength difference in two arms of a Michelson interferometer. These experiments are appropriate for electronics and optics laboratory classes for junior and senior level students.

## 1 Introduction

Feedback control systems are all around us. Cruise control, climate control, temperature regulation in engines, pressure control in industrial steam systems, power supply current and voltage regulators, frequency controllers and many other systems use feedback control. Our own bodies use this kind of control to stand and walk, to watch a passing object, and to regulate body temperature.

Your home or office climate-control system, for example, uses feedback to maintain an inside temperature of 23 °C (your set point). On a cold morning, the heater turns on. When the temperature rises above the set point, the heater turns off and the room gradually cools. Eventually the temperature falls below the set point, and the heater turns on again.

This particular kind of automatic feedback control is relatively crude. It falls into the class of “proportional controllers,” where the feedback signal is proportional to the error signal. In this example, the temperature is not maintained exactly at the set point, but oscillates within a small range around it. As long as the oscillation is not too great, the temperature feels constant, and the control system is adequate.

However, many applications require tighter regulation, and the feedback systems become more complicated. Better regulation requires detailed information about the response time of the system to a given input, the size and frequency content of the perturbing signals, and the necessary regulation tolerances for the system.

Several textbooks describe generalized approaches for implementing feedback control (see, for example, [1]). These treatments typically use mathematical models, differential equations, Laplace transforms, complex algebra, and computer simulations to design the optimum feedback system with the proper gain, roll-off frequency, and phase margin. The strength of these treatments is that they can be applied to all kinds of systems, from tiny voltage control circuits to large manufacturing operations and complex delivery systems.

For many students, these powerful and generalized treatments of feedback control are difficult to penetrate. Somehow the simple physical picture of stabilizing your system output is lost in mathematical models and in the jargon of the discipline.

This paper is an attempt to provide a few simple hands-on illustrations of feedback control in a laboratory setting. In it we walk the reader through two brief and relatively inexpensive implementations of feedback control. The presentation is fairly conceptual. It does not include a mathematical model of the systems. Also missing is a detailed discussion of system stability and the associated methods of modeling, measuring, and implementing high stability control systems. However, we do point out departure points in the discussion where interested readers can find more information in the literature. In our opinion, this introductory presentation gives students (and instructors) an intuitive introduction to the basic concepts of feedback control.

---

\*scott.bergeson@byu.edu

†emccorma@brynmawr.edu

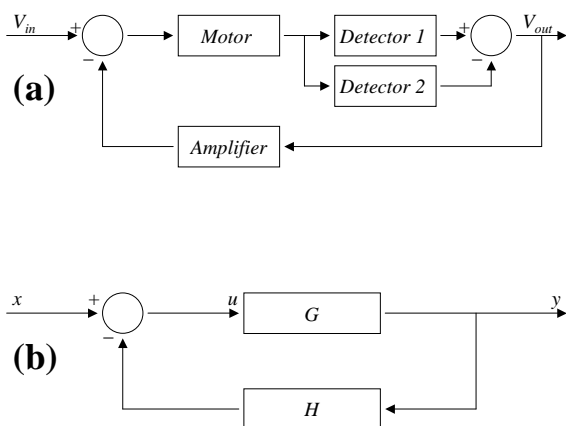


Figure 1: Block diagram of the laser tracker experiment. (a) Detailed diagram. An input voltage ( $V_{in}$ ) drives the motor. The difference of the two detector signals is the output voltage ( $V_{out}$ ), or in our case, the error signal. This error signal is amplified and added to the input voltage to change the pointing of the laser. (b) Traditional block diagram. The system input is  $x$ , and the output is  $y$ . The function  $G$  represents the transfer from voltage in to voltage out, sometimes called the forward gain of the system. The function  $H$  is the feedback gain.

## 2 Laser Tracking Device

Our first feedback control example is a laser tracker—a generic control system. With variations in the pointing device and the detector, the same basic idea is used for missile tracking systems and telescope pointing stabilization. In this lab, students build an automatic pointing system that keeps a laser pointing at the center of a “target.”

The block diagram in Figure 1 outlines the major portions of the experiment. We mount the small key-chain laser-pointer directly on the shaft of a DC motor. The detector is a two-segment photodetector that our students build, as described below.

In Figure 1a, the voltage  $V_{in}$  at the motor changes the laser’s pointing angle. If the laser points at the center of the target, the signal out from the two detectors is identical. The difference of the two detector signals,  $V_{out}$ , is zero. If the laser points a little to the right,  $V_{out}$  is negative (say); and if the laser points a little to the left,  $V_{out}$  is positive. The voltage  $V_{out}$  is amplified and added into the input signal to move the laser back toward the center of the target. This is the essence of closed-loop feedback control: the system output is sampled and compared to the desired output; and the system input is changed in such a way as to bring the system output closer to the desired output.

A more traditional block diagram, typical of those used in feedback-control analysis, is shown in Figure 1b. In the Figure,  $G$  represents the “forward gain” or open loop trans-

fer function that converts the input voltage into the output voltage. For small angular variations about the center of the target, the voltage output  $y$  is linearly proportional to the angular error, and passes through zero at zero angular error. (In other words, the system is linear and homogeneous in a mathematical sense.) The output  $y$  is amplified by the block  $H$  and subtracted from the input  $x$ . The variables  $x$ ,  $y$ , and  $u$  are related by the equations

$$y = Gu \quad (1)$$

$$u = x - Hy. \quad (2)$$

Solving the above equations, the input and output for the system are related by the equation

$$y = \left( \frac{G}{1 + GH} \right) x. \quad (3)$$

The term inside the parentheses is called the closed-loop transfer function for the system.

In the typical case where  $GH \gg 1$ , the closed loop transfer function is  $y \approx Gx/GH = x/H$ . So for large values of the feedback gain  $H$ , the output ( $V_{out}$  in the laser tracker experiment) goes to zero, meaning that the laser points exactly at the center of the target.

This analysis demonstrates that tight regulation of the output requires very high feedback gain. Of course there are practical problems with high feedback gain, depending on the particular system under study. For example, in mechanical systems when the feedback gain is high, the system responds quickly to perturbations. But if the gain is too high, the electronics can overdrive the motors, and damage gears or shafts.

There is another problem with very high feedback gain. In the above analysis we implicitly assume that the system can respond instantaneously to the correction signal. If there is a time delay between when the error signal is measured and when it is corrected, either because of mechanical or electrical limitations, then too large a feedback gain can send the system into oscillation.

In a more sophisticated analysis of the system, the forward gain  $G$  and the feedback gain  $H$  are both functions of frequency. The frequency-dependent gains and their associated phase shifts can be measured by driving the system with sinusoidally varying inputs of different frequencies, then comparing the input and output. With gain and phase shift information, students can model their transfer functions as either high-pass, low-pass, or band-pass filters. Equation 2 becomes a differential equation. The poles and zeros of the equation, which can be found using Laplace transforms and associated mathematical analysis, indicate natural resonances in the system. Obviously, the poles can cause problems unless the feedback gain is sufficiently low at those frequencies. It is possible to suppress the influence of the poles in  $G$  by adding zeros in  $H$  at those frequencies.



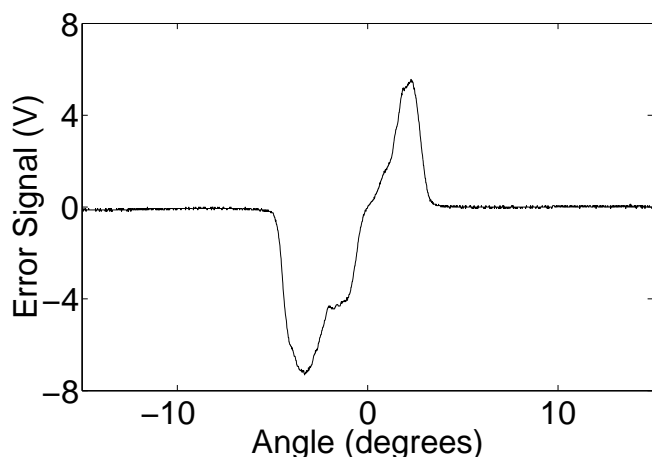


Figure 4: Error signal from our laser tracker. Even though it is not quite symmetric, due to the different sensitivities of our two detectors, it is roughly dispersion-shaped. Near the center, the error signal is linear, and passes through zero volts at zero pointing error.

students to move the laser into the capture range.

The output of U1 is called the “error signal,” the signal that indicates how far from the center of the detector the laser points, and which direction (left or right). In the jargon of feedback control, the amplifier U2 is called the “controller.” In the present case, our controller has only proportional gain. Other kinds of feedback controllers use integral gain or differential gain or combinations of the three.

An error signal generated in our setup is shown in Figure 4. This is the output from U2 (the controller) as the motor sweeps the laser across the face of our detector. Notice that when the laser points directly to the center of the detector, the error signal is zero, making the system homogeneous in the mathematical sense. Also notice that the slope of the error signal is approximately linear, and has a value near 2 Volts/degree. The output of U2 goes directly to the DC motor through a 120 Ohm, 2 Watt resistor. This resistor is chosen to prevent overdriving U2, which at 15 V can source only 0.13 A.

### 2.3 Putting it Together

Now you are ready to put the system together. To make the laser lock onto the target, you first need to get the laser pointing in approximately the right place with the feedback system disabled. Typically, we do this by first shorting out the feedback resistor on U2 (see Figure 3) with a wire, and then turning on the laser pointer and moving the detector so that the laser is centered on it. With the feedback resistor on U2 shorted, the motor should be stationary with no voltage driving it. (The Gain of U2 is proportional to the value of the feedback resistance. If that resistance is zero, the gain of U2 is also zero, meaning zero output voltage.)

When the detector is approximately in the right place,

we remove the wire that shorts out the feedback detector on U2. Assuming that your detectors are working properly, and that none of your op-amps has burned out, one of four things happens.

1. Nothing. If the feedback gain is not large enough, the error signal will not be large enough to make the motor move. So, assuming that everything else is working correctly, try increasing the feedback gain, i.e., increase the value of the feedback resistor on U2.
2. The laser swings off in the wrong direction. Be careful about this. Stray laser beams can pose a safety problem. It means that your error signal has the wrong polarity. The easiest way to fix this problem is to change the inputs on U1. So instead of connecting the right-hand detector to the inverting input and the lefthand connector to the non-inverting input, switch them. You can also achieve the same thing by turning your detector over so that left is now right, and vice versa.
3. The laser-pointing angle oscillates back and forth. The feedback gain is too high. Try reducing the gain by using a smaller feedback resistor on U2. Actually, it is interesting to see this behavior. You can induce it by replacing U2’s feedback resistor with a 0.1  $\mu$ F capacitor. Try it.
4. It works: the laser angle quickly changes to cause the laser to point to the center of the detector. When you get to this point, it is fun to find out how good your locking system really is. Move the target and watch the laser follow it. Move it fast and slow and watch what happens. Find out how close the laser has to be to the center of the target during the initial setup in order to lock the laser to the target. Change the gain (larger and smaller feedback resistors on U2) to see how it affects the stability and speed of response of the lock.

## 3 A Stabilizing Circuit for a Michelson Interferometer

With the rudiments of feedback control in hand, your students may wish to try a more advanced application. A few advanced projects, such as frequency stabilizing a laser diode [3] or a He-Ne laser [4] and intensity stabilizing an LED [5], are described in the literature. In this section we describe stabilizing a Michelson interferometer.

Probably the Michelson interferometer is familiar to all readers [6]. It is shown schematically in Figure 5a. Light enters the interferometer at a beam splitter. Part of the wave is transmitted through the beamsplitter, and part is reflected. Each of these beams is retroreflected by a mirror back to the beam splitter. During the round-trip from

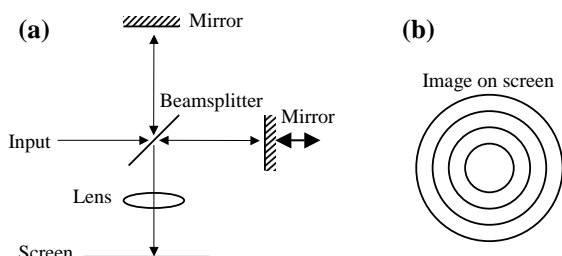


Figure 5: Optical layout for a Michelson interferometer.

the beamsplitter to the mirror and back to the beamsplitter, each beam accrues a phase relative to the input beam. If the round-trip distance is different for the two beams, they also accrue a phase relative to each other. When the two beams are recombined on the beamsplitter, this relative phase can produce constructive or destructive interference, making the output bright or dark.

In the standard arrangement, the output of the interferometer is projected onto a screen by a lens. The output is a concentric set of rings, alternately bright and dark, as shown in Figure 5b. When one of the retroreflecting mirrors moves either toward or away from the beamsplitter, the rings will either collapse into or expand outward from the center of the pattern. If your mirrors vibrate, or if there are air currents in the room, the ring position will fluctuate on the screen. It is this ring position on the screen that we want to control.

Controlling the ring position is quite similar to controlling the laser-pointing angle. It requires a small two-segment photo-detector, with an active area roughly equal to the width of one of the bright rings. The analysis of the locking circuit is identical to the laser pointer. The detector has a “left” and a “right.” The difference of the signals from the left and right sides of the detector indicate the position of the bright and dark fringe relative to the center of the detector. This difference is amplified and fed to a piezoelectric (PZT) crystal, which translates one of the retroreflecting mirrors in the right direction to move the edge of one ring to the center of the detector.

Our detector for this lab was a quadrant photodetector (Hamamatsu S1557). We mounted the detector onto a PC board and combined the four quadrants into two pairs, so that the detector output had only a “left” and “right” signal. The electronics are shown schematically in Figure 6. The laser intensity on the photodetector is much smaller in this lab exercise than in the laser pointer experiment. Accordingly, the summing amplifiers provide some gain (50x).

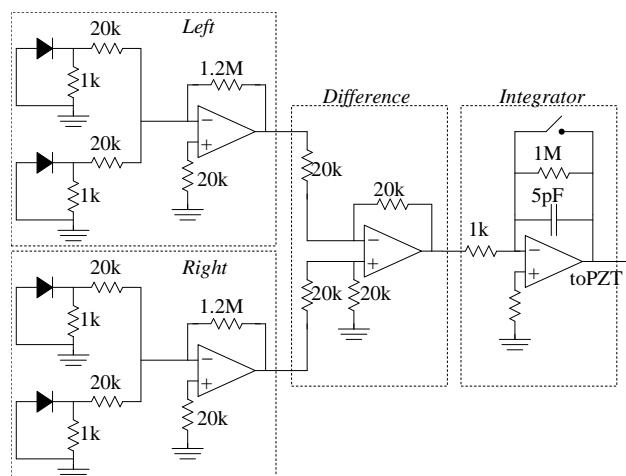


Figure 6: Schematic diagram of the electronics used to stabilize a Michelson interferometer. The op-amps are all the familiar 741's.

The values you use in your setting will depend on the intensity of the laser, the efficiency of your detector, and so forth.

The difference signal is generated by taking the difference between the left and right segments of the detector with a difference amplifier, as shown in Figure 6. The feedback amplifier follows the difference amplifier, with either integral gain (shown in the diagram) or proportional gain.

Not shown in the diagram is an optional offset circuit and high-voltage amplifier. Our PZT crystal (Thorlabs AE0203D04) expands at roughly  $0.08 \mu\text{m}/\text{V}$ , and has a maximum voltage rating of 150 V. It is intended to operate with a positive bias voltage. Reversing the voltage on the device shortens its lifetime, but the device can tolerate moderate negative voltages. In our experiment, we drive the PZT only to  $\pm 10\text{V}$ . In an optimized circuit, the output would be shifted from  $\pm 10\text{V}$  to range from 0V to 20V, and then amplified to range from 0V to 150V. However, these last steps make the laboratory exercise somewhat more involved, and don't significantly increase the student's understanding of closed-loop feedback control.

As before, the students place the detector in roughly the right position with the feedback gain set to zero (i.e., the switch across the capacitor in Figure 6 closed), and then open the switch to engage the “lock” to the fringe. As with most labs, the students' first attempt at locking probably won't work. The list of things to check are roughly the same as those for the laser pointer, and the reader is referred to the list above.

The goal is to have the error signal driving the PZT range over 10 Volts as the detector traverses one ring. If it does not, the feedback gain in the difference amplifier may need to be increased. In Figure 6 the difference amplifier gain is unity. Try increasing this gain by increasing the 20 k-ohm

feedback resistor. Conversely, if the gain is too high, the output of the integrator will saturate at the supply voltage. The 1M-ohm resistor in parallel with the capacitor between the negative input and the output of the integrator is used to keep the integrator from saturating due to inherent offset currents in the 741s. If the circuit refuses to lock, this may mean that the error signal going to the PZT has the wrong polarity. As with the laser pointer, the easiest way to fix this problem is to reverse the inputs to the difference amplifier or to turn the detector over, so left is now right and vice versa.

When the lock works, students can move the detector and watch the fringe pattern change. As the detector moves toward the center of the fringe pattern, the fringes will also collapse toward the center. When the detector moves away from the center of the fringe pattern, the fringe pattern will also expand away from the center. Of course, the PZT can only expand roughly one  $\mu\text{m}$  with these voltages, so this effect can be observed only over a relatively limited range. The switch can be momentarily closed to reset the signal to the PZT to zero in order to continue locking to the same edge as the detector is moved further.

## 4 Acknowledgements

EFM would like to thank M. Noel for his help with the Michelson interferometer experiment. This work is supported in part by a grant from the Research Corporation and from the National Science Foundation under Grants No. PHY-9985027 and PHY-9623569.

## References

- [1] R. C. Dorf, *Modern Control Systems*, (Addison-Wesley, Menlo Park, 1998).
- [2] When a system output is tightly regulated to a desired output, the system is said to be “locked” to the output.
- [3] R. A. Boyd, J. L. Bliss, and K. G. Libbrecht, “Teaching physics with 670 nm diode lasers—experiments with Fabry-Perot cavities,” *Am. J. Phys.* **64**, 1109-1116 (1996).
- [4] K.J. Jones and J.S. Strait, *Optics and Spectroscopy Undergraduate Laboratory Resource Book* (Optical Society of America, Washington, D.C. 1993), pp.7-13.
- [5] L. Sliwczynski and M. Lipinski, “Circuit uses simple LED for near-IR light,” *EDN Magazine*, Issue 18, 1998. This is also available at <http://www.ednmag.com/-ednmag/archive.asp> by following the link to the September 1, 1998 issue.
- [6] E. Hecht and A. Zajac, *Optics*, (Addison-Wesley, Menlo Park, 1974).