

Figure 2


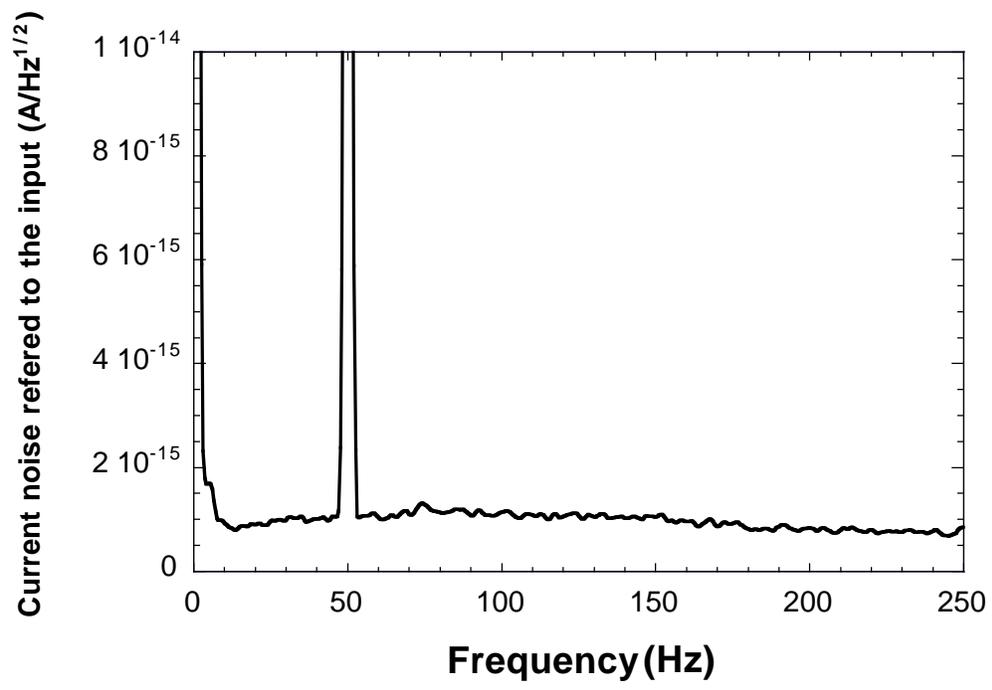


Figure 3

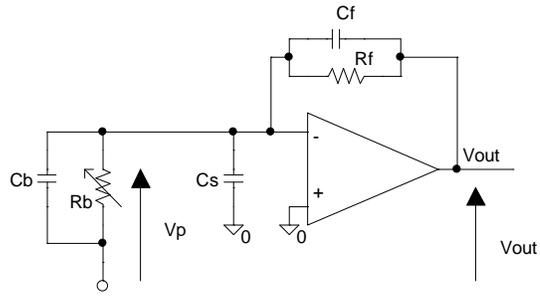

Looped current amplifier

Figure 1

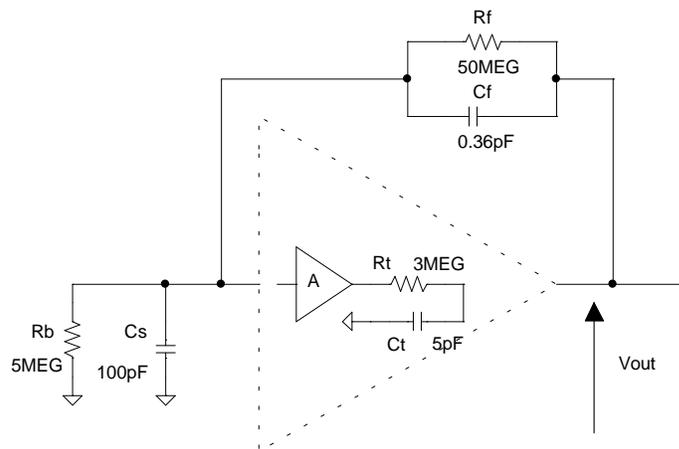


Figure 4

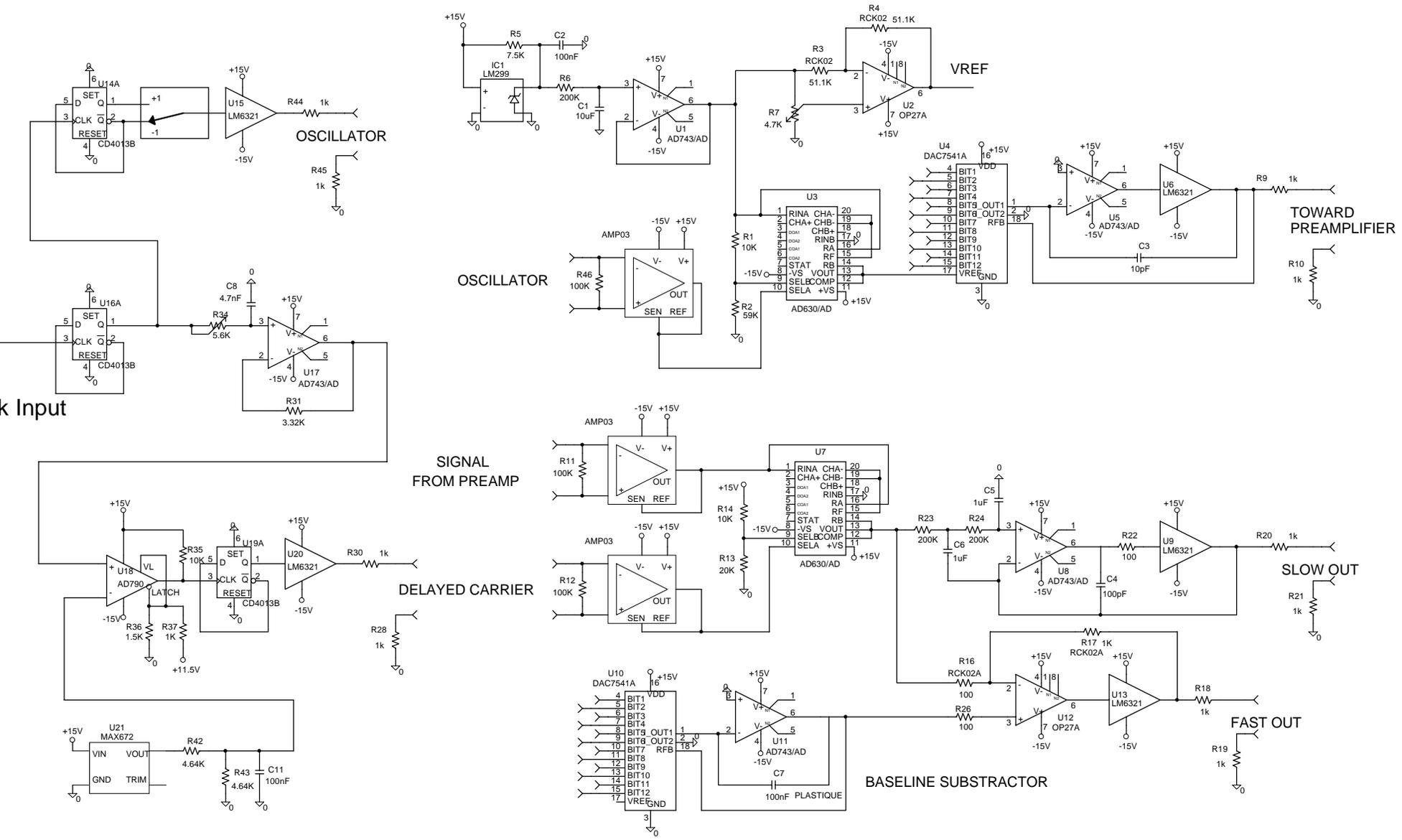


Figure 5

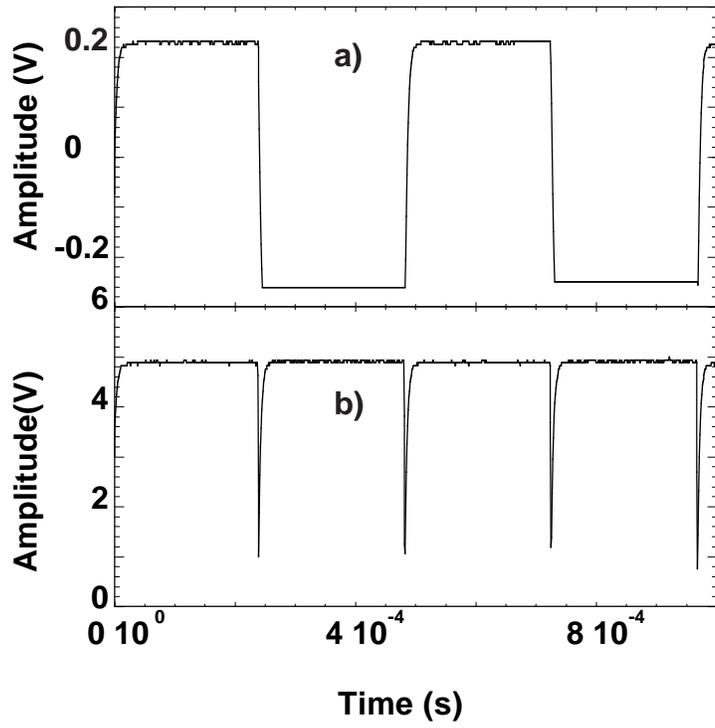


Figure 6)

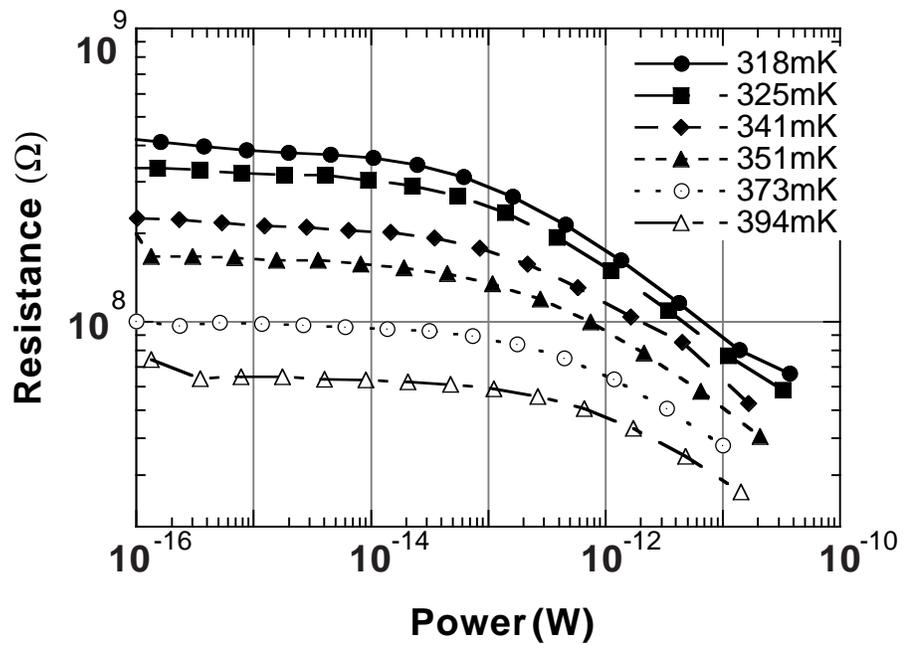


Figure 7

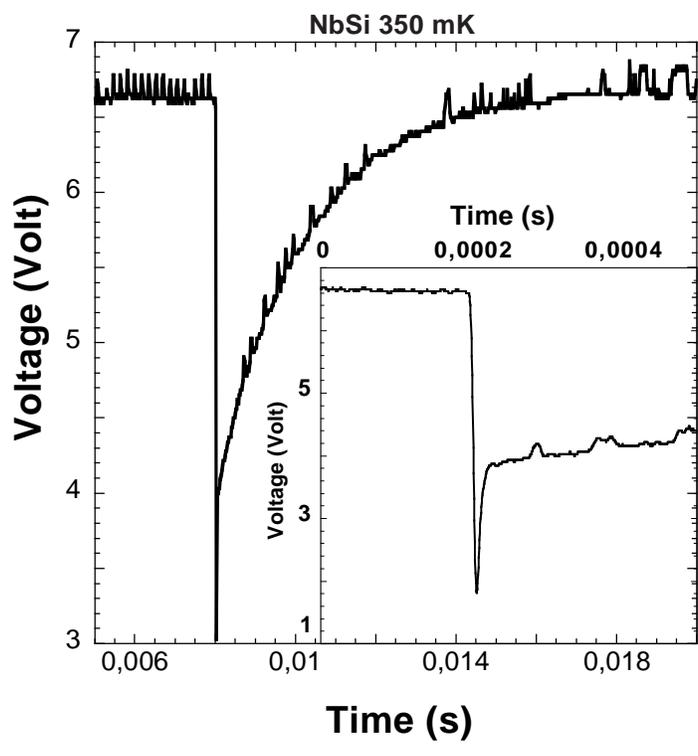


Figure 8)

Lock-in detection using a cryogenic low noise looped current preamplifier for the readout of resistive bolometers

D. Yvon^{1,*}, V. Sushkov^{2,#}, R. Bernard², B. Cahan², O. Cloue³, O. Maillard²,
B. Mazeau³, J.P. Passerieux², B. Paul², C. Veyssiere³.

¹CEA, Centre d'Etude de Saclay, DAPNIA, Service de Physique des Particules,
bat 141, F-91191 Gif sur Yvette Cedex.

²CEA, Centre d'Etude de Saclay, DAPNIA, Service d'Electronique d'Informatique,
bat 141, F-91191 Gif sur Yvette Cedex.

³CEA, Centre d'Etude de Saclay, DAPNIA, Service d'Instrumentation Générale,
bat 472, F-91191 Gif sur Yvette Cedex.

*Corresponding author, electronic mail address: yvon@hep.saclay.cea.fr,
Tel: (33) 0169083911, Fax: (33) 0169086428

#Now at University of California Riverside, IGPP, Riverside CA 92521, USA.

We implemented a low noise current looped preamplifier for the readout of resistive bolometers. We tested the apparatus on thermometer resistances ranging from 1 k Ω to 500 M Ω . The use of looped preamplifier overcomes constraints introduced by the readout time constant due to the thermometer resistance and the input capacitance. Using cold JFETs, this preamplifier board is shown to have very low noise: the Johnson noise of the source resistor (1 fA/Hz^{-1/2}) dominated in our noise measurements.

We also implemented a lock-in chain using this preamplifier. Because of fast risetime, compensation of the phase shift may be unnecessary. If implemented, no tuning is necessary when the sensor impedance changes. Transients are very short, and thus low-passing or sampling of the signal is simplified. In case of spurious noise, the

modulation frequency can be chosen in a much wider frequency range, without requiring a new calibration of the apparatus.

Introduction

Low temperature bolometers address detection problems that require high sensitivity, high-energy resolution and/or low thresholds: X-ray and far infrared spectroscopy, double beta decay, Dark Matter particle searches. To reduce thermal noise they must be operated at temperature generally in the 10-300 milliKelvin range. Their performance critically depends on the quality of the thermometer and on the readout electronics and wiring of the apparatus. This work relies on the experience acquired by the detector community [3, 4]. In ref. [1] we discussed different preamplifiers configurations. This paper describes the implementation and test results of the looped current preamplifier, and the design of a lock-in detection chain using it.

Cryogenic constraints:

We assume in the following that the thermometers used are resistive, of the order of $1\text{ M}\Omega$ resistance, or more. In this context, JFETs, MOSFET, AsGa MESFET and HEMT are natural candidates for front end devices. For example, Alessandrello et al. [5] designed a voltage preamplifier using AsGa transistors, working at a temperature of 1K, and dissipating only 54 mW. The main drawback of MOSFET and MESFET is that up to now, their low frequency noise performance is poorer than the commercially available JFET. Since we expect detector Johnson noises of the order of few $\text{nV}/\text{Hz}^{1/2}$ (few $\text{fA}/\text{Hz}^{1/2}$), we were led to choose JFETs, known to achieve voltage noises of the order of $1\text{ nV}/\text{Hz}^{1/2}$ and current noises of the order of $0.1\text{ fA}/\text{Hz}^{1/2}$. One could consider placing the full preamplifier at cryogenic temperature as in [5], but this is expensive because of liquid helium consumption. We decided to run the preamplifier at room temperature, only the JFET being cold. We used JFET power dissipation ranging from 0.5 mW to 10 mW, per channel: the more power in the JFET, the lower the voltage noise. In some cryostats, the JFET can be anchored to the liquid nitrogen shield, where thermal dissipation is not expensive. But most dilution or ^3He cryostats do not allow this, and the JFET has to be placed at 4K stage. Then the user has to make a

compromise between the helium boiling rate and voltage noise in the JFET. Unfortunately, silicon JFETs do not work at 4 K and to minimise voltage and current noise, the JFET has to be cooled to a temperature between 130 K and 180 K. Thus we had to place the JFET on a computed thermal impedance.

The temperature increase of the bolometer (due to particle interaction or Infrared incoming power) induces a variation of the thermometer impedance. Signals may be slow: from 1 second to few μs . We wish then to use a DC coupled preamplifier. But, when powered, the JFET self heats to a temperature around 150 K. Gate to source JFET voltage do depends on the temperature. To prevent the amplification of the offset voltage one may use a differential preamplifier [6]. This option is expensive in a cryogenic environment, because it requires four wires per channel to bias the JFETs of the first stage, doubles the power dissipation at 4 K, and increases the white voltage noise by a factor of $\sqrt{2}$. We choose to use single JFET, with the drawback that it is more sensitive to pickup noise and a biasing regulation of the JFET is necessary. This JFET biasing regulation will bring a very low frequency high-pass filter behaviour in the preamplifier.

The coldest stage of most low temperature cryostats cannot handle power dissipation larger than 1 μW . Thus the readout JFET cannot stay right next to the detector. Typically, front end JFETs are placed at 20 to 40 cm from the detector. Due to the thermometer high impedance, microphonics and electromagnetic noise pickup as well as capacitance of the wiring then become crucial problems, and great care has to be taken, to optimise the wiring from these points of view. We decided to design and order low capacitance, low noise cryogenic coaxial cables. Their performance turned out to be quite satisfactory.

To summarise the configuration, we chose to design a low noise wide bandwidth, DC coupled JFET preamplifier. Active regulation of the current flowing through the JFET will high-pass frequencies below 0.1 Hz. The power applied to the JFET range from 0.5 mW to 10 mW. It is thermally anchored to the 4.2K liquid helium

or liquid nitrogen bath, depending of the cryostat schematic, through computed thermal impedance so as to achieve a stabilised temperature close of 150 K.

Preamplifier design

From the electronics point of view, the goal was to design a state of the art low noise preamplifier to achieve the best threshold and resolution performances. So as to allow detector characterisation and optimisation, readout had to induce minimal distortion of the thermal signal of the bolometer. But large thermometer impedance and stray capacitance low-pass the signal. Since reference [2] we rediscovered and enhanced what Silver et al. [7] had previously used to readout fast microcalorimeter.

Schematic

Figure 1 shows the simplified schematic of the looped preamplifier configuration. A heat pulse induces a resistance change of the thermometer. A biasing voltage V_p is applied to the thermometer. The operational amplifier actively regulates the voltage at its inverted input to be zero and the stray capacitance C_s does not charge. Thus the signal is not low-passed with the time constant $R_b C_s$.

$$V_{out}(s) = -V_p \frac{R_f}{1+s R_f C_f} \frac{1+s R_b C_b}{R_b} \quad \text{where } s \text{ is the Laplace variable, } R_b$$

and R_f are the bolometer and feedback resistance, C_b , C_f are the bolometer and the feedback stray capacitance, and C_s the input capacitance of the preamplifier.

In the limit of small thermometer impedance change,

$$\Delta V_{out}(s) = \frac{R_f}{R_b^2} V_p \frac{\Delta R_b}{(1+s R_f C_f)}$$

To achieve this in the context presented in the introduction, we designed a preamplifier board whose schematic is given in figure 2.

The electronic circuit runs at room temperature outside the cryostat, except for the JFET, staying at 77K or 4 K, and the bolometer and feedback resistor on the cold plate of the cryostat.

Preamplifier loop

The preamplifier loop (figure 2) includes two circuits. First a very fast common base current amplifier of gain 5 amplifies the small signal current coming from the

JFET. This amplifier raises the current above the input current noise of the following AD844. The AD844 further amplifies the current with an open loop transresistance gain of $3 \text{ M}\Omega$ yielding the preamplifier output. A feedback resistor (R 18) has been added between the output and inverted input of the AD844 to allow the tuning the open loop gain of the preamplifier.

FET biasing circuit

From the basic schematic, when no voltage bias is applied, we expect the output of the preamplifier to be close to ground. Since the gate current of the cold FET is negligible, this is the equilibrium condition of this preamplifier too. To achieve this, we have to adjust the JFET source voltage, to ensure the proper DC conditions. This voltage depends of the FET temperature and an active correction of offset is necessary to prevent the output from saturating. This is the purpose of the OPA111 based integrator circuit. Assuming no input voltage from “Polar DC” (a lock-in symmetrical square waveform is used), the integrator integrates the output voltage of the preamplifier. Through R22, the OP111 output drives the JFET source voltage and cancels the offset drifts. The time constant of the integrator has to be much slower than the pulse time scale, since it high-passes the input signals. We chose $\tau=1 \text{ s}$ to ensure that a preamplifier is active one minute after being powered. The biasing voltage is then low-pass filtered to suppress noise from noise OPA 111.

Thermometer biasing circuits

The biasing of the thermometer may look odd in this configuration. Two common biasing conditions had to be implemented: when used to measure slow signals AC biasing and lock-in detection is often optimal, when used with fast bolometers for particle interactions DC biasing is preferred. The difficulty comes from the fact that modulation is applied to the lowest noise stage of the preamplifier so the modulation voltage noise has to be lower than preamplifier noise.

Good oscillators generate signals of volts amplitude with noise level lower than $100 \text{ nV/Hz}^{1/2}$. It has to be divided by at least a factor 100 to meet our requirements.

This is the purpose of the R28 and R29 resistor divider. The carrier signal then feeds directly the thermometer. We emphasise that the JFET biasing system requires the modulation frequency to be above 20 Hz.

Applying a DC voltage to bias the thermistor is somehow incompatible with the FET biasing circuit. If a constant voltage V is applied through the AC biasing circuit the bolometer, the FET biasing circuit changes the FET source voltage to recover ground at the preamplifier output. The FET gate potential rises to $V_g = \frac{VR_f}{R_f + R_b}$, inducing an

effective polarisation voltage on the bolometer $V_p = V \frac{R_b}{R_f + R_b}$. Typical operating

biasing potentials of thermometer are in the 10 mV range, and the resistor ratios are typically of 10. This induces gate potentials of few 100 mV, and sets two potential problems. First when the gate wire is no longer grounded, microphonics interference happens through the varying capacitance between the gate wire and its grounded shielding. Second, because of low power cryogenic requirements, the FET is run with a drain voltage below 3 volts. Changing the source and gate potential by a 100 mV may drive it out of saturation zone, (where its has lower gain and its white noise increases).

To prevent this, we implemented an additional feature for DC biasing. We apply a DC Voltage V_{DC} at the input of the DC polarisation AMP03 chip and the AC biasing circuit is grounded. This changes the reference voltage of the JFET biasing, the preamplifier

output rises V_{DC} and the FET gate potential rises to $V_g = \frac{V_{DC}R_b}{R_f + R_b} = V_p$ much lower than

the previous configuration. The drawback is that the output offset has to be removed before further amplification of the signal, but we assumed our signals were relatively fast in this detection mode. This is the purpose of the C5 capacitor, when not shorted.

Post amplification and power supply

The preamplifier has no symmetry to implement common mode noise rejection. Very careful power supply noise filtering is required. We use low noise linear power supplies and the classical low pass filter around 2N2905, BC560C and 2N2219A, MPSA18 transistors to power the card. To prevent “motorboarding” and to further filter

the power supply, we added large value capacitors on the power supply lines of the preamplifier.

The AD829 operational amplifier and the LM6321 driver provide post amplification and allow secure driving of most post stage electronic cards. To reduce pick up in the incoming and outgoing lines, we used shielded twisted pair cables, differential amplifiers (AMP03) at the voltage inputs and we symmetrised the impedance of the two leads using $1\text{k}\Omega$ resistors and we kept this design philosophy in the lock-in boards design.

Tests results

Noise measurements

Noise measurements were performed in two conditions. The first one with a 300 K JFET, and liquid nitrogen cooled high value feedback resistors. We operated our apparatus with feedback resistors up to 10 G Ω the thermometer being open circuited. The bandwidth of the preamplifier was limited to $\omega_f = 1/(R_f C_f)$. We measured (figure 3) current noise referred to the input as low as 10^{-15} A.Hz^{-1/2}, dominated by the Johnson noise of the feedback resistor. Noise measurements were also performed within a cryostat. As described in the introduction, the JFET ran at 150 K in a 77 K environment. However we use regular cryogenic coaxial wiring, because we cannot afford the heat load of the available low noise coaxial wires. Not surprisingly, the observed spectrum on a 10 M Ω resistor at 320 mK displays strong microphonics and 50 Hz contamination. Nevertheless, on the plateau we measure $i_n \sim 1.8$ fA.Hz^{-1/2}, corresponding to the predicted value of resistor Johnson noise. Previous measurements using a 50 M Ω cold resistor and a dilution fridge at 20 mK, showed the cold JFET current noise is as low as 0.2 fA.Hz^{-1/2}.

Bandwidth measurements

For this test, we placed the cold circuits in the 300 mK cryostat. A 1 M Ω resistor was readout by a NJ132L Interfet JFET, and placed in series with a $R_f = 10$ M Ω MiniSystem cold resistor [13]. Then we plugged a regular voltage amplifier [2] and measured a bandwidth of 2.05 kHz, corresponding to an input capacitance of 80 pF. Plugging the above current preamplifier, we measured a bandwidth of 45 kHz, much larger than the previous one as expected. The corresponding stray capacitance on the feedback resistor is $C_f = 0.36$ pF, in accordance with the provider data sheet value of 0.2 pF, and additional capacitance due to the wiring of the surface mount resistor chip.

Stability

When we first ran this preamplifier on a cold very resistive bolometer ($R_b > R_f$) with $R_f = 10^7 \Omega$ and $C_f = 0.2$ pF, we saw low frequency oscillations of the amplifier, similar to “motorboarding”. The surprising fact was, the slower the preamplifier, the stronger were the oscillations. This effect can be understood as the following. Figure 4 shows a model of the poles of the circuit. The gain 5 current amplifier is fast enough so that its effect is negligible in this discussion. The first pole of the open-loop amplifier is dominated by AD844 chip. The cutting angular frequency ω_1 can be easily computed from the transresistance of the chip $R_t = 3 \text{ M}\Omega$ and the known internal lag capacitor $C_1 = 5$ pF: $\omega_1 = 1/(R_t C_1)$. Assuming that the thermometer has a very large impedance, two other poles are important: $\omega_b = \frac{R_f + R_b}{R_b R_f C_s}$ and $\omega_f = 1/(R_f C_f)$. ω_1 and ω_b are driving instability, ω_f is a stabilising pole. The purpose of the current looped preamplifier is to move the first pole. To ensure stability ω_f has to be less than ω_1 . That was not the case since $\omega_1 \sim 6.6 \cdot 10^4 \text{ rad.s}^{-1}$ and $\omega_f \sim 5 \cdot 10^5 \text{ rad.s}^{-1}$. To ensure stability, and keep a relatively large bandwidth, we reduced the transresistance gain of the AD844 using the 200 k Ω R18 resistor, and achieving $\omega_1 \sim 10^6 \text{ rad.s}^{-1}$ and stability on high impedance thermometer.

Then, starting our preamplifier when the cryostat was at 4K, and the thermometer of few Ohms impedance, we observed the output of the preamplifier oscillate rail to rail at a few Hz. This behaviour does not happen when the thermometer is of high impedance ($R_b/R_f > 0.01$). It is related to the FET biasing circuit, which is a second slow loop. When the DC gain of the loop $\frac{R_f}{R_b} \frac{R_{21}}{R_{19} + R_{21}}$ is greater than unity the circuit enters slow oscillation. If necessary, this oscillation can be prevented by placing a cold resistor in series with the bolometer, without worsening the noise performance.

Practical limitations.

From the above discussion, two technological limitations to the rise-time appear. The first one comes from the availability of low temperature feedback resistors. The rise time is set by the feedback resistor pole $\omega_f = 1/(R_f C_f)$. Most high ohmic value resistors diverge to very high resistance, when placed at temperatures lower than 4K. Using the MSI 10 M Ω resistors[13] available on the market, ($C_f = 0.2$ pF) we expect a rise time of 4.4 μ s, independent of the thermometer impedance. The second comes from the stability criterion: ω_f has to be lower than ω_1 . This sets the shortest rise time achievable with this board to 1 μ s.

It must be pointed out that the thermal relaxation time of the bolometer is slower using the looped current amplifier configuration than a looped or unlooped voltage amplifier. If this turns out to be a problem, the same preamplifier could be used as a very good looped voltage amplifier [1]. Also, under extremely strong biasing, the detector preamplifier chain could become thermally unstable. This was never observed by us as expected from simple calculations (see for example in reference [1]).

Lock-in design using the current amplifier

When the thermal signal is slower than a few tens of millisecond, classical readout electronics includes a lock-in amplifier to extract the signal from 1/f preamplifier noise and microphonics. We designed test boards to demonstrate the performance and convenience of a lock –in design using a current amplifier. So as to simplify design and debugging we placed the preamplifier, oscillator and modulator/demodulator on three distinct boards. Necessary signal exchanges was achieved through shielded twisted pair cables, to prevent pick up. This choice necessitated the use of numerous differential receivers and driver chips. In future implementations of this circuit, these could be removed using a single board design. The test boards were made of a few modules, whose schematics are drawn at figure 5.

Oscillator

A pulse generator provides an adequate frequency reference that drives the modulator and the time-delayed carrier mono-polar square waves. These are used to trigger the modulator and demodulator AD630 chips.

Modulator

The modulator provides a square wave signal of chosen amplitude. So as not to degrade the resolution of measurements three main features have to be achieved. The noise on the square wave signal has to be smaller than $100 \text{ nV} \cdot \text{Hz}^{-1/2}$. Chips available on the market meet this requirement easily. More difficult is to achieve an amplitude stability of few $10^{-6}/^{\circ}\text{C}$ on a digitally chosen signal amplitude. This uncommon feature can be achieved on square wave signals using high performance DAC resistor bridges and a good voltage reference. The LM299 voltage reference output is chopped by the AD630 to produce a fixed amplitude stable symmetric square wave. This square wave enters the reference voltage input of a DAC 7541A and is divided by the DAC high stability resistor's bridge and AD743 operational amplifier. The C3 capacitor allows smoothing of ringing due to stray capacitors in the DAC. The output provides the square wave biasing of the thermometer. Every part or chip relevant for the amplitude stability was chosen to have a temperature coefficient smaller than $10^{-6}/^{\circ}\text{C}$.

Demodulator

The preamplifier provides a detected square wave with minimal distortion (figure 6a): the phase shift (time delay) is small and does not depend on the sensor impedance, but only on the feedback resistor. Compensation of time delay might be unnecessary. If implemented, it will reduce transient amplitudes and the delay adjustment is fixed: no tuning is necessary when sensor impedance changes.

The demodulator block has to meet the same amplitude stability requirement. SSM2141 chips provide adequate temperature coefficients. Then the time-delayed oscillator output triggers the AD630 chip that rectifies the square wave. The resulting signal is close to a constant voltage (figure 6b) with fast spike down to ground. The DC value of this voltage is directly related to the thermometer impedance, and is an

important datum to register. Thus we implemented a “slow output” after a 2 Hz low-pass filter. Most of the time however we are interested in faster very small signals. Thus for the “fast output”, we subtracted the signal DC value, and further amplified the signal using an OP27A. To generate the offset tension, we used again a DAC7541A chip, and the same voltage reference as for the modulation (same board). If this voltage reference drifts, then it generates no DC signal on the fast output. After baseline subtraction, in most applications a temperature coefficient of $10^{-4}/^{\circ}\text{C}$ is adequate. Commercial products commonly achieve this.

Baseline subtraction and filtering issues.

Baseline subtraction induces another noise contribution. When low-passing the OP 27A output, we get the average DC value of the signal. This value is offset from the “true” value by the average of the integral of transients and can be easily corrected by the offset subtraction. This implies that the gain of the lock-in loop depends somewhat on the modulation frequency. If the modulation frequency is unstable, the gain and induced offset changes too. This additional noise voltage is less than e_{offset} given by:

$$e_{\text{offset}} = \frac{ATf}{G} \left(\frac{\Delta f}{f} \right)$$

where e_{offset} is the equivalent noise contribution ($\text{V}\cdot\text{Hz}^{-1/2}$) at the input of the preamplifier, A and T are the amplitude and the duration of transients, G is the gain of the electronic chain before subtraction, and f is the modulation frequency. For typical values (A= 10 V, T= 10 μs , G=5.10³, f=1kHz), a frequency stability of 10^{-4} is enough to ensure negligible noise contribution.

After demodulation and offset subtraction, the output signal has to be low-pass filtered in order to get rid of the short transients (Figure 6b). This is relatively easy, since the transients are of high frequency (more than 50 kHz) far above the harmonics of regular modulating frequencies. But unlike in most lock-in designs in order to remove the high frequency preamplifier white noise, the filter has to be at least of second order [1].

Tests results

We measured noise spectrum of the full lock-in chain. All of measurements showed that the noise of the lock-in chain is dominated by the preamplifier contributions. We then used the above preamplifier and lock-in to study two bolometers, one constructed by Infrared Labs [11] and one fast bolometer model useful for particle detectors.

As a validation tool for these developments we constructed a 300 mK cryostat and instrumented it with four channel cold JFET readout electronic. The cryostat is a Infrared Space Observatory (ISO) test cryostat [8] consisting of liquid nitrogen cooled first stage on which the JFET and wiring are thermally anchored, then of a pumped ^4He 1.8 K cold plate, where all the wiring is thermalised. Finally, we bought a single shot pumped ^3He cryocooler from L. Duband[9]. This apparatus achieved a temperature of 315mK, limited by the thermal load from the 25 cryogenic coaxial cables used in the readout electronics, with a cold plate of 100 cm² surface. Computer control and data acquisition was achieved through a GPIB interface. The following measurements have been made using the above presented current loop preamplifier and when necessary the lock in chain.

Infrared bolometer

We first measured the IV curves of the Infrared Labs bolometer [11] kindly provided by J-M. Lamarre. Figure 7 plots the results of the measurements, presented as the “blind” bolometer impedance (no infrared light power incoming the bolometer) versus of the biasing thermal power load. This allowed to determine the thermometer law $R(T)$ and the thermal conductivity to bath. We find $R(T) = R_0 \left(\frac{T}{1K} \right)^{-8.3}$, with $R_0 = 27.9 \text{ k}\Omega$, and a heat leak behaviour at 373 mK well fitted at low power by : $P(\Delta T) = 2.9 \cdot 10^{-9} (\Delta T)^2$, P in Watt and ΔT in Kelvin. This shows that the heat leak is complex, not dominated by a Kapitza resistance or a metal-like conductivity.

These measurements were performed at a modulation frequency of 20 Hz, on thermometer resistances up to 450 M Ω . Using a regular voltage preamplifier, the input

stray capacitance would have required measuring at modulation frequencies below 1 Hz, considerably lengthening data taking, an annoying fact on a single shot cryostat! Furthermore, in case of spurious noise, the modulation frequency can be chosen in a much wider frequency range, without requiring a new calibration of the apparatus.

Pulses data acquisition

We use the current looped preamplifier to readout a fast bolometer model, made of a $8 \times 12 \times 0.3 \text{ mm}^3$ Sapphire test plate onto which an NbSi thin film thermometer [10] is evaporated. Heat leak was made of a gold wire, wire-bonded on the Sapphire plate. An ^{241}Am alpha source induced the detected heat pulses.

Figure 8 plots typical alpha events obtained at a temperature of 350 mK. The pulse shape displays two different regimes. A fast part, and a slow relaxation. As stated in [10,12], the fast part is due to conversion of out of equilibrium phonons in the thin film thermometer: the thermometer overheats relative to the Sapphire substrate. Within few tens of microseconds, the thermometer temperature relaxes to the substrate temperature, and then the whole device temperature relaxes through the heat leak. Had we been using an unlooped voltage amplifier the fast signal part would have been low-passed filtered by the input capacitance and thermometer resistance (80 pF and 300 k Ω) of this device. Historically, this effect remained unknown until it was found on a low resistance thermometer (few k Ω).

Conclusion

We implemented a current looped preamplifier for the readout of resistive bolometers. We tested the apparatus on thermometer resistances ranging from 1 k Ω to 500 M Ω . We showed that the looped current amplifier allows much flexibility and convenience in the design. Looped preamplifier overcomes constraints introduced by the readout time constant due to the thermometer resistance and the input capacitance. It allows the study of pulse shapes and detector behaviour that would be unnoticed using unlooped voltage amplifier. Using a cold JFET, this preamplifier board is shown to

have very low noise: the Johnson noise of the source resistor ($1 \text{ fA/Hz}^{1/2}$) dominated in our noise measurements.

We also implemented a lock-in chain. We showed that it is very convenient to use a looped preamplifier in a lock-in chain, with square wave biasing. Compensation of phase shifts might be unnecessary. If implemented, the adjustment is fixed, no tuning is necessary when sensor impedance changes. Transients are very short, and thus low-passing and sampling of the signal is simplified. In case of spurious noise, the modulation frequency can be chosen in a much wider frequency range, without requiring a new calibration of the apparatus.

Acknowledgement

We are grateful to J.L. Bret and A. Benoit, (CRTBT Grenoble, France), for stimulating discussions, to J-P.Torre (Laboratoire d'aéronomie, Verrière le Buisson, France), L. Dumoulin and P. Garoche (Universite d'Orsay, France) for their advice in designing low noise cryogenic wiring of the cryostat. We want to thank M. Taluro (DESPA, Observatoire de Paris-Meudon) for his advice and help using the ISO cryostat and J. Rich for reading proofs of this paper.

References

[1] D. Yvon and V. Sushkov, submitted to IEEE TRANSACTIONS ON NUCLEAR SCIENCE, “Low noise cryogenic electronics: preamplifier configurations with feedback on the bolometer”

[2] D. Yvon et al, “Low noise voltage and charge preamplifiers for phonon and ionization detectors at very low temperature”, Nucl. Inst. Meth. in Phys. Res. A 368 (1996) 778-788

[3] L. De Carlan et al., “Discrete analog electronics for high-resistivity silicon detectors used for X-rays and γ -rays spectroscopy in whole-body monitoring” Nucl. Inst. Meth. in Phys. Res. A 380 (1996) 371-375

[4] V. Radeka, “Low-noise techniques in detectors”, Ann. Rev. Nucl. Part. Sci. 38 (1988) 217-277; N. Madden private discussions.

- [5] A. Allesandro et al., “Cryogenic voltage-sensitive preamplifier using GaAs MESFETs of low 1/f noise”, Nucl. Inst. Meth. Phys. Res. A 295 (1990) 405-410
- [6] D.V. Camin et al., Alta Frequenza 56 (1987) 347
- [7] Silver E. et al., “High resolution x-ray spectroscopy using germanium microcalorimeters”, in “X-Ray, and Gamma-Ray Instrumentation for Astronomy and Atomic Physics“, SPIE, vol. 1159 EUV, (1989) 423-432
- [8] Observatoire de Paris, Département de Recherche Spatiale DESPA, 5 place Janssen, 92195 Meudon Cedex, France.
- [9] L. Duband, CEA-Grenoble, Service des Basses Températures, 17 Av. des Martyrs, F-38054 Grenoble Cedex 9, France.
- [10] S. Marnieros et al., “Development of massive bolometers with thin film thermometers using ballistic phonons”, Proc. of the VIIth International Workshop on Low Temperature Detectors (LTD-7), Max Planck Institute of Physics, Munich, (July 1997) 134-136.
- [11] Bolometer #1876, Infrared Laboratories, 1808 East 17th Street, Tucson, AZ 85719–6505, USA.
- [12] D. Yvon et al., “Evidence for signal enhancement due to ballistic phonon conversion in NbSi thin film bolometers”, Nucl. Inst. Meth. in Phys. Res. A370 (1996) 200-202
- [13] Mini-Systems Incorporated, Attleboro, MA 02703, USA

Figures captions

Figure 1) A simplified schematic of the current looped preamplifier configuration. R_b and C_b are the bolometer thermometer resistance and capacitance. R_f and C_f are the feedback resistor resistance and capacitance. C_s is the input stray capacitance of the preamplifier.

Figure 2) Schematic of the current preamplifier board we implemented. For clarity we omitted the decoupling capacitors and resistors on the power lines of the operational amplifier chips, and first stage preamplifier. We delimit the preamplifier loop, the JFET biasing circuit, the thermometer biasing circuit and the second stage amplifier and driver. See text for more details.

Figure 3) Noise spectrum referred to the input, as measured with the current looped preamplifier and $R_b = 1\text{ G}\Omega$. The flat noise level is measured at $1.0\text{ fA}\cdot\text{Hz}^{-1/2}$. AC Industrial noise pick up in cables at 50 Hz is clearly seen. The bandwidth was limited by the stray capacitance of the $10\text{ G}\Omega$ feedback resistor (250 fF).

Figure 4) Simple model of the circuits poles. Assuming C_b is negligible three main poles appear: $\omega_b = \frac{R_f + R_b}{R_b R_f C_s}$ and $\omega_f = 1/(R_f C_f)$ and ω_1 first pole of the operational amplifier. ω_b and ω_1 are driving instability, ω_f is the stabilising pole. Since in practice ω_b is the lowest, to ensure stability ω_1 has to be at higher frequency than ω_f .

Figure 5) Modular schematic of the lock-in chain we developed. The classical functions are implemented: Modulator, preamplifier, demodulator, and baseline subtraction. The design is simplified because of the fast risetime of the current looped preamplifier: when the thermometer resistance changes, no adjustment of the phase of the demodulator is necessary. If, due to difficult noise conditions, it is necessary to

modulate at a frequency above ω_b , we do not suffer from signal amplitude loss, and therefore, there is no need to recalibrate the detector and electronics chain.

Figure 6) Waves forms as measured at different stages of the lock-in board. The bolometer circuit was simulated with a 1 M Ω passive resistor (R_b), C_s was set to 100 pF, and R_f to 10 M Ω . The used a modulation angular frequency 4π krad.s⁻¹, above $\omega_b = 10$ krad.s⁻¹. Figure 5a shows that the modulation square wave is minimally distorted at the output of the preamplifier. After demodulation and amplification (no offset subtraction requested, figure 5b), the signal is rectified, transients are very fast and thus relatively easy to filter out.

Figure 7) Measured charge curves (resistance versus power) of an Infrared Labs Bolometer placed in and ³He single shot cryostat, using this preamplifier board and lock-in. We were able to measure thermometer impedance with power dissipation on the bolometer down to 10⁻¹⁶ Watt.

Figure 8) Fast pulses registered on digital oscilloscope, from a home-made bolometer model using a Sapphire test plate and an evaporated NbSi thin film thermometer [10]. Two ²⁴¹Am alpha pulses are shown. The trace is plotted on the millisecond time scale and displays the thermal relaxation through the heat leak. The second is a zoom on the fast part of the pulse (time scale of a few hundred of milliseconds). Without loop amplifier technology, the low pass filter due to thermometer impedance and input capacitance would wash out the fast pulse.